

WAR II SURPLUS

CIRCUITS

ARC 5 X MITTER

calibration will be correct if 1.0 Mc. is mentally added to the dial reading.

Plate and screen voltage should be applied to the p-a stage. The transmitter should be tuned to 7.2 Mc. and loaded to the antenna. The p-a padding condenser C-67 should be resonated for minimum plate current and then locked. C-65 should always be re-resonated whenever there is a major change in antenna loading or coupling.

Transmitter Conversion for 20, 15 and 10 Meters

The conversion of the 4.0-5.3 Mc. transmitter for high frequency use is based upon retaining single dial control and the use of one doubler stage.

The space left by the removal of the electron eye tube and the calibrating crystal may be used for a 6AG7 doubler and a slug tuned coil. The basic circuit for 20, 15 and 10 meters is shown in Figure 22.

The basic filament and socket modifications as described for the low frequency units should be completed. For 20 and 15 meters, the 6J5 oscillator must work on the 7-Mc. band, using the existing dial calibration lines, with new figures. The main winding of the oscillator coil should be reduced to 12 turns, by removing

turns from the top of the coil. The oscillator tuning condenser, C-63, should have all but two rotor plates removed. One of the remaining plates should be the slotted one for tracking adjustment.


At the oscillator coil terminals under the chassis, C-62 (the neutralizing condenser) should be removed and the bias return of the doubler stage moved from the center tap of the coil to the free end.

An octal socket is placed in the crystal calibrator socket hole. The electron eye socket hole is covered by a small metal plate. A National XR-50 slug tuned coil is mounted in the center of this plate with its slug adjustment above the chassis. This coil (L1) is wound with 10 turns of No. 24 enamelled wire, spaced to occupy the full winding length. Condenser C16 con-


C-58—0.05/0.05/0.05 μ fd., 300v.
C-59—175-185 μ fd.
C-60—air padder.
C-61—0.006 μ fd., mica.
C-62—neutralizing condenser.
C-63, C-65, C-67—220 μ fd.
C-64—0.002 μ fd., 1000v.
C-66—0.01 μ fd., 2500v., mica.
C-68—3.0 μ fd., 750 p.p.m.
K-53—D.p.s.t. relay, 300-ohm coil.

K-54—S.p.d.t. antenna relay, 90-ohm coil.
R-67, R-75—51,000 ohms.
R-68, R-76—20 ohms.
R-69—1.0 megohm.
R-70—1000 to 1500 ohms.
R-71—126 ohms, 7w.
R-73—5100 to 15000 ohms.
R-74—15,000 ohms.
R-77—390 ohms.
R-78—51 ohms.
RL-50, RL-51—parasitic suppressors on 51-ohm resistors.

Fig. 18. This is a typical wiring schematic of the 274N series transmitters.

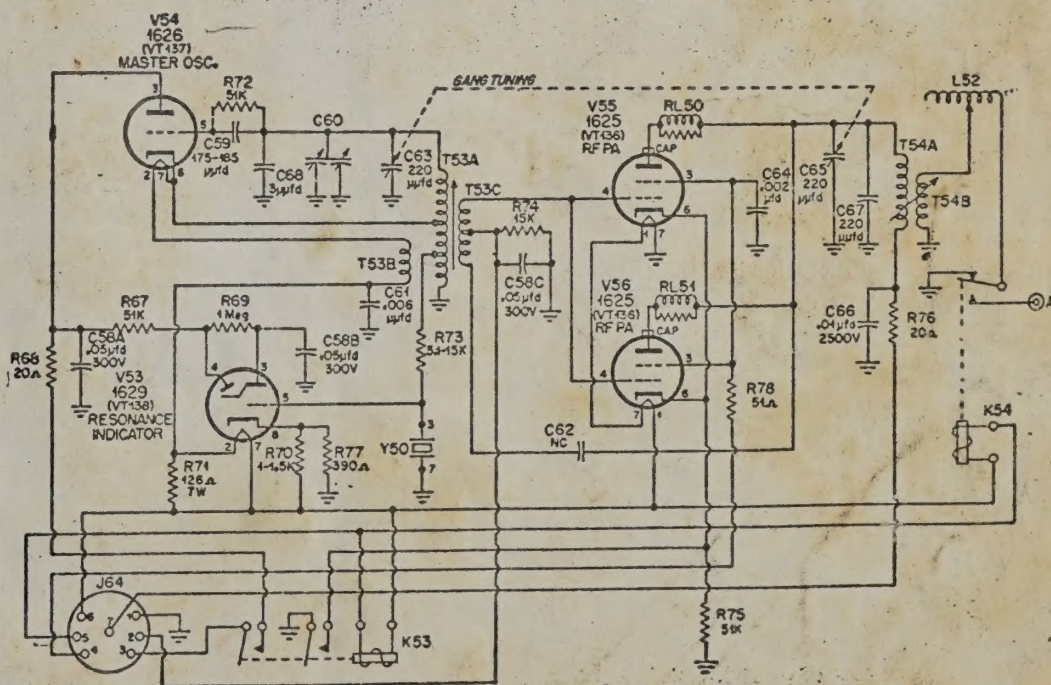

V22 - 5A2

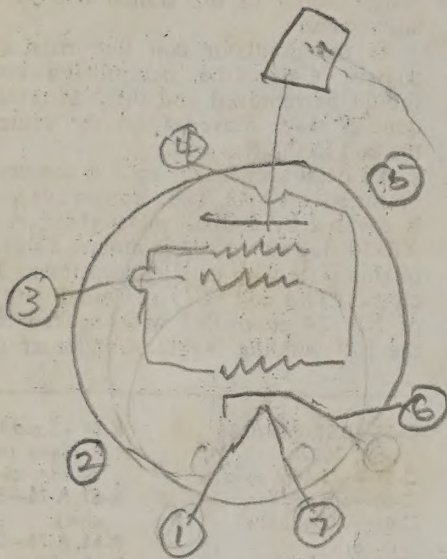

calibration will be correct if 1.0 Mc. is mentally added to the dial reading.

Plate and screen voltage should be applied to the p-a stage. The transmitter should be tuned to 7.2 Mc. and loaded to the antenna. The p-a padding condenser C-67 should be resonated for minimum plate current and then locked. C-65 should always be re-resonated whenever there is a major change in antenna loading or coupling.

Transmitter Conversion for 20, 15 and 10 Meters

The conversion of the 4.0-5.3 Mc. transmitter for high frequency use is based upon retaining single dial control and the use of one doubler stage.

The space left by the removal of the electron eye tube and the calibrating crystal may be used for a 6AG7 doubler and a slug tuned coil. The basic circuit for 20, 15 and 10 meters is shown in Figure 22.

The basic filament and socket modifications as described for the low frequency units should be completed. For 20 and 15 meters, the 6J5 oscillator must work on the 7-Mc. band, using the existing dial calibration lines, with new figures. The main winding of the oscillator coil should be reduced to 12 turns, by removing

turns from the *top* of the coil. The oscillator tuning condenser, C-63, should have all but two rotor plates removed. One of the remaining plates should be the slotted one for tracking adjustment.


At the oscillator coil terminals under the chassis, C-62 (the neutralizing condenser) should be removed and the bias return of the doubler stage moved from the center tap of the coil to the free end.

An octal socket is placed in the crystal calibrator socket hole. The electron eye socket hole is covered by a small metal plate. A National XR-50 slug tuned coil is mounted in the center of this plate with its slug adjustment above the chassis. This coil (L1) is wound with 10 turns of No. 24 enamelled wire, spaced to occupy the full winding length. Condenser C16 con-

C-58—0.05/0.05/0.05
μfd., 300v.
C-59—175-185 μfd.
C-60—air padder.
C-61—0.006 μfd.,
mica.
C-62—neutralizing
condenser.
C-63, C-65, C-67—
220 μfd.
C-64—0.002 μfd.,
1000v.
C-66—0.01 μfd.,
2500v., mica.
C-68—3.0 μfd., 750
p.p.m.
K-53—D.p.s.t. relay,
300-ohm coil.

K-54—S.p.d.t.
antenna relay,
90-ohm coil.
R-67, R-75—51,000
ohms.
R-68, R-76—20 ohms.
R-69—1.0 megohm.
R-70—1000 to 1500
ohms.
R-71—126 ohms, 7w.
R-73—5100 to 15000
ohms.
R-74—15,000 ohms.
R-77—390 ohms.
R-78—51 ohms.
RL-50, RL-51—parasitic
suppressors on 51-ohm
resistors.

Fig. 18. This is a typical wiring schematic of the
274N series transmitters.

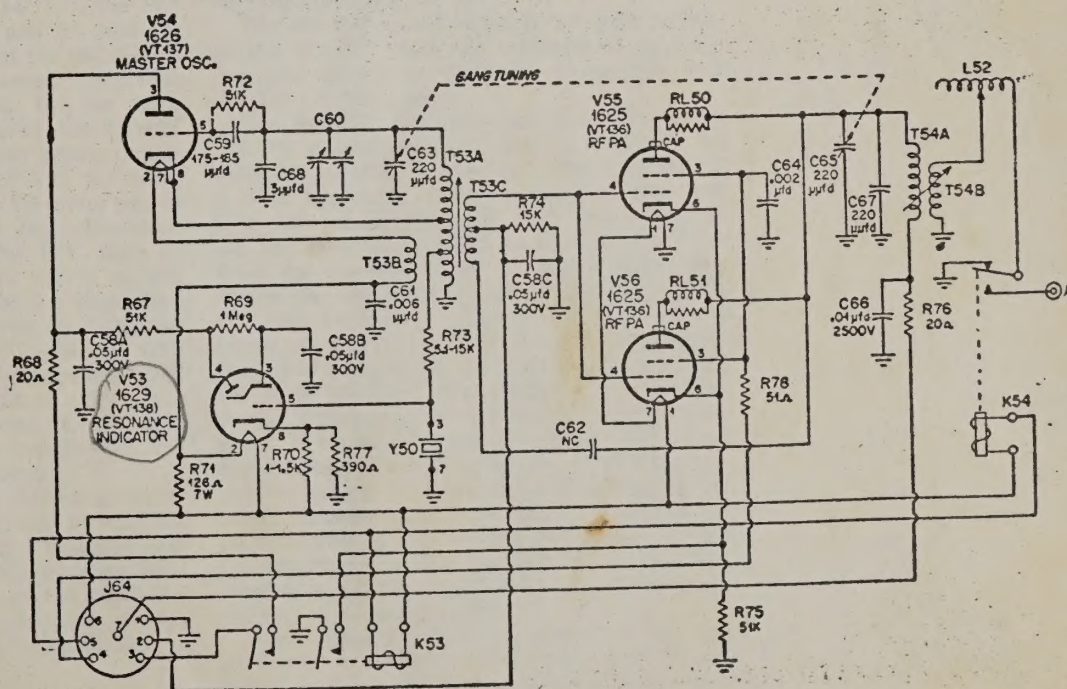

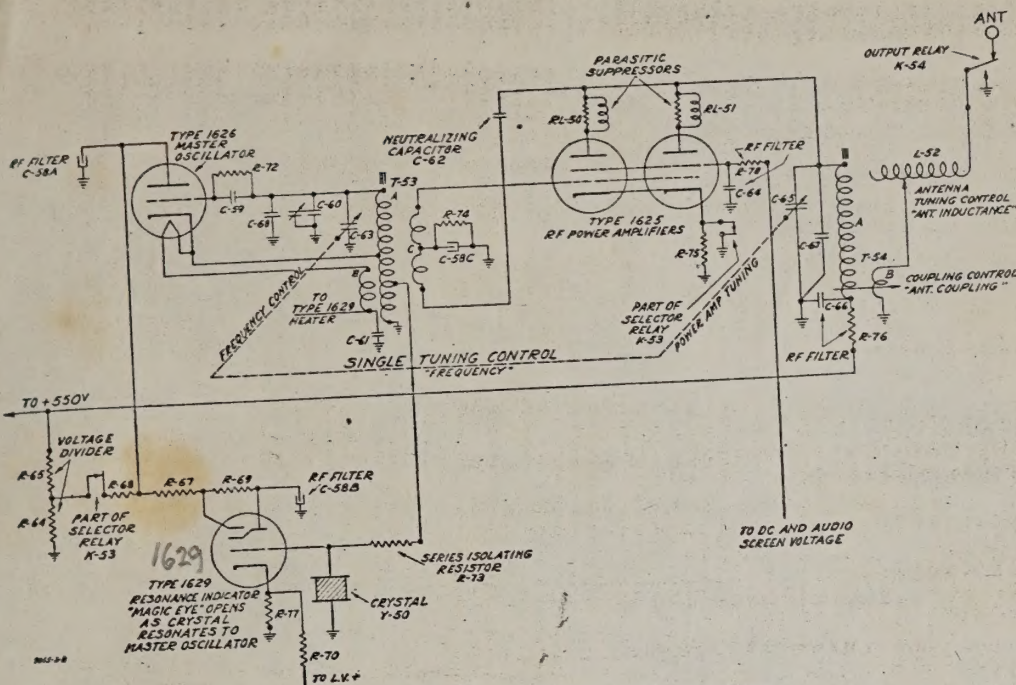


Fig. 17. Functional diagram of "Command" transmitter.

volts when this adjustment is completed. The transmitter is now ready for installation in the car.

80-Meter notes—

Either the BC-696 (3.0-4.0 Mc.) or the BC-457 (4.0-5.3 Mc.) transmitter may be used for 80-meter operation. The dial of the BC-696 is directly calibrated for the 80-meter band, but this advantage is outweighed by the high surplus price of this unit. Actually, the BC-457 is much better suited to 80-meter phone operation than is the BC-696. The BC-457 will actually cover the top 60 kc of the 80-meter phone band (3940-4000 kc) without any adjustment of the padding condensers. The L/C ratio of the BC-457 is also much more nearly correct for amplitude modulation of the p-a stage than is the BC-696. The BC-457 tunes the 80-meter phone band with almost 350 $\mu\text{fd.}$ of tank capacity, whereas the BC-696 tunes the same range with only about 150 $\mu\text{fd.}$ of tank capacity. Under heavy modulation, the BC-696 tends to splatter badly, due to insufficient "fly-wheel" effect in the p-a tank circuit.

The BC-457 may be easily shifted to cover the complete 80 meter phone band by increasing the capacity of C-67, the p-a padding condenser, and C-60, the oscillator padding condenser. The slug adjustments of the oscillator and p-a coils should not be changed, as this would alter the tracking of the transmitter.

40-Meter notes—


Either the BC-459 (7.0-9.1 Mc.) or the BC-

458 (5.3-7.0 Mc.) may be used for 40-meter operation. The L/C ratio in the p-a tank of either transmitter is satisfactory for phone operation. The conversion of the BC-459 is exactly the same as described for the BC-696 on 80-meters (Figure 20).

The BC-458 modification is the same as that of the BC-459, with the addition of retuning the tank circuits to make the transmitter tune the 7.0-7.3 Mc. range.

The BC-458 oscillator can easily reach 7.3 Mc. by decreasing the capacity of C-60, the oscillator padding condenser. However, this is a poor approach, since it degrades the high C/L ratio of the oscillator. It is best to remove the oscillator coil shield and remove 4 turns from the top end of the oscillator coil. Next, loosen the set screws holding the rotor shaft of C-60. Drill a $\frac{1}{4}$ " hole in the side of the shield can so that the shaft can be turned when the shield is replaced. Remove two plates from the rotor of C-63, the oscillator tuning condenser. Flex the plates gently with a long-nosed pliers. If too much force is applied to the condenser, the rotor will jump out of its bearings, and the minute ball bearings will fall out of the joint. Remove two rotor plates in the same fashion from C-65, the p-a tuning condenser. Loosen the rotor lock on C-67, the p-a padding condenser. Finally, remove four turns from the top of the p-a coil, T-54A.

Plate voltage should be applied to the 6J5 oscillator, and C-60 and the slug of T-53 adjusted until 7.0 Mc. falls at 6.0 Mc. on the tuning dial, and 7.3 Mc. falls at 6.3 Mc. Thus the

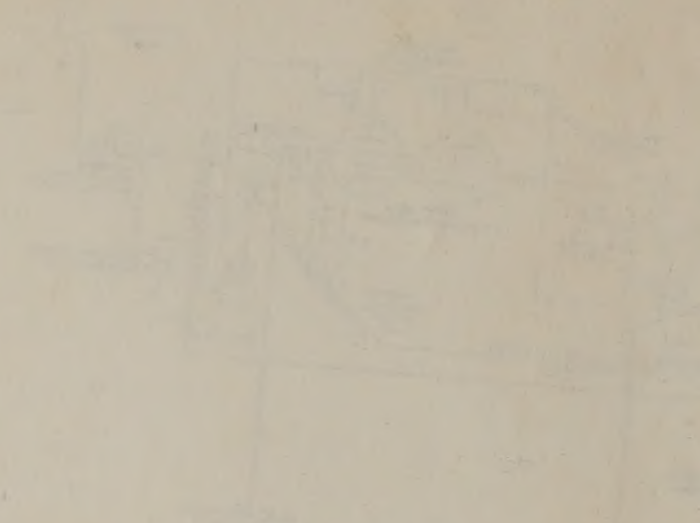

[The following text is extremely faint and largely illegible due to fading and bleed-through from the reverse side of the page. It appears to be a handwritten letter or document.]


Dear Sir,

I have the honor to acknowledge the receipt of your letter of the 10th inst. and in reply to inform you that the same has been forwarded to the proper authorities for their consideration.

I am, Sir, very respectfully,
Your obedient servant,
[Signature]

\$2.00

Conversion Diagrams

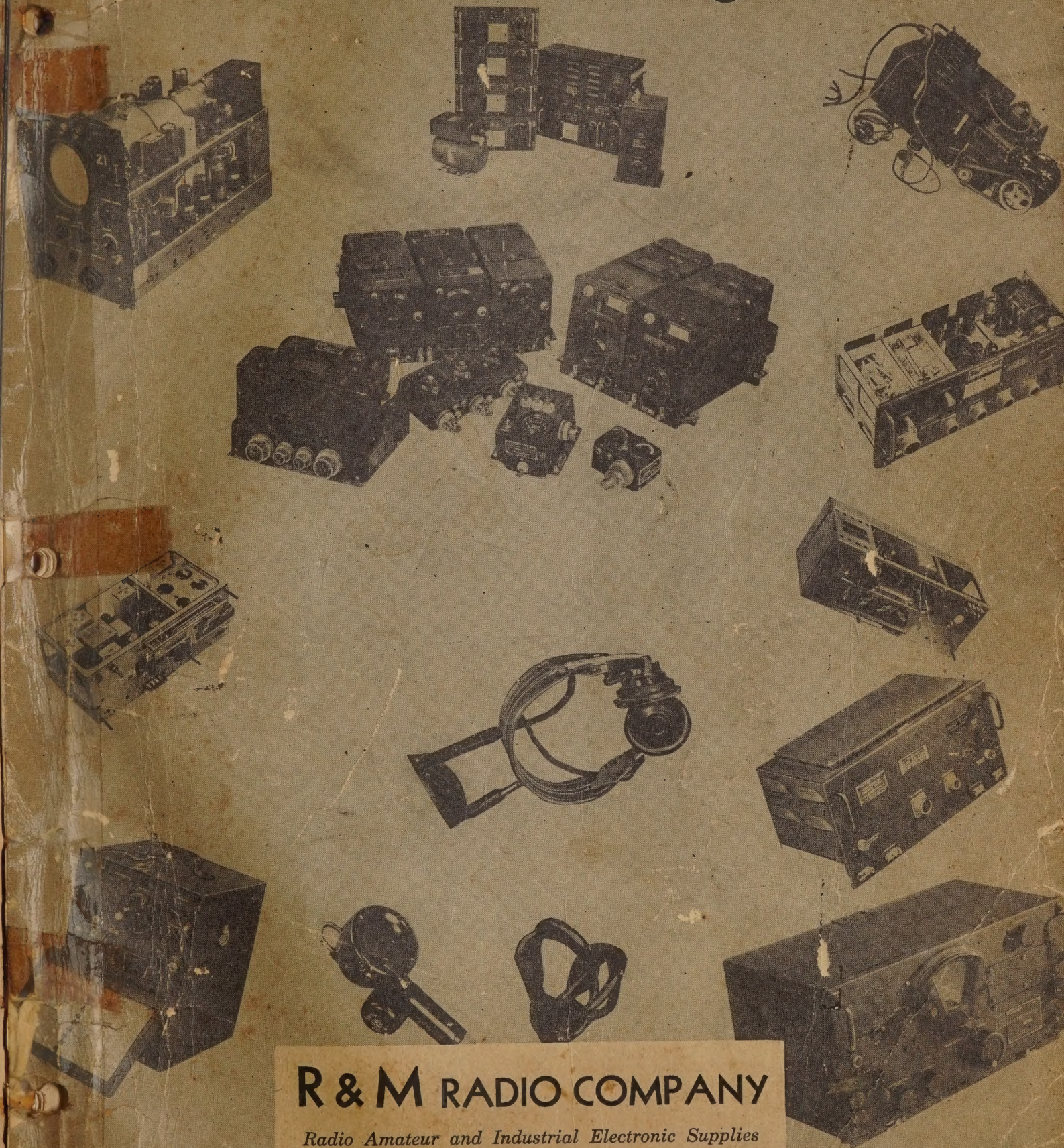

R & M RADIO COMPANY

Radio Amateur and Industrial Electronic Supplies

1426 N. Quincy St.

Arlington, Virginia

INTRODUCTION

The R & M Radio Co. since its inception has been deluged with requests for schematic diagrams covering various conversions of war surplus equipment and in view of the many requests, R & M put their engineers to work - hence this book.

It would be impossible for anyone to cover all phases of conversions and modifications possible. However, the basic ones are covered and being "Hams" at heart ourselves, we know that most Hams will go so far on any conversion or modification and then get ideas of their own and come up with something different and probably better.

Here is a good start and we are open to suggestions; and request your comments or questions.

R & M Radio Co.

The Editor

Newest conversion book—complete
with schematic diagrams, instructions, and discussion—covers all
these war surplus sets:

DIAGRAMS AND CONVERSION DATA ON . . .

- BC-348
- BC-375
- SCR-522
- SCR-274
- SCR-274—10
meter mobile

ALSO DIAGRAMS COVERING . . .

- BC-221 Freq.
meter
- ART-13 Collins
transmitter
- APN-1
- SCR-718
- APN-4

SCR-274-N

The SCR-274-N Command Set though originally designed to operate from a 27 VDC power source, can, with a new power supply, become one of the most useful pieces of gear to be found in the ham shack. For instance; the transmitters perform admirably as V.F.O.-Driver units for high power final RF amplifiers, or, by themselves as small, lightweight 50 watt transmitters. Pursuing the former thought, the SCR-274-N combined with the BC-375-E will provide the Ham with a high powered transmitter with VFO Driver unit and the 274-N receivers complete his station; further, the modulator unit has the audio driver stage necessary to put the wallop needed into the BC-375-E audio circuit and will make those big bottles of the BC-375-E get up and perform in a manner of which they are capable.

The receivers are superhets and due to the fine workmanship and parts in them will stand a lot of abuse. They are designed to operate with a wide variety of conditions and may be powered by vibrator, 110 AC-DC, dry cells or most any kind of power at hand. By rewiring the filament circuits for six volts and supplying plate power from a small vibropack no better portable communication receiver set would be desired.

Figure 1—Gives the necessary rack FT-220 wiring changes for the use of the receivers and suggests a simple power supply which may be built up on the rack itself.

Figure 2—Shows connections to be made in changing adaptor FT-230 to FT-260.

Figure 3—Advances one of the many ways the modulator may be converted to use in conjunction with audio and RF driving power necessary to develop the sock of which the BC-375-E is capable.

Figure 4—Is practical wiring diagram of the modulator with unused parts marked.

Figure 5—Shows transmitter filament wiring changes to operate with 12 vac filament power.

Figure 6—Is original overall schematic of modulator-transmitter.

Figure 7—Original receiver schematic.

RECEIVERS

When the 274-N receivers are used with an AC supply it is not necessary to make any changes in the receiver wiring provided the filament voltage supplied is 24 volts AC or DC. We considered the question and decided it was much simpler to dig up a 24 volt supply than to change the filament wiring of three receivers. Casting about the junk box we found a 6 volt center tapped filament transformer and decided it would make a nice auto transformer if we had 12 volts to put across one half of it. This could be had if we put the two filament windings of our power transmitter in series. We did this and we had our 24 volts. How it is done is shown in **Figure 1 274-N**. Next thoughts were for a regular step up auto transformer. We remember of by gone years when six volt tubes were plentiful but most transformers were equipped with 2½ volt filament windings. It was a neat trick then to take the core from an audio transformer and wind up another bobbin for it to step up 2½ volts to 6.3. This time we had a core of fair cross section so counting five turns per volt we put on 120 turns and took off a tap at 30 turns. With the power transformers 6.3 across the bottom and middle tap we got a nice 25 across the two outside terminals. This is also shown in **Figure 1**.

RECEIVER LOCAL CONTROL

The SCR-274-N Receivers BC-453-454-455 were designed for both remote and local control, but most are found

equipped for remote control only. For local control and adaptor with on-off switch, CW or MCW, and volume control resistor incorporated with it are used. (These adaptors, known as FT-260-A are practically unobtainable). The adaptor fits into the front of the receiver panel and is held in position by four small screws. For remote control, adaptor FT-230 is used. This is only a plug with one connection on it and has no controls on its face. It may be used to make an adaptor similar to the FT-260. Loosen the four screws holding FT-230 and by pulling out the knob in the center of its panel, it will come out. Remove the two small screws holding the cover over the plug and slip off the cover. You will find the eight prong plug supported by two aluminum shafts which are swaged to the cover. Remove these shafts for they will be in the way of the controls, also remove the knob from the front of the adaptor. Take the back and control knobs off remote control BC-450 and take out the receiver on-off switch and radio control. These may now be mounted on the FT-230 panel and connected to the socket plug from this unit. Connections are shown in **Figure 2**. Use leads that are a couple inches longer than necessary to reach from the receiver panel to the plug prongs to enable us to push the socket wafer on the prongs before screwing the FT-230 panel on the receiver side.

THE MODULATOR

Modulator BC-456 contains the dynamotor and its relays, the audio system and voltage divider networks for the SCR-274-N transmitters. The dynamotor is very nicely designed and built and puts out an astounding amount of soup for its size but we shall forget it in this writing and assume it will never be used. The audio circuit is a beam type transmitting tube, 1625, which has the carbon mike circuit directly to its grid and sans any amplifier stages ahead of it. This tube is used to suppressor grid modulate the pair of 1625's in the transmitter. There is the usual resistor-capacitor net work of voltage divider circuits and a VR-150 gas tube to stabilize and drop the screen voltage when the 274-N is on "voice".

Many service or war time audio circuits have only one tube doing service as an audio system. The explanation for this is simple. The carbon mike used carried more current than half the tubes could; 60 and sometimes 75 miles at 24 or less volts. With this sort of zip the mike, voltage stages are not necessary but we are dealing with civilian mikes that have not that sort of output so we must add a stage of audio in our modulator. This easy for there is a tube labeled V-50 in **Figure 3, 274-N**. This is equivalent of a 6-J-5. To some the idea of starting the infinite trickle of voltage from a crystal mike to a triode and then putting it to a high gain beam tube may sound a little backwards but it works out very nicely. First thing to do is start removing a few odds and ends that won't be necessary anymore. Refer to the Modulator Practical wiring diagram **Figure 4** to locate these parts for we have drawn diagonal lines through those not needed.

Namely, these will be three relays K-50, K-51 and K-52 (two of these are on top, under the tube cover), RF Choke L-150, mike transformer T-51, tone oscillator T-50.

Snip all the leads from J-54 for we won't need that plug at all and it will help clear the way under the chassis.

Where T-50 and T-51 come out there will now be room for mike jacks, gain controls and switches.

Now the **Figure 3** and **Figure 4** we can re-wire the modulator and take off from there to the few changes in the transmitters.

TRANSMITTER

The 274-N transmitters, when used as VFO, require very little change in wiring and this is in the filament circuits only. Figure 5 gives these changes. These transmitters are so arranged that the crystal is not an integral part of the oscillator but is used instead to check the accuracy of same. For service use it was sufficient to check on one dial point only and assume the rest of the range correct enough. This would hardly do for civilian use but may be improved on by using crystals to check and confine the settings to proper bounds, for instance, two crystals may be used to mark the higher and lower band edges and thus assure the user of not trespassing on adjacent spectrums, or the user may wish a spot frequency and plug in the correct crystal, tune to resonance as usual just as though the circuit functioned as a crystal oscillator. The tuning procedure is simple to the extreme for it is only necessary to lift the rear tube cover, insert the crystal, leave the cover opened at an angle that will enable the ray tube glow to be seen in the little mirror riveted to the top, and tune the transmitter until the shadow angle of the tube is greatest. As the oscillator and power amplifier are ganged together this is all the tuning necessary other than to observe if tuning the antenna loading circuit has any effect on the frequency. Care must be taken in loading as is the case in all VFO's.

Dial calibration may be lined up to the proper frequency by inserting a small insulated screw driver through the hole in the top back portion of the transmitter that is covered by a snap slide. This will reach a small trimmer condenser in the oscillator circuit.

For ease in tuning to any crystal it is suggested that a small meter be put either in the cathode or plate circuit of the target tube and mounted on the transmitter where it may be easily seen. This will make any appreciable drift immediately apparent, however, the variation is small and some circuit modification base. This may necessitate an adaptor to allow the crystal holders usually found in the shack to be used in the set although there are several types on the market that can be plugged into an octal socket.

The final amplifier is coupled to the antenna loading circuit by a variable coupling loop that is fastened to a shaft within the final plate tank if it is desired, this loop may be utilized to connect to a low impedance line and well serve to carry the output to an antenna or power amplifier.

The loading coil may be used to resonate a random length wire antenna or may be tuned by the addition of an other condenser and coupled directly to the grid of a following amplifier.

Still another thought is to remove the antenna tuner coil and substitute the usual plug-in coil and condenser. The later would probably be the most efficient if the user contemplated doubling in the following stage for much loss would result in the shorted turns of the antenna coil.

When the transmitter is to be used without the following stage it would be handy to install a co-ax connector in the panel face to enable the user to couple to low impedance feeders such as center fed antennas sometimes use.

Figure 5 gives the necessary detail for wiring changes for 274-N transmitters for operation from 12 volt AC filament supplies.

TUNING BY CALIBRATING CRYSTAL

In order to test the theory that more than one crystal

could be used in parallel in place of the one supplied. It was decided to put six crystal in the place of the one.

For testing purposes an adaptor was made up from a thin bakelite strip $1\frac{1}{4}$ " wide. This was mounted vertically from the center of an octal tube base. Tube prong jacks removed from six prong tube sockets were mounted on the strip to allow three crystals to be mounted on each side. The six crystals were ganged in parallel in place of the single original rock and were separated in frequency by 10 kc. In the set-up there was found no interaction, the adjacent channels were easy to locate by the target tube shadow. By careful tuning, the frequency was plus or minus 100 cps, the crystal frequency, with ease. By tuning within the range of the target tube shadow movement the frequency could be varied 500 to 2,000 CPS depending on the transmitter used. The same condition existed for any frequency covered by the transmitter dial markings. The dials are marked off in 10 kc steps and are driven by a reduction gear from the small knob in lower right hand of the panel. By removing the knob and fixing a small disc to it which had been marked off in 20 divisions we have a vernier control. One-fifth revolution of the vernier covers about 10 kc on the main dial of the 7-9 mc transmitter and one-third revolution on the 3-4 mc.

A Word About The Stability Of SCR-274-N Transmitters

When modulated by the original screen grid method the frequency is apt to swing a good many hundred cycles if the final is too heavily loaded. Completely removing the load from the final and replacing it will cause a frequency drift of roughly 5,000 cycles.

For perfect operation a VR tube, stabilized oscillator plate voltage or some similar arrangement would be necessary. The original circuit has a VR tube in the final amplifier screen grid circuit which is used to drop and stabilize the screen voltage of the final to allow modulation via that grid. As the oscillator operates at 250 volts plate and the small amount of frequency variation noticed was caused by voltage drop along the divider resistor network of the modulator, perhaps it would be easier to supply the oscillator plate voltage from a nearby receiver or separate small supply. As it stands the variation is not objectionable if properly handled.

In the transmitter schematic there will be noticed R-77 and R-70 of the resonance indicator which form the cathode resistors of this tube. With these two resistors for forming the target bias the indication is small at the resonance peak and difficult to see in a bright light. R-70 originally placed a positive voltage upon the cathode from the 27 VDC to provide constant biasing of the tube. With AC on the filaments it should be removed and as R-70 is the right value should be put in place of the cathode resistor R-77. This will greatly improve the target shadow swing and facilitate tuning.

One method tried works nicely for controlling the transmitters. The relays were removed and rewound by filling the bobbins with 24DCC wire. This allowed them to be operated by a small three volt battery pack.


For mobile use many of the gang and also several branches of the government service have used the familiar PE-103 dynamotor to power the 274-N transmitter and modulator. PE-103 has a 12 or 6 volt input and 500 volts at 160 mills. By feeding 6 volts into the dynamotor, 12 volts and 500 may be taken out. By re-wiring the filament circuits and the relays for 12 volts plus a lower value of resistance in the mike supply circuit the equipment may be used exactly as it was in the aircraft.

For crystal control a clever scheme has come to our

attention. In the original circuit the oscillator grid leak and capacitor are in series with the grid. By changing the grid leak position so that it will go from grid to ground and placing the grid capacitor in a crystal holder, crystals may be placed in series with the grid circuit. This in effect forms a crystal filter and will not permit the circuit to function at any frequency but that of the crystal. By removing the crystal and replacing the condenser the circuit is again a VFO.




FIGURE 1-274N

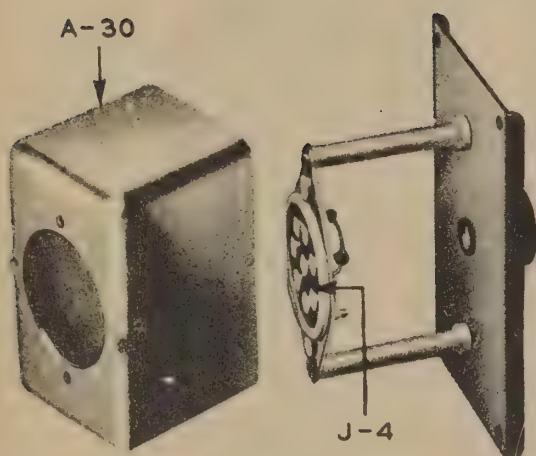

COVER REMOVED

SIDE VIEW

ADAPTER FT-230-A

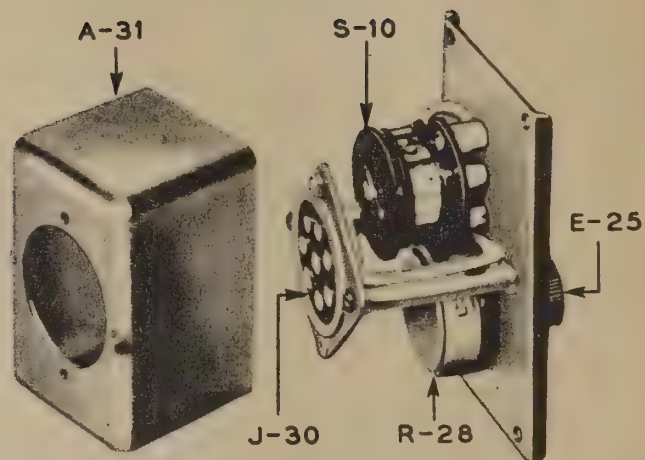

COVER REMOVED

SIDE VIEW

ADAPTER FT-260-A

FIG. 2-274



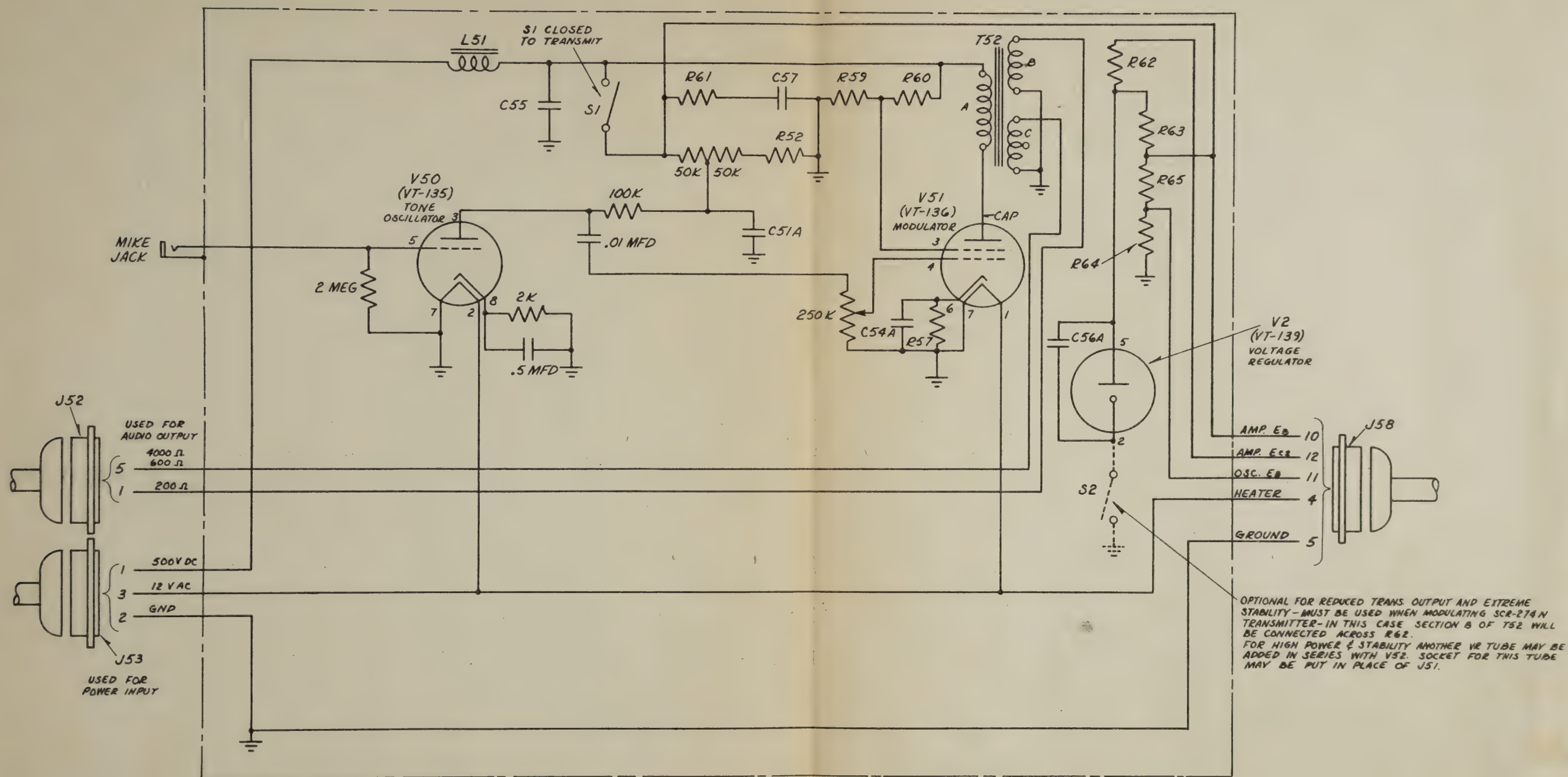
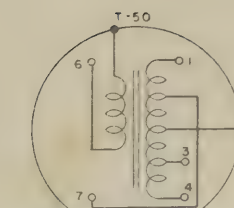



Fig 3-274-N

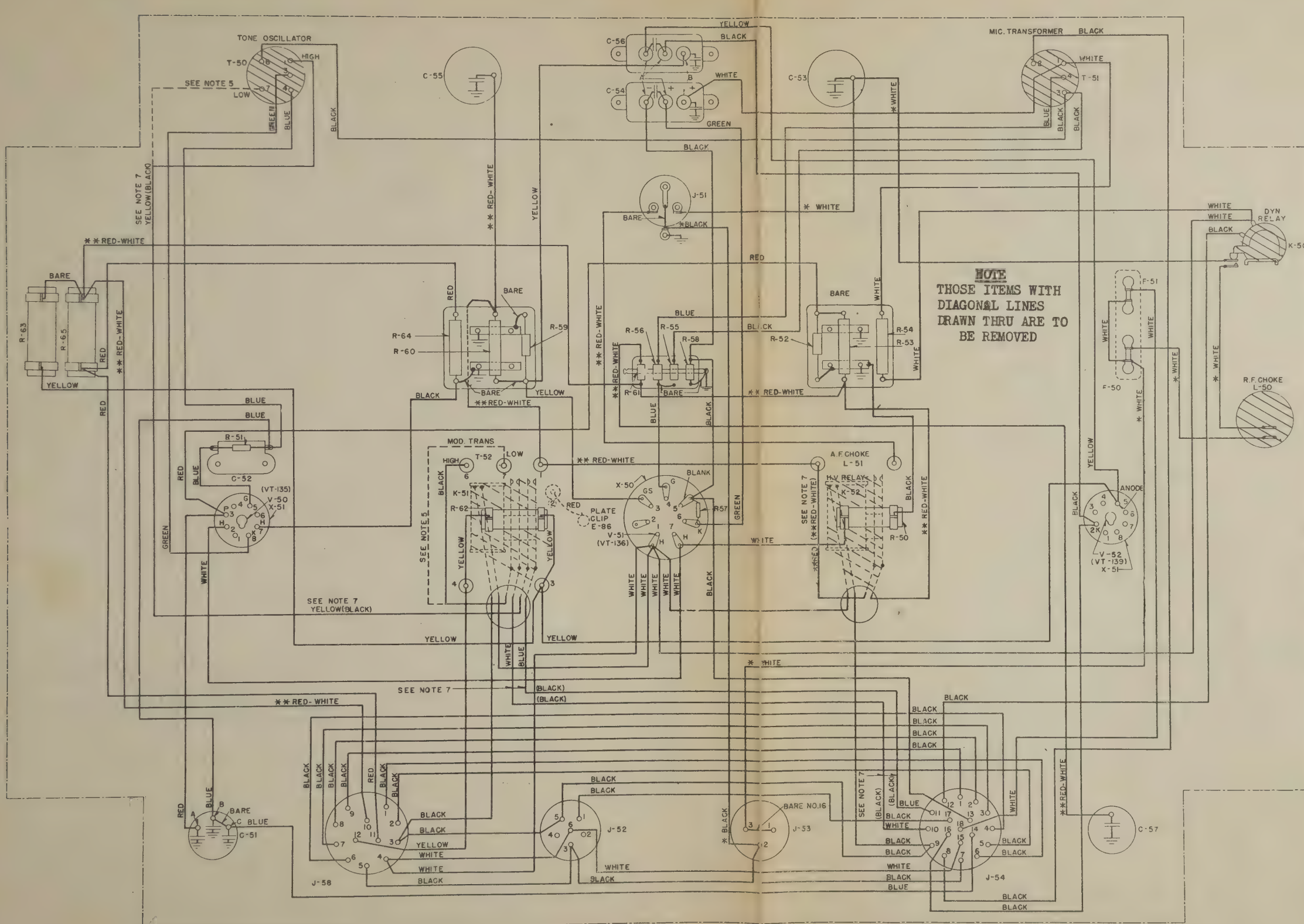

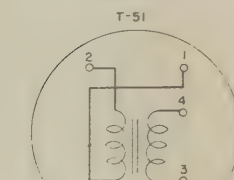TONE OSCILLATOR TRANSFORMER.
TAP 7 IS PROVIDED IN BC-456-B ONLY
SEE NOTE 5





MICROPHONE TRANSFORMER

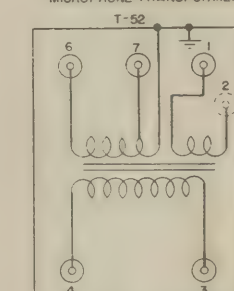


MODULATION TRANSFORMER
TAP 7 PROVIDED IN BC-456-B ONLY
SEE NOTE 5

- NOTES:
1. ALL WIRES MARKED (*) TO BE NO.18 STRANDED COPPER.
 2. ALL WIRES MARKED (**) TO BE NO.22 SINGLE CONDUCTOR TINNED COPPER, HEAVY INSULATION.
 3. ALL BARE WIRES ARE NO.22 TINNED COPPER EXCEPT AS NOTED.
 4. ALL OTHER INSULATED WIRES TO BE NO.22 SOLID COPPER.
 5. MODULATOR UNIT BC-456-B IS EQUIPPED WITH TRANSFORMERS DESIGNATED "MOD. TRANS." AND "TONE OSCILLATOR" EACH OF WHICH INCLUDES TAP 7 FOR MAKING A LOW IMPEDANCE HEADSET CONNECTION. BC-456-B MODULATOR UNITS AS SUPPLIED ARE WIRED FOR THE HIGH IMPEDANCE CONNECTION. CHANGES IN THE WIRING FROM TAP 1 TO TAP 7 ON TONE OSCILLATOR AND FROM TAP 6 TO TAP 7 ON MOD. TRANS. AS INDICATED ARE REQUIRED FOR THE LOW IMPEDANCE HEADSET CONNECTION.
 6. TERMINAL NUMBERS AND LETTERS AT TUBE SOCKETS AND MOD. TRANS. ARE FOR REFERENCE PURPOSES AND DO NOT APPEAR ON APPARATUS.
 7. WIRE COLORS SHOWN IN PARENTHESIS ARE USED IN MODULATOR UNITS BC-456-A AND IN EARLY PRODUCTION UNITS BC-456-B.


FIGURE 4-274N

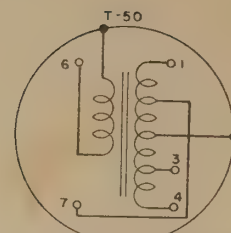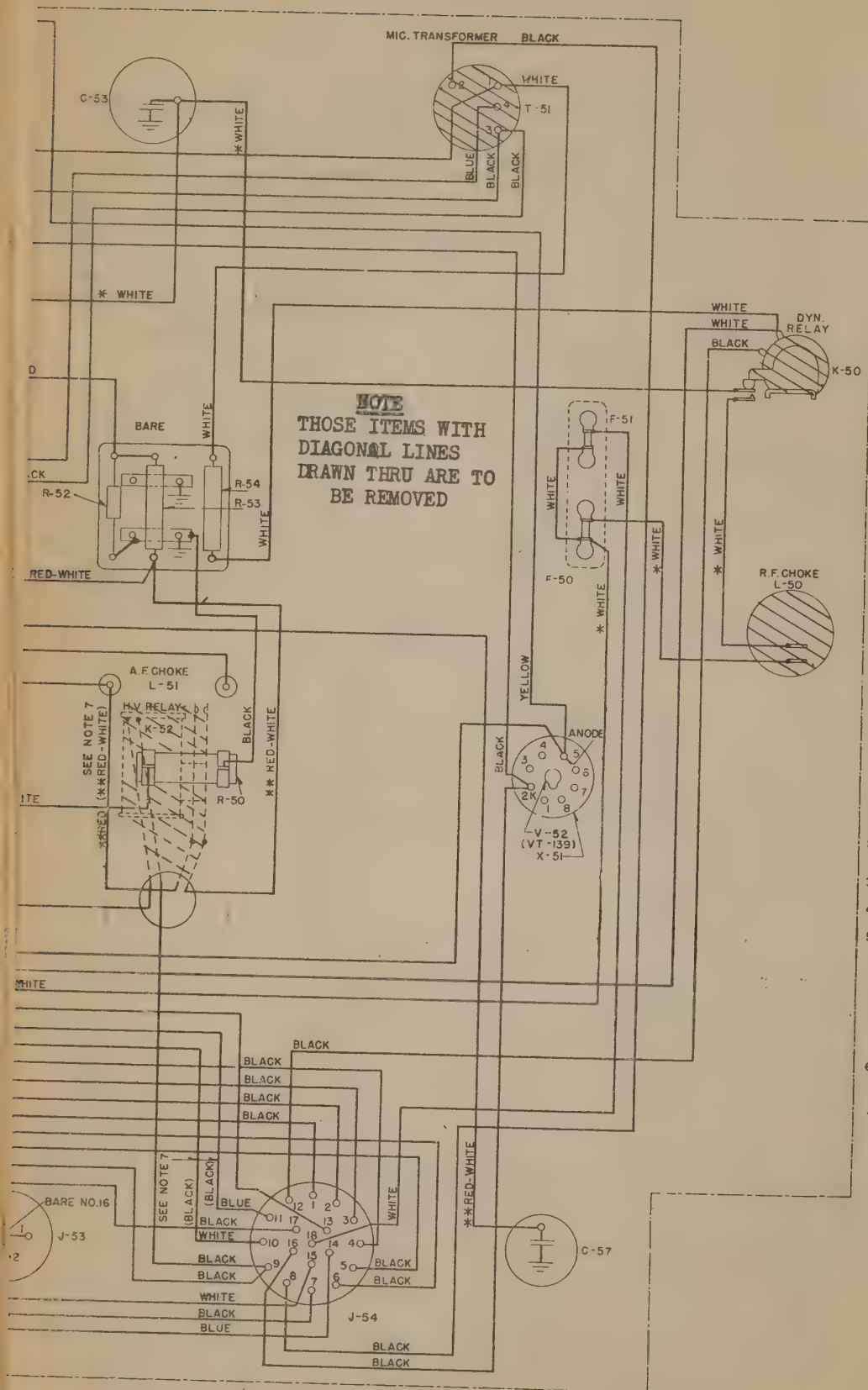

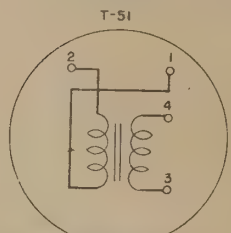1. TONE OSCILLATOR TRANSFORMER.
TAP 7 IS PROVIDED IN BC-456-B ONLY
SEE NOTE 5



2. MICROPHONE TRANSFORMER

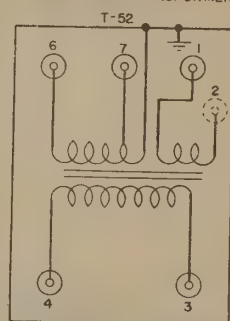


3. MODULATION TRANSFORMER
TAP 7 PROVIDED IN BC-456-B ONLY
SEE NOTE 5

NOTES:

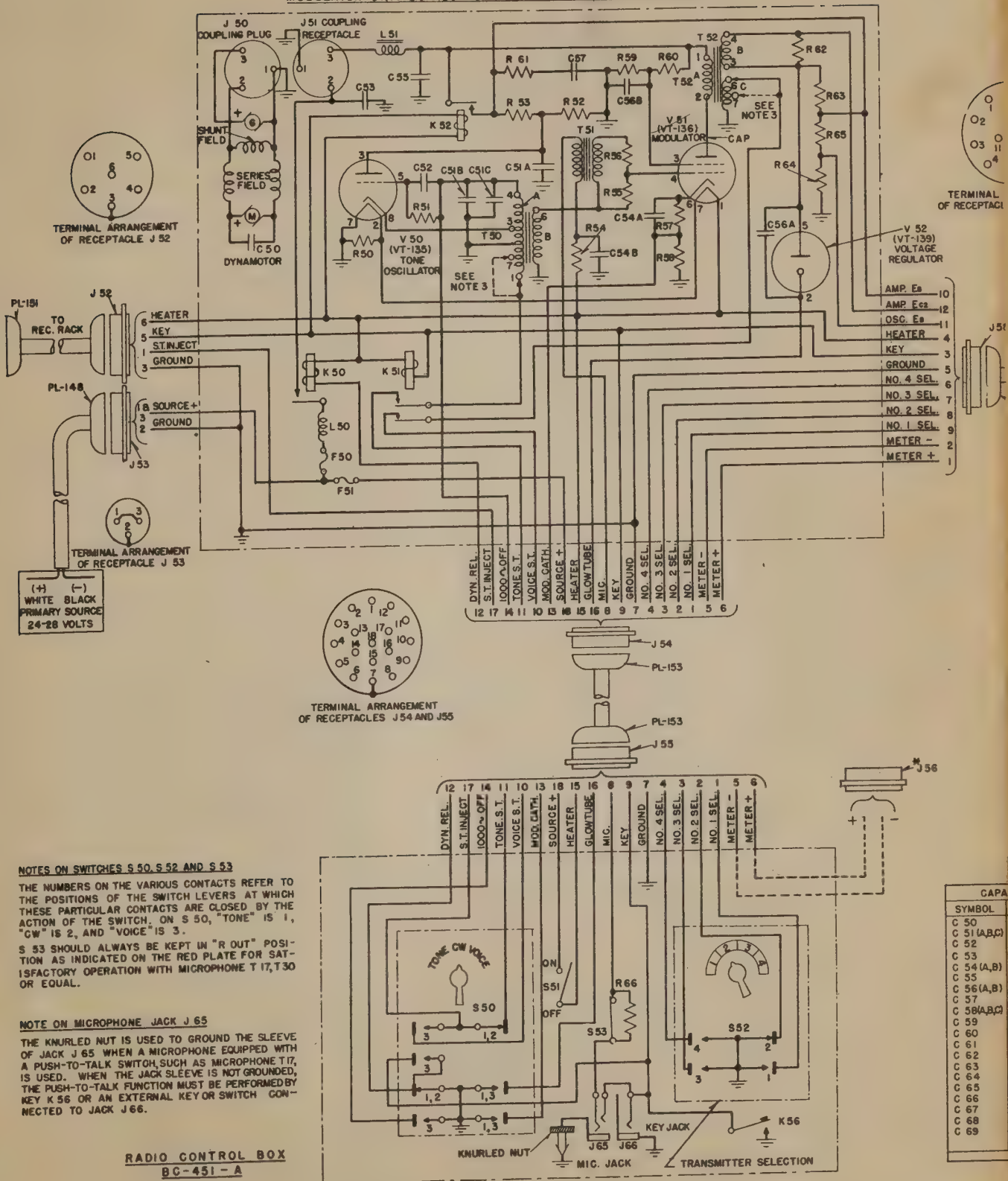1. ALL WIRES MARKED (*) TO BE NO.18 STRANDED COPPER.
2. ALL WIRES MARKED (**) TO BE NO.22 SINGLE CONDUCTOR TINNED COPPER, HEAVY INSULATION.
3. ALL BARE WIRES ARE NO.22 TINNED COPPER EXCEPT AS NOTED.
4. ALL OTHER INSULATED WIRES TO BE NO.22 SOLID COPPER.
5. MODULATOR UNIT BC-456-B IS EQUIPPED WITH TRANSFORMERS DESIGNATED "MOD. TRANS." AND "TONE OSCILLATOR" EACH OF WHICH INCLUDES TAP 7 FOR MAKING A LOW IMPEDANCE HEADSET CONNECTION. BC-456-B MODULATOR UNITS AS SUPPLIED ARE WIRED FOR THE HIGH IMPEDANCE CONNECTION. CHANGES IN THE WIRING FROM TAP 1 TO TAP 7 ON TONE OSCILLATOR AND FROM TAP 6 TO TAP 7 ON MOD. TRANS. AS INDICATED ARE REQUIRED FOR THE LOW IMPEDANCE HEADSET CONNECTION.
6. TERMINAL NUMBERS AND LETTERS AT TUBE SOCKETS AND MOD. TRANS. ARE FOR REFERENCE PURPOSES AND DO NOT APPEAR ON APPARATUS.
7. WIRE COLORS SHOWN IN PARENTHESIS ARE USED IN MODULATOR UNITS BC-456-A AND IN EARLY PRODUCTION UNITS BC-456-B.

MODULATOR UNIT BC-456-A(OR-B) WITH DYNAMOTOR DM-33-A



NOTES ON SWITCHES S 50, S 52 AND S 53

THE NUMBERS ON THE VARIOUS CONTACTS REFER TO THE POSITIONS OF THE SWITCH LEVERS AT WHICH THESE PARTICULAR CONTACTS ARE CLOSED BY THE ACTION OF THE SWITCH. ON S 50, "TONE" IS 1, "CW" IS 2, AND "VOICE" IS 3.



S 53 SHOULD ALWAYS BE KEPT IN "R OUT" POSITION AS INDICATED ON THE RED PLATE FOR SATISFACTORY OPERATION WITH MICROPHONE T 17, T 30 OR EQUAL.

NOTE ON MICROPHONE JACK J 65


THE KNURLED NUT IS USED TO GROUND THE SLEEVE OF JACK J 65 WHEN A MICROPHONE EQUIPPED WITH A PUSH-TO-TALK SWITCH, SUCH AS MICROPHONE T 17, IS USED. WHEN THE JACK SLEEVE IS NOT GROUNDED, THE PUSH-TO-TALK FUNCTION MUST BE PERFORMED BY KEY K 56 OR AN EXTERNAL KEY OR SWITCH CONNECTED TO JACK J 66.

RADIO CONTROL BOX
BC-451-A


FIGURE 6-

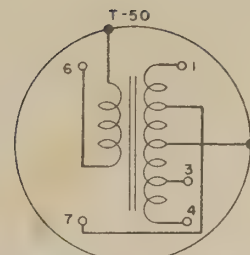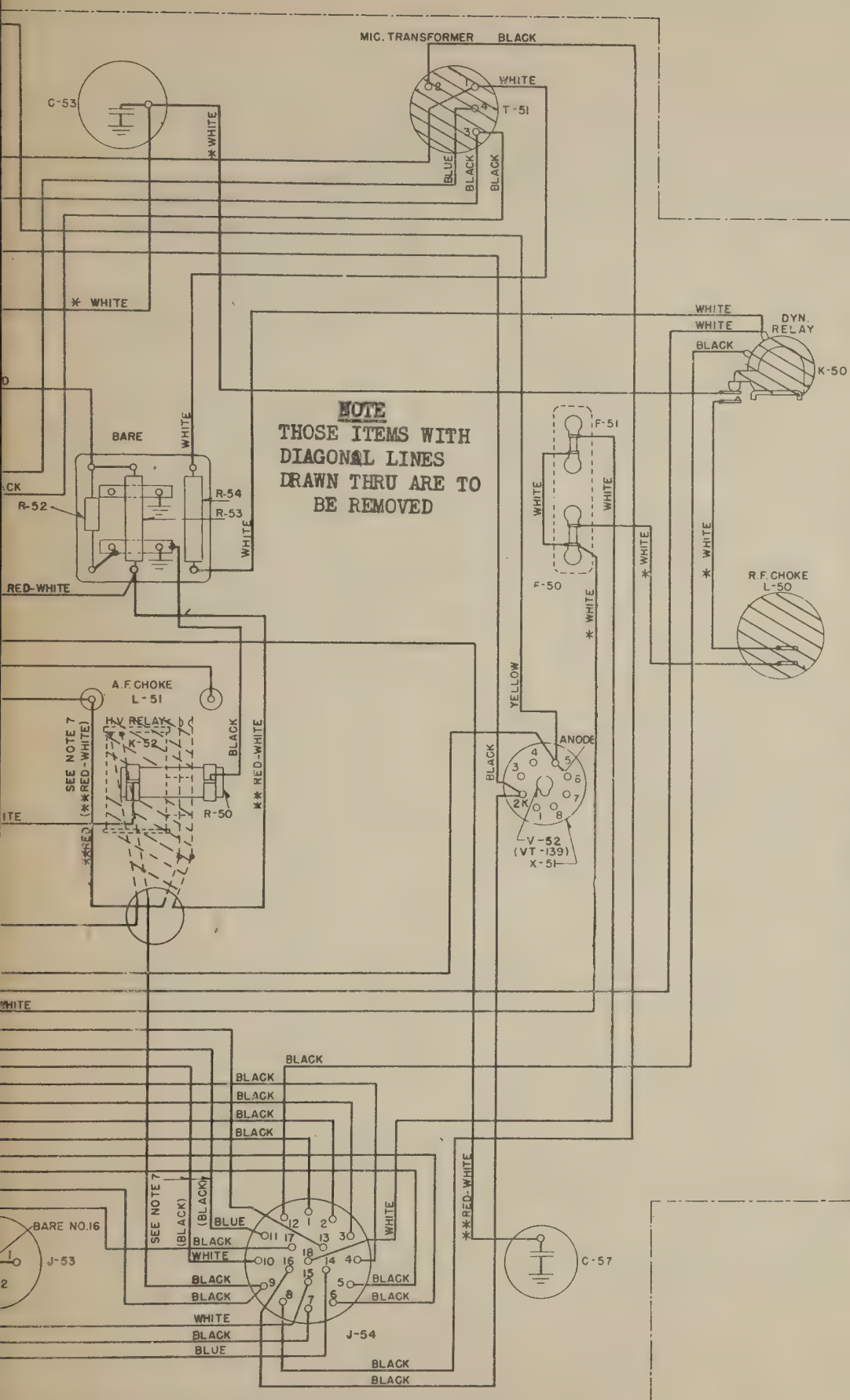

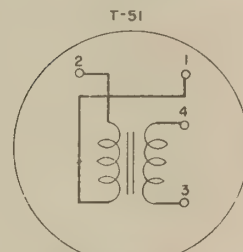TONE OSCILLATOR TRANSFORMER.
TAP 7 IS PROVIDED IN BC-456-B ONLY
SEE NOTE 5



MICROPHONE TRANSFORMER

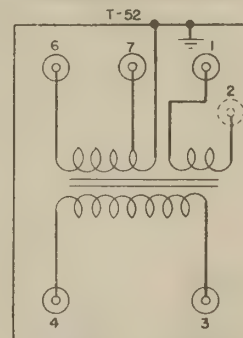


MODULATION TRANSFORMER
TAP 7 PROVIDED IN BC-456-B ONLY
SEE NOTE 5

NOTES:

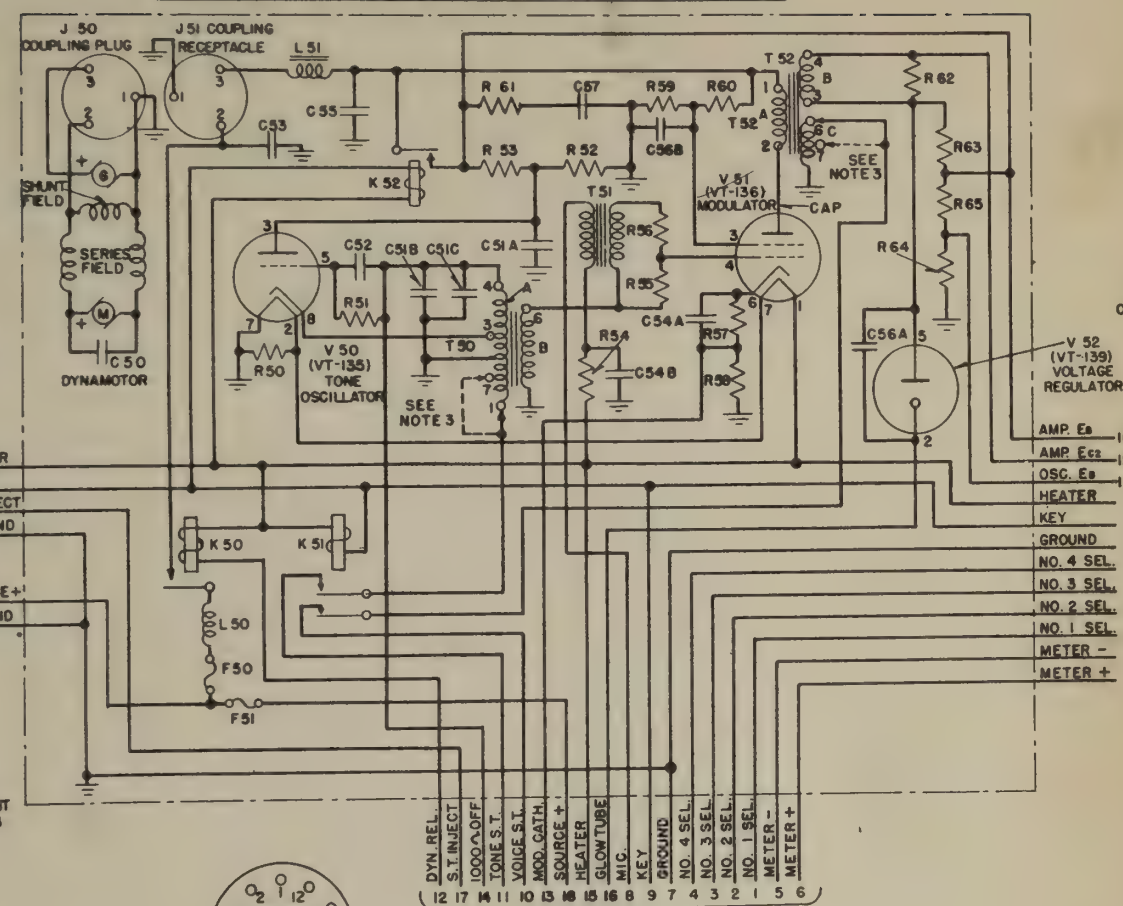1. ALL WIRES MARKED (*) TO BE NO.18 STRANDED COPPER.
2. ALL WIRES MARKED (**) TO BE NO.22 SINGLE CONDUCTOR TINNED COPPER, HEAVY INSULATION.
3. ALL BARE WIRES ARE NO.22 TINNED COPPER EXCEPT AS NOTED.
4. ALL OTHER INSULATED WIRES TO BE NO.22 SOLID COPPER.
5. MODULATOR UNIT BC-456-B IS EQUIPPED WITH TRANSFORMERS DESIGNATED "MOD. TRANS." AND "TONE OSCILLATOR" EACH OF WHICH INCLUDES TAP 7 FOR MAKING A LOW IMPEDANCE HEADSET CONNECTION. BC-456-B MODULATOR UNITS AS SUPPLIED ARE WIRED FOR THE HIGH IMPEDANCE CONNECTION. CHANGES IN THE WIRING FROM TAP 1 TO TAP 7 ON TONE OSCILLATOR AND FROM TAP 6 TO TAP 7 ON MOD. TRANS. AS INDICATED ARE REQUIRED FOR THE LOW IMPEDANCE HEADSET CONNECTION.
6. TERMINAL NUMBERS AND LETTERS AT TUBE SOCKETS AND MOD. TRANS. ARE FOR REFERENCE PURPOSES AND DO NOT APPEAR ON APPARATUS.
7. WIRE COLORS SHOWN IN PARENTHESIS ARE USED IN MODULATOR UNITS BC-456-A AND IN EARLY PRODUCTION UNITS BC-456-B.

MODULATOR UNIT BC-456-A(OR-B) WITH DYNAMOTOR DM-33-A



NOTES ON SWITCHES S50, S52 AND S53


THE NUMBERS ON THE VARIOUS CONTACTS REFER TO THE POSITIONS OF THE SWITCH LEVERS AT WHICH THESE PARTICULAR CONTACTS ARE CLOSED BY THE ACTION OF THE SWITCH. ON S50, "TONE" IS 1, "CW" IS 2, AND "VOICE" IS 3.

S53 SHOULD ALWAYS BE KEPT IN "R OUT" POSITION AS INDICATED ON THE RED PLATE FOR SATISFACTORY OPERATION WITH MICROPHONE T17, T30 OR EQUAL.


NOTE ON MICROPHONE JACK J65

THE KNURLED NUT IS USED TO GROUND THE SLEEVE OF JACK J65 WHEN A MICROPHONE EQUIPPED WITH A PUSH-TO-TALK SWITCH, SUCH AS MICROPHONE T17, IS USED. WHEN THE JACK SLEEVE IS NOT GROUND, THE PUSH-TO-TALK FUNCTION MUST BE PERFORMED BY KEY K56 OR AN EXTERNAL KEY OR SWITCH CONNECTED TO JACK J66.

RADIO CONTROL BOX BC-451-A

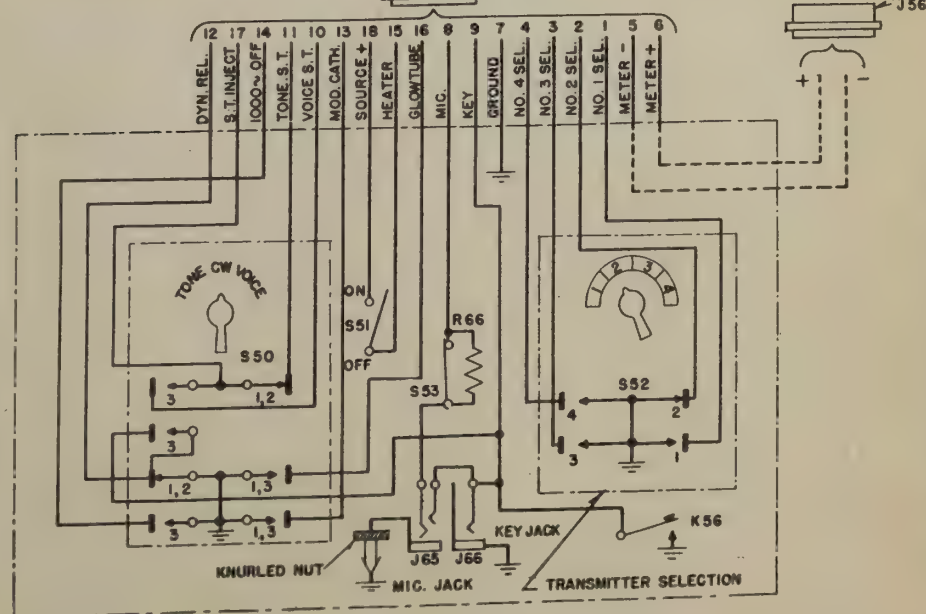

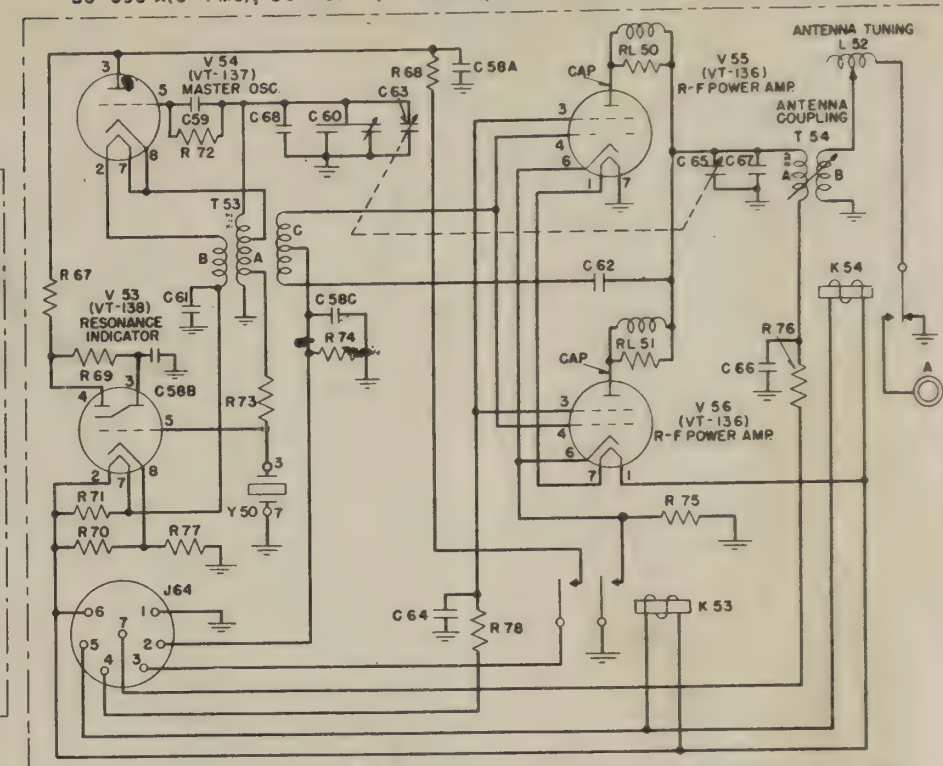TYPICAL RADIO TRANSMITTER BC-696-A(3-4 MC), BC-457-A(4-5.3 MC), BC-458-A(5.3-7 MC) OR BC-459-A(7-9.1 MC)



NOTES


- ALL RELAYS ARE SHOWN IN THE NON-ENERGIZED POSITION.
- ALL COUPLING PLUGS AND RECEPTACLES SHOWN AS VIEWED FROM THE OUTSIDE. ALL PLUGS AS VIEWED FROM THE CORDAGE END HAVE THE SAME ORIENTATION OF CONDUCTORS AS THAT SHOWN HERE FOR THEIR RESPECTIVE RECEPTACLES.
- TRANSFORMERS T50 AND T52 IN MODULATOR UNIT BC-456-B ARE PROVIDED WITH SIDETONE TAPS FOR LOW IMPEDANCE HEADSETS (70M T50 AND 7 ON T52). MODULATOR UNITS BC-456-A AND BC-456-B ARE NORMALLY FURNISHED WITH CONNECTIONS SHOWN IN SOLID LINES FOR USE WITH HIGH IMPEDANCE (8000 OHMS) HEADSETS. MODULATOR UNIT BC-456-B CAN BE CHANGED FOR USE WITH LOW IMPEDANCE (600 OHMS) HEADSETS BY SUBSTITUTING CONNECTIONS SHOWN IN DASHED LINES.
- TERMINAL NUMBERS APPEARING ON RECEPTACLES OF JACK J51 IN MODULATOR UNIT AND J64 IN TRANSMITTER AND ALL CIRCUIT SYMBOLS ARE FOR REFERENCE PURPOSES ONLY. THEY DO NOT APPEAR ON THE EQUIPMENT.
- * DISCONTINUED ON LATER EQUIPMENTS.

ANTENNA RELAY UNIT BC-442-A OR ANTENNA RELAY UNIT BC-442-AM (LESS C-69 AND BINDING POSTS "C")

CAPACITORS		INDUCTORS		RELAYS & KEYS		RESISTORS		SWITCHES		TRANSFORMERS		MISCELLANEOUS	
SYMBOL	MICROFARADS	SYMBOL	DESCRIPTION	SYMBOL	DESCRIPTION	SYMBOL	OHMS	SYMBOL	DESCRIPTION	SYMBOL	DESCRIPTION	SYMBOL	DESCRIPTION
C50	.006	L50	RF CHOKE APPR. 15 MICROHENRIES	K50	DYNAMOTOR INPUT	R50	42	S50	CHOICE OF EMISSION	T50	TOUCH OSC. MICROPHONE	TC50	THERMOCOUPLE
C51(A,B,C)	.05/.05/.05	L51	1.7 HENRIES	K51	SIDETONE, VOICE AND TONE	R51	100,000	S51	MAIN "ON-OFF"	T51	MODULATION	M50	ANT. CURRENT INDICATOR (LOCAL)
C52	.006	L52	ANT. TUNING INDUCTOR	K52	DYNAMOTOR HIGH VOLTAGE (KEYING)	R52	300,000	S52	BATTERY LINE TRANSMITTER SELECTION	T52	MASTER OSC.	Y50	CRYSTAL UNIT
C53	1.2			K53	SELECTOR	R53	91,000	S53	SHUNTS MIC. SERIES RESISTOR	T53	TRANS. OUTPUT	F50	20 AMP. FUSE
C54(A,B)	5/20.			K54	TRANSMITTER OUTPUT	R54	360	S54	METER SWITCHING	T54	ANT. CURRENT	RL50	PARASITIC SUPPRESSOR
C55	1.2			K55	ANTENNA SWITCH-ING REC. TO TRANS. BUILT-IN KEY	R55	2,000			T55		RL50	PARASITIC SUPPRESSOR
C56(A,B)	.5/5.					R56	13,000						
C57	.05					R57	390						
C58(A,B,C)	.05/.05/.05					R58	51,000						
C59	.00018					R59	30,000						
C60	MO. PADDING					R60	75,000						
C61	.006					R61	20						
C62	FIXED NEUTR.					R62	10,000						
C63	MO. TUNING					R63	20,000						
C64	PA. TUNING					R64	100,000						
C65	.01					R65	15,000						
C66	PA. PADDING					R66	510						
C67	.000003					R67	51,000						
C68	.000003					R68	20						
C69	.00005					R69	1,000,000						

FIGURE 6-274N

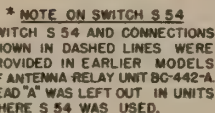BC-696-A(3-4 MC), BC-457-A(4-5.3 MC), BC-458-A(5.3-7 MC) OR BC-459-A(7-9.1 MC)



ANTENNA RELAY UNIT BC-442-AM
(LESS C-69 AND BINDING POSTS "C")

- ### NOTES
1. ALL RELAYS ARE SHOWN IN THE NON-ENERGIZED POSITION.
 2. ALL COUPLING PLUGS AND RECEPTACLES SHOWN AS VIEWED FROM THE OUTSIDE. ALL PLUGS AS VIEWED FROM THE GORAGE END HAVE THE SAME ORIENTATION OF CONDUCTORS AS THAT SHOWN HERE FOR THEIR RESPECTIVE RECEPTACLES.
 3. TRANSFORMERS T 50 AND T 52 IN MODULATOR UNIT BC-456-B ARE PROVIDED WITH SIDETONE TAPS FOR LOW IMPEDANCE HEADSETS (70N T 50 AND 7 ON T 52). MODULATOR UNITS BC-456-A AND BC-456-B ARE NORMALLY FURNISHED WITH CONNECTIONS SHOWN IN SOLID LINES FOR USE WITH HIGH IMPEDANCE (8000 OHMS) HEADSETS. MODULATOR UNIT BC-456-B CAN BE CHANGED FOR USE WITH LOW IMPEDANCE (600 OHMS) HEADSETS BY SUBSTITUTING CONNECTIONS SHOWN IN DASHED LINES.
 4. TERMINAL NUMBERS APPEARING ON RECEPTACLES OF JACK J 51 IN MODULATOR UNIT AND J 64 IN TRANSMITTER AND ALL CIRCUIT SYMBOLS ARE FOR REFERENCE PURPOSES ONLY. THEY DO NOT APPEAR ON THE EQUIPMENT.
 5. * DISCONTINUED ON LATER EQUIPMENTS.

274N

WIRES	ARE
W	NO. 16
X	NO. 18
Y	NO. 20
Z	NO. 22


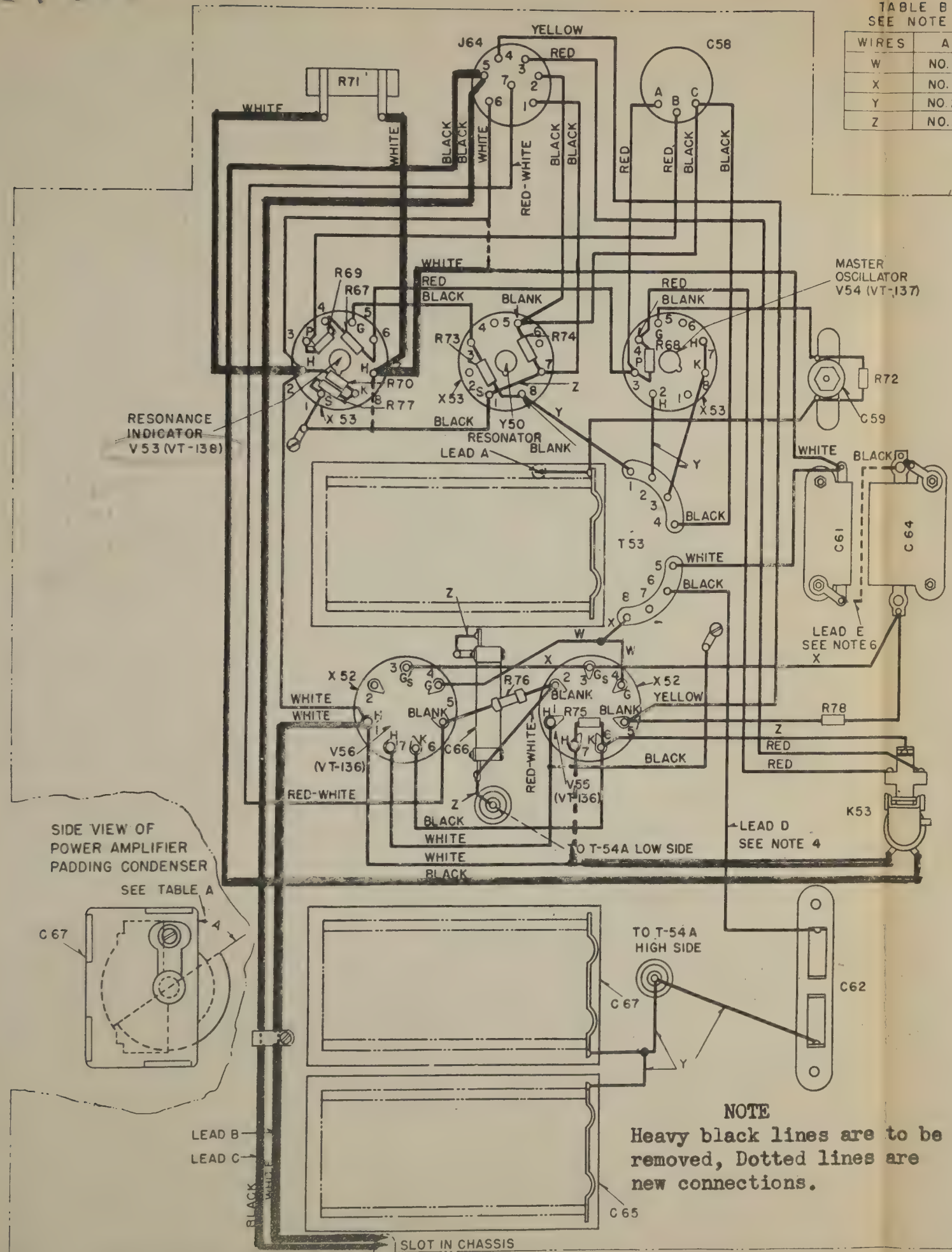
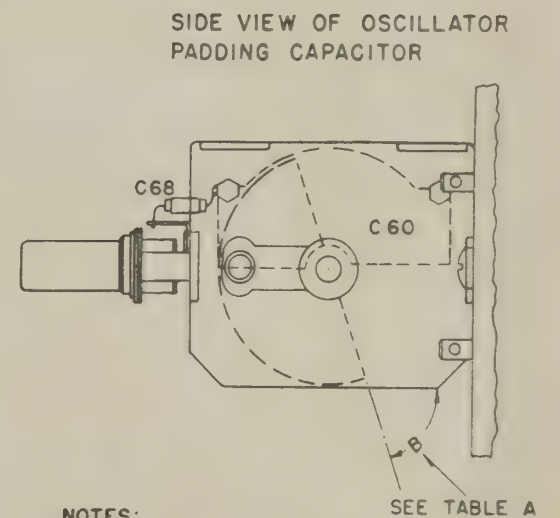
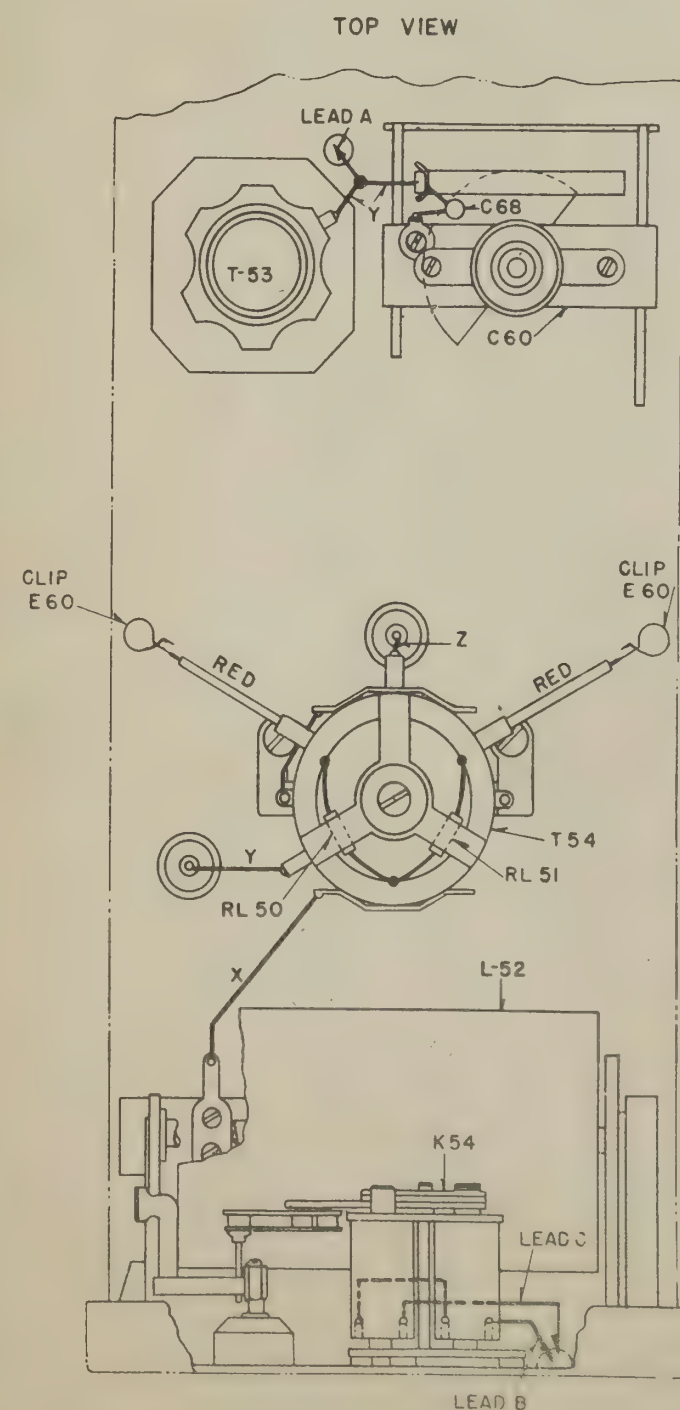
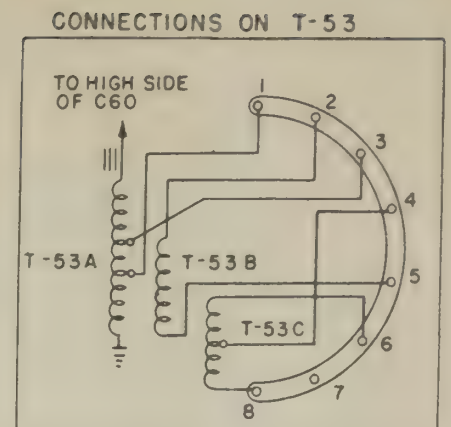



FIGURE 5-274N

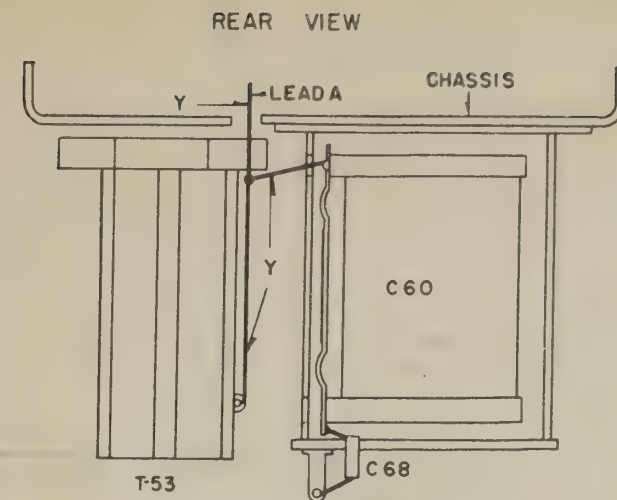


- NOTES: SEE TABLE A
1. ALL WIRES MARKED WITH COLOR ARE NUMBER 22 SOLID COPPER, WIRES MARKED RED-WHITE HAVE HEAVY INSULATION.
 2. WIRES MARKED W, X, Y AND Z ARE BARE TINNED SOLID COPPER WITH SIZES SHOWN IN TABLE B.
 3. TERMINAL NUMBERS AND LETTERS ARE FOR REFERENCE PURPOSES AND DO NOT APPEAR ON APPARATUS.
 4. PLACE LEAD "D" IN CORNER OF CHASSIS SO THAT IT WILL BE HELD SECURELY IN POSITION BY OTHER LEADS.
 5. DRESS LEADS RUNNING NEAR THREADED INSERTS IN THE CHASSIS SO THAT SCREWS PROJECTING THROUGH INSERTS WILL CLEAR THE LEADS BY AT LEAST 1/16 INCH WHEN SCREWS ARE FULLY TIGHTENED.
 6. GROUND TERMINAL ADDED TO C 61 AND LEAD "E" SHOWN IN DASHED LINES OMITTED IN LATER MODELS.
 7. TERMINALS MARKED BLANK ARE TIE POINTS ONLY & HAVE NO CONNECTION TO TUBES OR CRYSTAL IN SOCKET.

PADDING CONDENSER SETTINGS		
RADIO TRANSMITTER	C 67 ANGLE "A"	C 6Q ANGLE "B"
BC-696-A (3-4 MC)	52°	77 1/4°
BC-457-A (4-5.3 MC)	53 1/2°	78°
BC-458-A (5.3-7 MC)	56°	81 1/2°
BC-459-A (7-9.1 MC)	73 1/2°	95 1/2°

274 H
RCVR

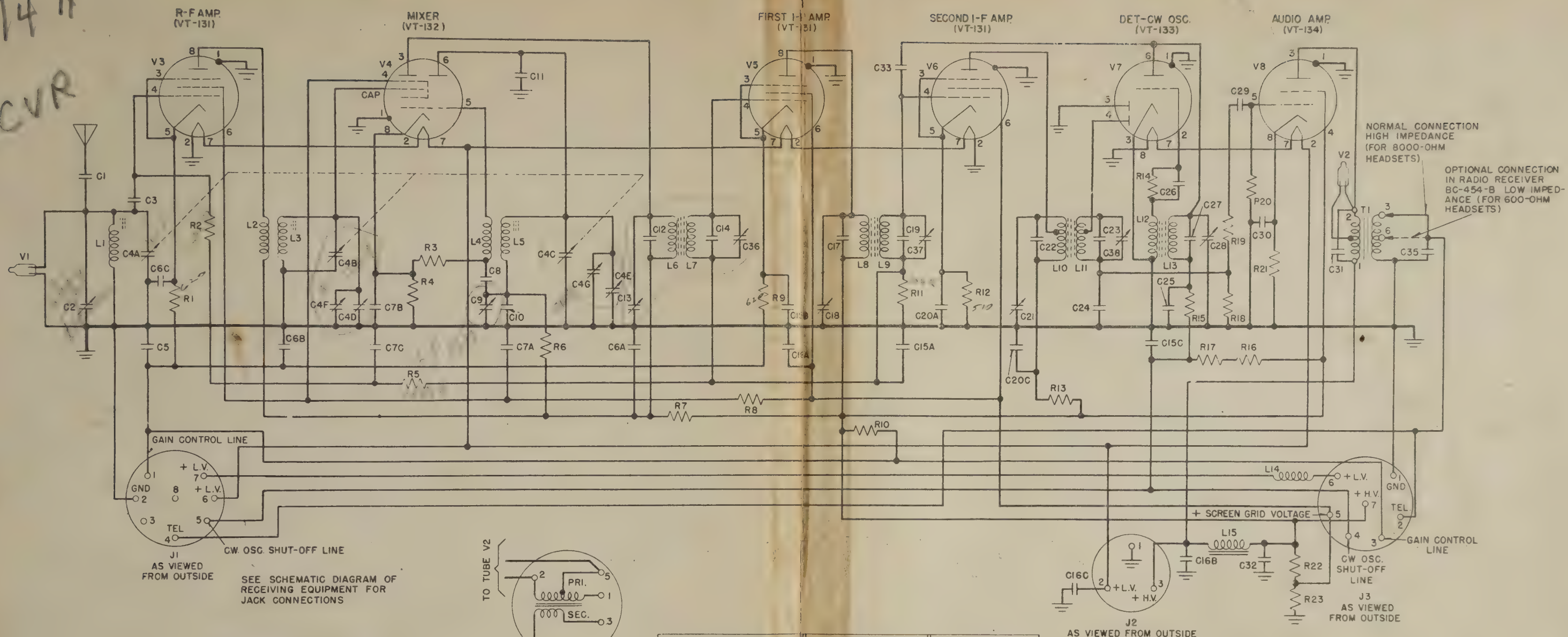

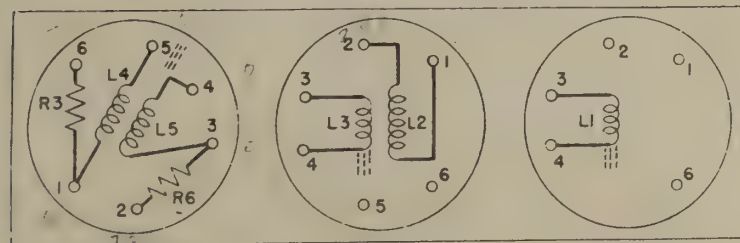DETAIL SCHEMATIC DIAGRAMS
COIL ASSEMBLIES AND TRANSFORMERS




SYMBOL Z5C
R-F OSCILLATOR

SYMBOL Z5B
R-F AMPLIFIER

SYMBOL Z5A
R-F ANTENNA

R-F COIL UNIT (3-6 MC) SYMBOL Z5

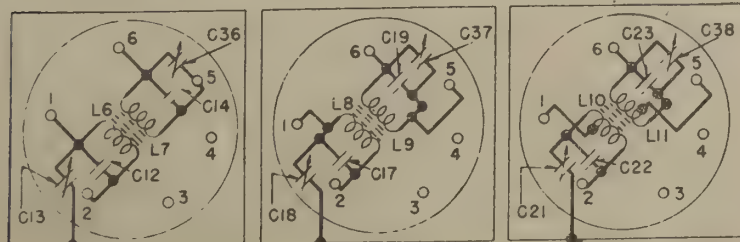


SYMBOL Z1
1ST I-F
1415 KC


SYMBOL Z2
2ND I-F
1415 KC

SYMBOL Z3
3RD I-F
1415 KC


I-F COUPLING UNITS

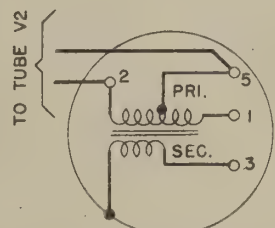

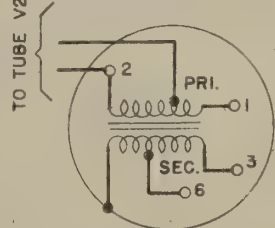SYMBOL T1
OUTPUT TRANSFORMER
RADIO RECEIVER BC-454-A



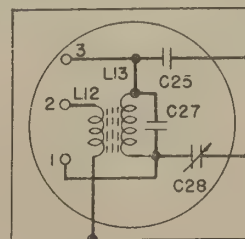
SYMBOL T1
OUTPUT TRANSFORMER
RADIO RECEIVER BC-454-B



SYMBOL Z4
CW OSCILLATOR
1415 KC

CAPACITORS		INDUCTORS		RESISTORS	
SYMBOL	DESCRIPTION	SYMBOL	DESCRIPTION	SYMBOL	OHMS
C1	11 MMF.	L1	ANT. INPUT	R1	620
C2	15 MMF.	L2, L3	RF AMP.	R2	2,000,000
C3	100 MMF.	L4, L5	RF OSC.	R3	51,000
C4 (A TO G)	GANG (147 MMF.)	L6, L7	IN 1ST IF	R4	620
C5	3 MF.	L8, L9	IN 2ND IF	R5	150,000
C6 (A,B,C)	.05/.05/.05 MF.	L10, L11	IN 3RD IF	R6	200,000
C7 (A,B,C)	.05/.05/.05 MF.	L12, L13	CW OSC.	R7	200
C8	200 MMF.	L14	RF CHOKE, 112	R8	200
C9	40 MMF.		MICRO-HENRIES	R9	620
C10	365 MMF.	L15	AF CHOKE	R10	360,000
C11	3 MMF.		3 HENRIES	R11	100,000
C12	180 MMF.			R12	510
C13	17 MMF.			R13	200
C14	180 MMF.			R14	100,000
C15 (A,B,C)	.05/.05/.05 MF.			R15	5100
C16 (A,B,C)	.22/.22/.22 MF.			R16	51,000
C17	180 MMF.			R17	51,000
C18	17 MMF.			R18	510,000
C19	180 MMF.			R19	100,000
C20 (A,B,C)	.05/.01/.05 MF.			R20	2,000,000
C21	17 MMF.			R21	1500
C22	180 MMF.			R22	7000
C23	180 MMF.			R23	7000
C24	200 MMF.				
C25	.001 MF.				
C26	100 MMF.				
C27	180 MMF.				
C28	34 MMF.				
C29	.006 MF.				
C30	15 MF.				
C31	.001 MF.				
C32	5 MF.				
C33	*				
C35	750 MMF.				
C36	17 MMF.				
C37	17 MMF.				
C38	17 MMF.				

* WIRING CAPACITANCE (LESS THAN 2 MMF.).

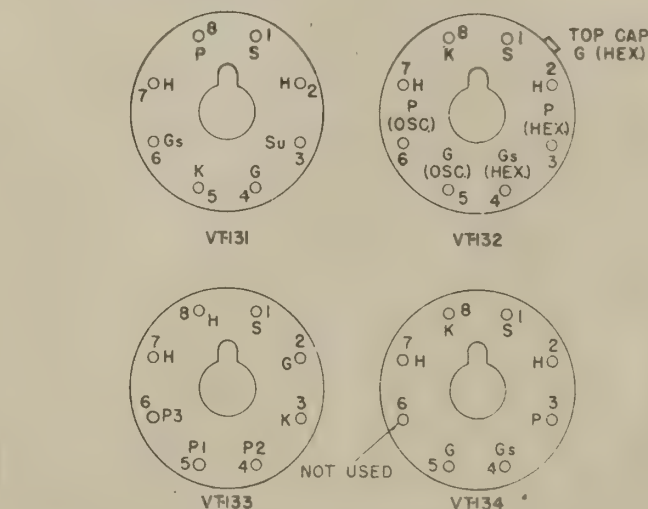

TUBE SOCKET TERMINALS AS VIEWED FROM BOTTOM

G=CONTROL GRID
G (HEX)=CONTROL GRID, HEXODE SECTION
G (OSC)=CONTROL GRID, OSC SECTION
Gs=SCREEN GRID
Gs (HEX)=SCREEN GRID, HEXODE SECTION
H=HEATER
K=CATHODE
P=PLATE
P (HEX)=PLATE, HEXODE SECTION
P (OSC)=PLATE, OSC SECTION
P1=FIRST DIODE PLATE
P2=SECOND DIODE PLATE
P3=TRIODE PLATE ON TUBE VT-133
S=SHELL
Su=SUPPRESSOR GRID

CIRCUITS IN R-F COIL SET, I-F COUPLING UNITS, CW OSCILLATOR, AND OUTPUT TRANSFORMER. THE TERMINAL NUMBERS ON THESE UNITS AGREE WITH THOSE SHOWN AT THE CORRESPONDING LOCATIONS ON THE PRACTICAL WIRING DIAGRAM.

FIGURE 7-274N

BC-375-E TRANSMITTER

As it stands, the BC-375-E is a master oscillator power amplifier type transmitter. It has been proven to most amateurs that it is not wise to use it in the present form for much difficulty would be experienced in trying to keep within frequency tolerances and the transmitter will not produce the power it is capable of or built to stand. It is our suggestion that the transmitter be revamped to allow it to use the present oscillator stage as a power amplifier. It is also our suggestion that the SCR-274-N command set transmitter and modulator be used as driver stages for both audio and RF for it is a "natural" for the job and is available at low prices.

Present audio input of BC-375-E is for carbon mike, directly to the grid of the driver stage of a class "B" set-up. The driver is a "210" type tube and will do the driving nicely if sufficient audio voltage is applied to the grid of this stage.

The oscillator of BC-375-E when re-wired to function as a power amplifier or doubler requires quite a bit of power to drive it well, and this may be furnished by the SCR-274-N transmitter. This particular unit is suppressor grid modulated, has approximately fifty watts output at max coupling and is a "bang up" fine business VFO. We have only to utilize the modulation voltages of the 274-N to drive the BC-375-E audio and the RF output of the same equipment to drive the RF and we have a very fine rig at the lowest possible cost.

The information given here is not offered as the acme of ways to use the BC-375-E and may not be entirely scientific in its approach but it will serve as a rough guide and when used will give the amateur a thought to build upon and work out his own needs and ideas.

Three drawings are included, Figure 1, BC-375-E is the original circuit schematic. Figure 2, 375 is a practical wiring diagram which is necessary to show positions and wire placements. Figure 3, 375, Figure 3, 274-N, Figure 5, 274 shows schemes suggested above.

The BC-375-E has the necessary components to work over into many different rigs or it may be left in its original form or torn apart and re-assembled.

The proud possessor of a newly acquired BC-375-E may be somewhat cowed or intimidated by the appearance of the inside of the set. There is good reason for this because of the compactness and the maze of wires that seem to be connected to everything at once.

Perhaps if we offer the following tips and hints the way might not be hard and after becoming familiarized with the set, its compactness can be appreciated.

To start; completely strip the transmitter of all cover plates. These are the back, top, and sides and come off easily by removing the screws. May we suggest at this point that you get all small wrenches, screw drivers, pliers, socket wrenches and other sundry tools that may be found on the premises for the set is bolted together as solid as the Rock of Gibraltar and it will take quite a variety of tools to break it down. Start at the top by cutting the leads that go to resistor 1196, that's the big filament dropping resistor, and remove it from its holding clamps by taking out the long mounting through the resistor.

Take out the screws that hold the resistor terminal board and lift the assembly off. Turn the transmitter upside down and unsolder those heavy, bare, tinned leads that reach back to the resistor strip that's mounted in the rear of the set. When there are no more solid bus leads to hold the resistor strip go to its ends and remove the two screws that hold each end to its mounts. A long heavy screw

driver is required for the antenna tuner end for reaching through holes in the chassis. When the strip is free it may be manipulated enough to pull it out and back from the chassis. Now start with a sharp knife or razor blade to cut the binding cords that are used to cable the leads together. Don't try to save the pretty cabled appearance of the lead groups, for, too many leads will have to be removed or changed. Cut all the cord that can be reached for the looser the wires are the easier the work will be. Now with the wires loose and the strip pulled back, turn the set right side up and facing front. On the panel behind the oscillator tube compartment are four good sized binder head screws. Remove these and you will find the bakelite submounting panel for the audio input components is now loose. Pull it back from the panel and you can reach the nuts on choke 1146 mountings and those on the capacitor 1147. These formed a filter for using 27 VDC in the carbon mike. Take the two parts off and there will be more room to work.

The article in "Dec. 1946 QST" suggests a speech amplifier stage that can be mounted in this space. This done, put the set back on its top and start removing the Tone-CW-Voice switch 1141. Snip off all leads first to facilitate things. Removing the shaft extension also speeds up the work; next, remove the trimmer and compensator condensers 1103 and 1104. These are beautiful pieces of work but we don't need them for the oscillator is to be changed to a power amplifier. (1104 is a bi-metal supported temperature compensating condenser) also remove the interlock switch 1102 and test key switch 1131 and while we are about it let's remove a few by pass condensers that are not immediately needed and will give us a little more space to work in. These are condensers 1142 (up on the panel that holds the power plugs) and 1150 (attached to the bakelite speech input mounting) and 1180 (on the inside of main resistor strip).

With these parts out we have one deft manipulation to perform before the actual wiring can be begun. In order to get to the audio amplifier tubes socket the modulation transformer must be lifted out of the way. The nuts on the transformer bottom are reached by a socket wrench through the antenna loading section. There is one nut that will give trouble. It is behind the RF switch 1168 in the loading section. After looking over the possibilities of removing the switch this department decided it wasn't worth the effort and so went to work on the nut with a long pin punch from the back of the transmitter. With a little patience the nut can be removed in this fashion. By pulling the resistor strip as far away from the set as possible to give more room, the audio transformer may be jockeyed out of position and pulled back and out of the way of the tube sockets.

Unsolder the leads from the voltmeter to the by-pass condenser and then take out the meter face screws for voltmeters and milliammeter. By slipping the meters partly out of their mounting holes it is much easier to get into the wiring of the sockets.

Now with everything out of the way the re-wiring may proceed. Please note that there are two ground connections to the filament circuits that must be removed. These are copper straps and very solidly soldered to the minus filament terminal on the sockets of the master oscillator and one of the audio tubes.

We will not attempt to give a wire by wire description for there is the practical schematic 2-375 showing location and number of each part.

The audio line which formerly went to the aircraft sidetone circuits may be used to inject the audio driver

power. This winding is tapped so that most any audio amplifier can be matched into it. The tap switch 1179 is adjusted from the front and is on the panel behind the tubes. The wiring for this is shown in diagram 3. The sidetone was taken from a winding on the driver transformer. The taps on this transformer are approximately for the following impedances:

- No. 1— 150 ohms
- No. 2— 400 ohms
- No. 3—2000 ohms
- No. 4—4000 ohms

This is a fair range of taps and should allow the use of practically any type amplifier to be found in the usual ham shack.

For audio drive from a smaller voltage source of power use the jack shown that goes to the primary of the mike transformer 1149.

For the RF input we installed a Jones S-101 type coax socket in the front panel in the hole left from the "test key". A lead was soldered from the contact of this plug to the grid line behind the Parasitic suppressor of the former oscillator. A small transmitter condensor of 50 MMFD was put in place of the tone CW-VOICE switch and connected across the oscillator grid. (This is not shown in the drawing). This was used to aid in resonating the vari-

ous types of RF input tried. For those who do not wish to use the audio driver tube, the socket may be utilized for a plug-in input grid coil. This would work out very nicely for all purposes.

The antenna relay possesses little merit for AC voltage operation. It is simpler to screw down the limit adjustments till relay is closed and leave it in that position, although it may be used by employing dry cell batteries.

For CW operation the antenna relay shorted out resistor 1115 thus lowering the bias on the tube grids. The Hi voltage negative return was across this resistor thereby biasing all tubes to cut-off. This type keying may be preserved by bringing the shorting lead for this resistor to a jack located on the panel.

For bias the best and simplest method are "B" batteries. Modulator tubes require 72-75DC volts, speech amplifier requires 35-40 DC volts. To simplify wiring a biasing controlled as usual by potentiometers provided in the original.

In order to use the tuning units supplied it will be necessary to change or modify them somewhat. As they are now there will be insufficient driving voltage to the final grid and the taps on the coil must be changed. We suggest the owner look up a December 1946 copy of QST for reference to coil changes.

BC 375E
xmitter

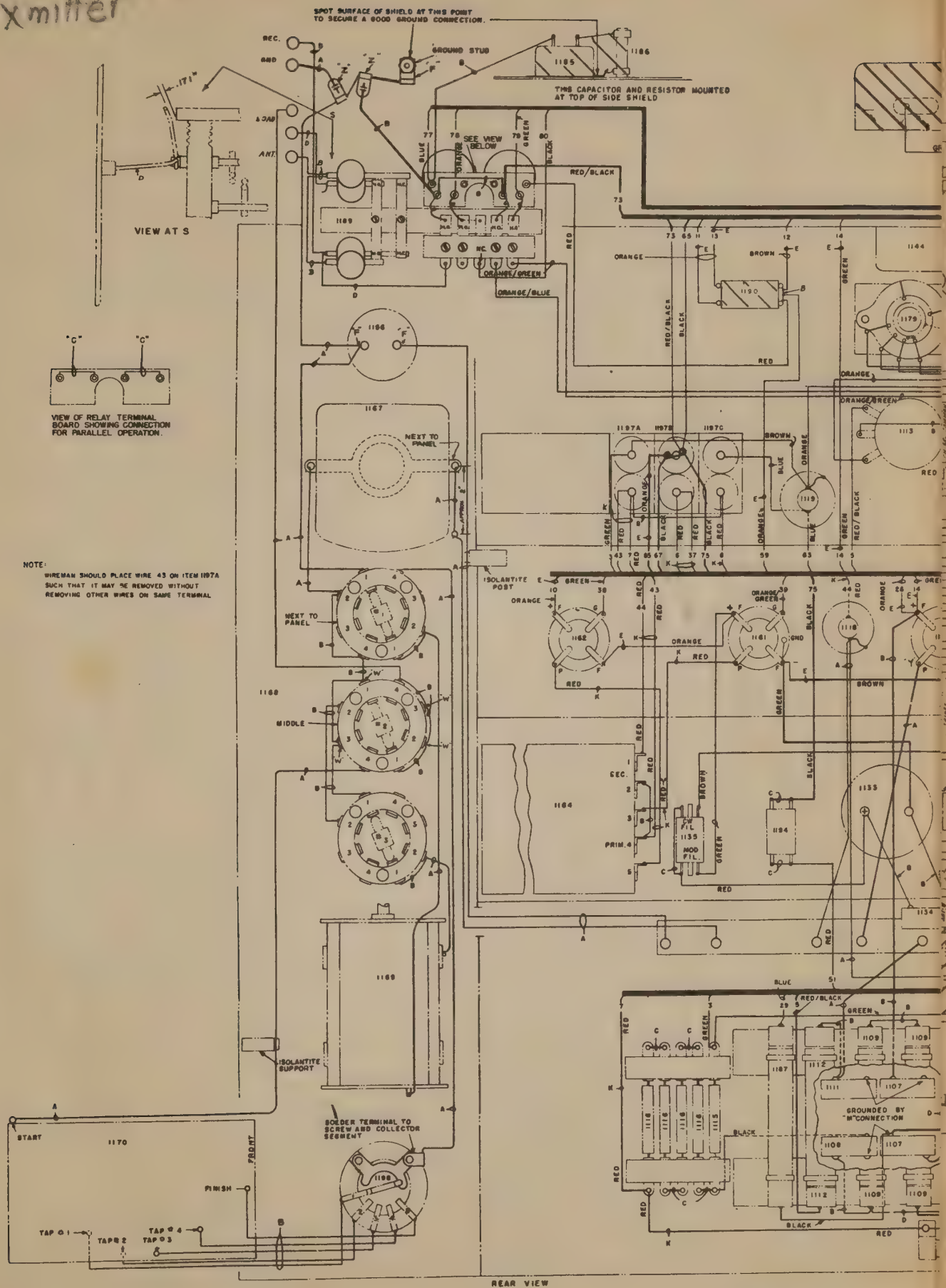


FIGURE 2-375

power. This winding is tapped so that most any audio amplifier can be matched into it. The tap switch 1179 is adjusted from the front and is on the panel behind the tubes. The wiring for this is shown in diagram 3. The sidetone was taken from a winding on the driver transformer. The taps on this transformer are approximately for the following impedances:

- No. 1— 150 ohms
- No. 2— 400 ohms
- No. 3—2000 ohms
- No. 4—4000 ohms

This is a fair range of taps and should allow the use of practically any type amplifier to be found in the usual ham shack.

For audio drive from a smaller voltage source of power use the jack shown that goes to the primary of the mike transformer 1149.

For the RF input we installed a Jones S-101 type coax socket in the front panel in the hole left from the "test key". A lead was soldered from the contact of this plug to the grid line behind the Parasitic suppressor of the former oscillator. A small transmitter condensor of 50 MMFD was put in place of the tone CW-VOICE switch and connected across the oscillator grid. (This is not shown in the drawing). This was used to aid in resonating the vari-

ous types of RF input tried. For those who do not wish to use the audio driver tube, the socket may be utilized for a plug-in input grid coil. This would work out very nicely for all purposes.

The antenna relay possesses little merit for AC voltage operation. It is simpler to screw down the limit adjustments till relay is closed and leave it in that position, although it may be used by employing dry cell batteries.

For CW operation the antenna relay shorted out resistor 1115 thus lowering the bias on the tube grids. The Hi voltage negative return was across this resistor thereby biasing all tubes to cut-off. This type keying may be preserved by bringing the shorting lead for this resistor to a jack located on the panel.

For bias the best and simplest method are "B" batteries. Modulator tubes require 72-75DC volts, speech amplifier requires 35-40 DC volts. To simplify wiring a biasing controlled as usual by potentiometers provided in the original.

In order to use the tuning units supplied it will be necessary to change or modify them somewhat. As they are now there will be insufficient driving voltage to the final grid and the taps on the coil must be changed. We suggest the owner look up a December 1946 copy of QST for reference to coil changes.

BC 375E
xmitter


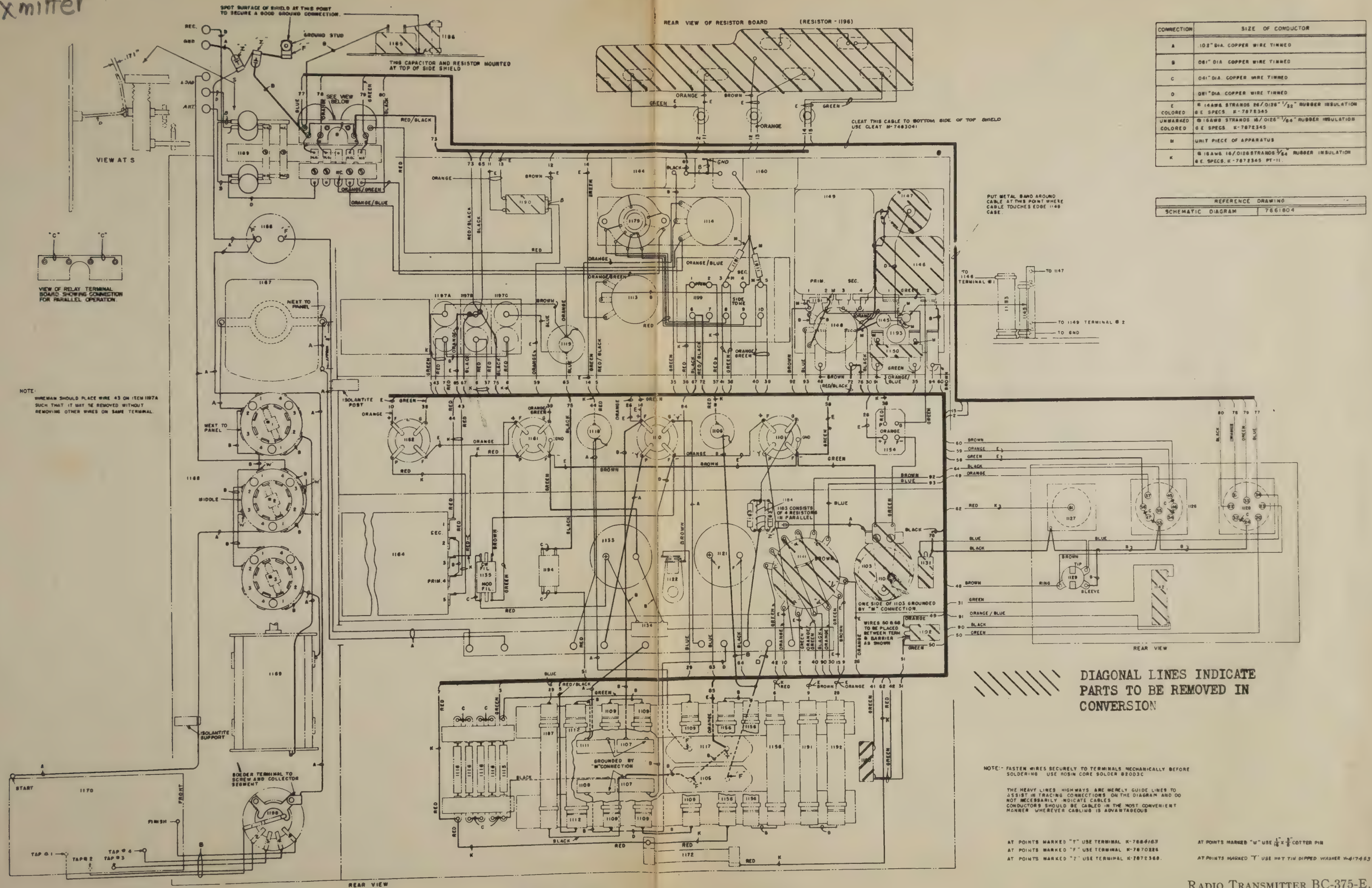
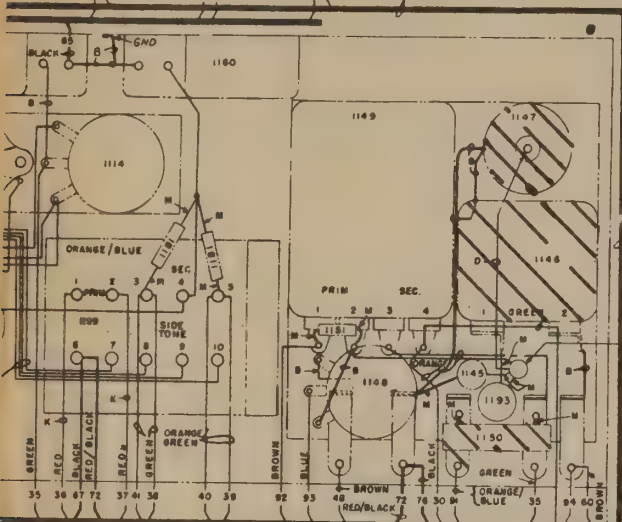



FIGURE 2-375

RADIO TRANSMITTER BC-375-E, CONNECTION DIAGRAM

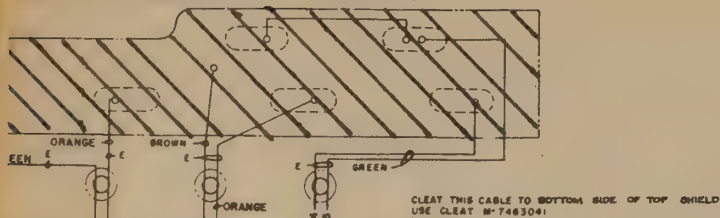REAR VIEW OF RESISTOR BOARD (RESISTOR - 1196)





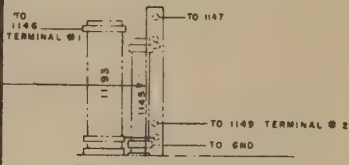PUT METAL BAND AROUND CABLE AT TWO POINT WHERE CABLE TOUCHES EDGE 1146 CASE



CONNECTION	SIZE OF CONDUCTOR
A	.102" DIA. COPPER WIRE TINNED
B	.061" DIA. COPPER WIRE TINNED
C	.061" DIA. COPPER WIRE TINNED
D	.061" DIA. COPPER WIRE TINNED
E	8 14AWG STRANDS 96/0126" 1/32" RUBBER INSULATION COLORED G.E. SPECS. K-7872345
UNSHARDED	8 14AWG STRANDS 96/0126" 1/32" RUBBER INSULATION COLORED G.E. SPECS. K-7872345
M	UNIT PIECE OF APPARATUS
K	8 16AWG 16/0126 STRANDS 3/64" RUBBER INSULATION G.E. SPECS. K-7872345 PT-11.

REFERENCE DRAWING	
SCHEMATIC DIAGRAM	7561804

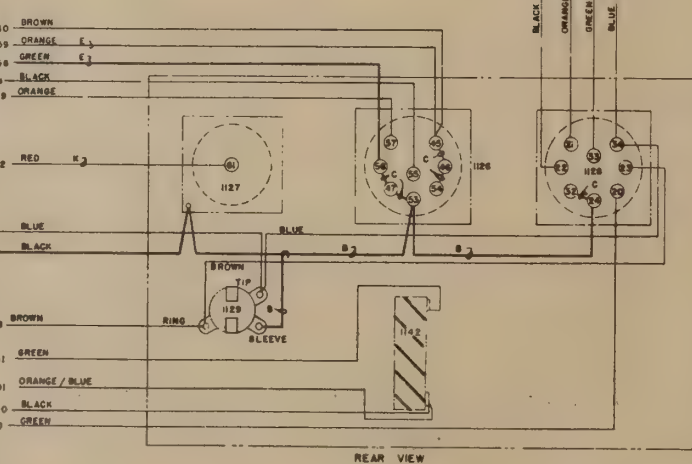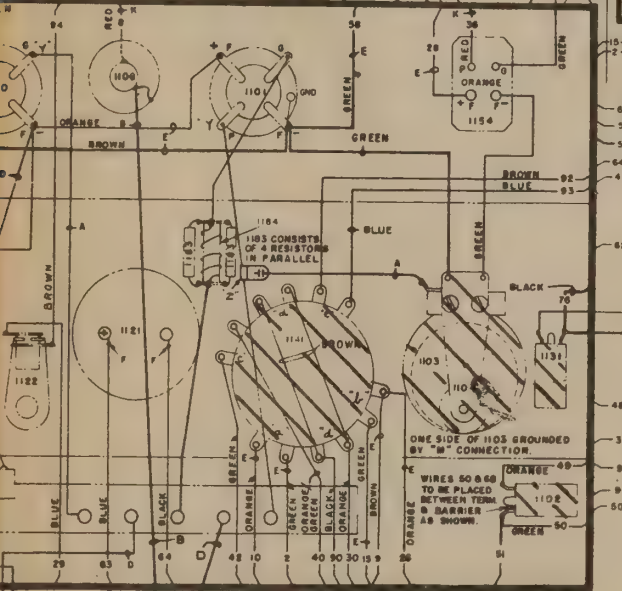

DIAGONAL LINES INDICATE PARTS TO BE REMOVED IN CONVERSION

NOTE:- FASTEN WIRES SECURELY TO TERMINALS MECHANICALLY BEFORE SOLDERING. USE ROSIN CORE SOLDER 820D3C.


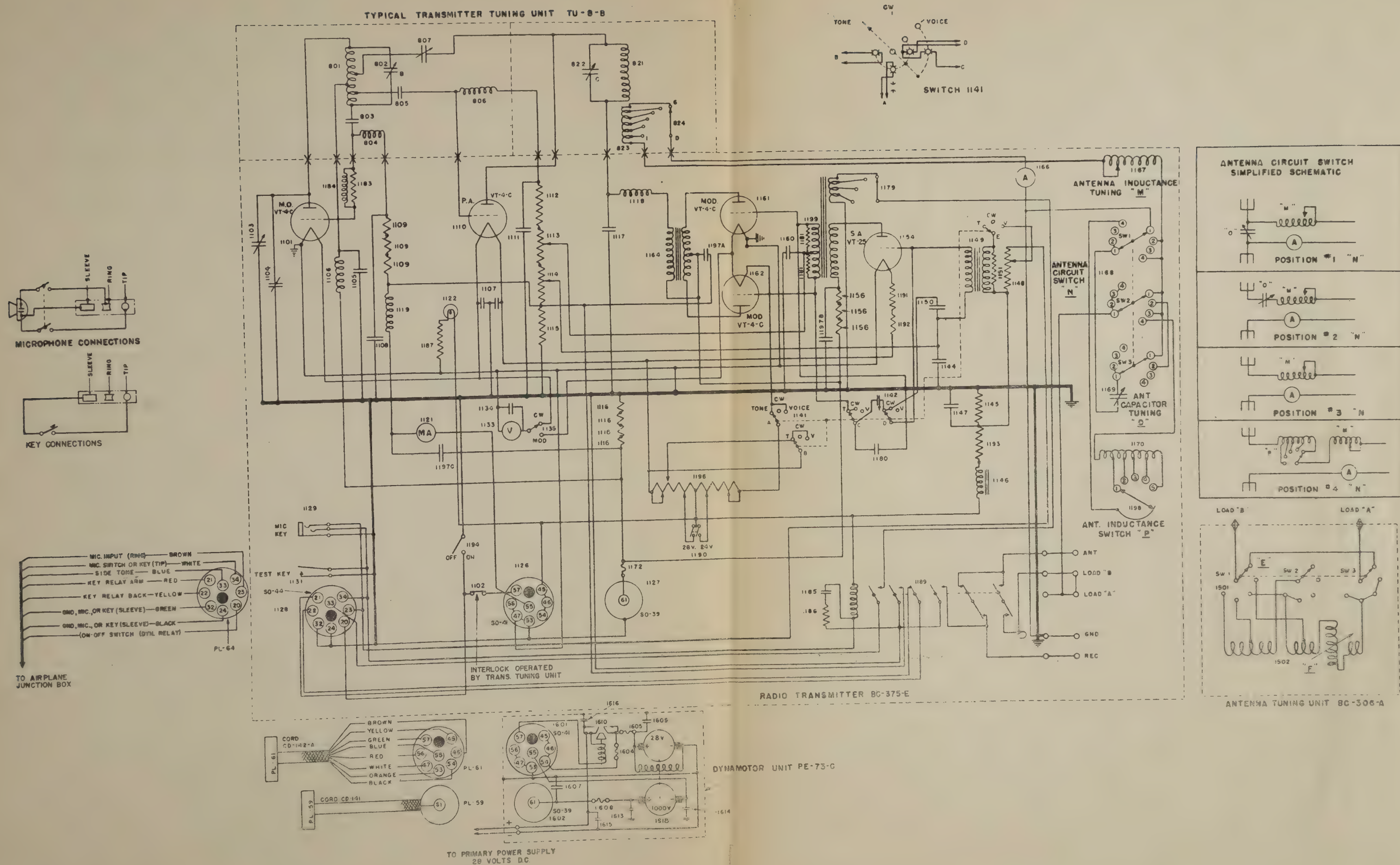


Figure 1-375

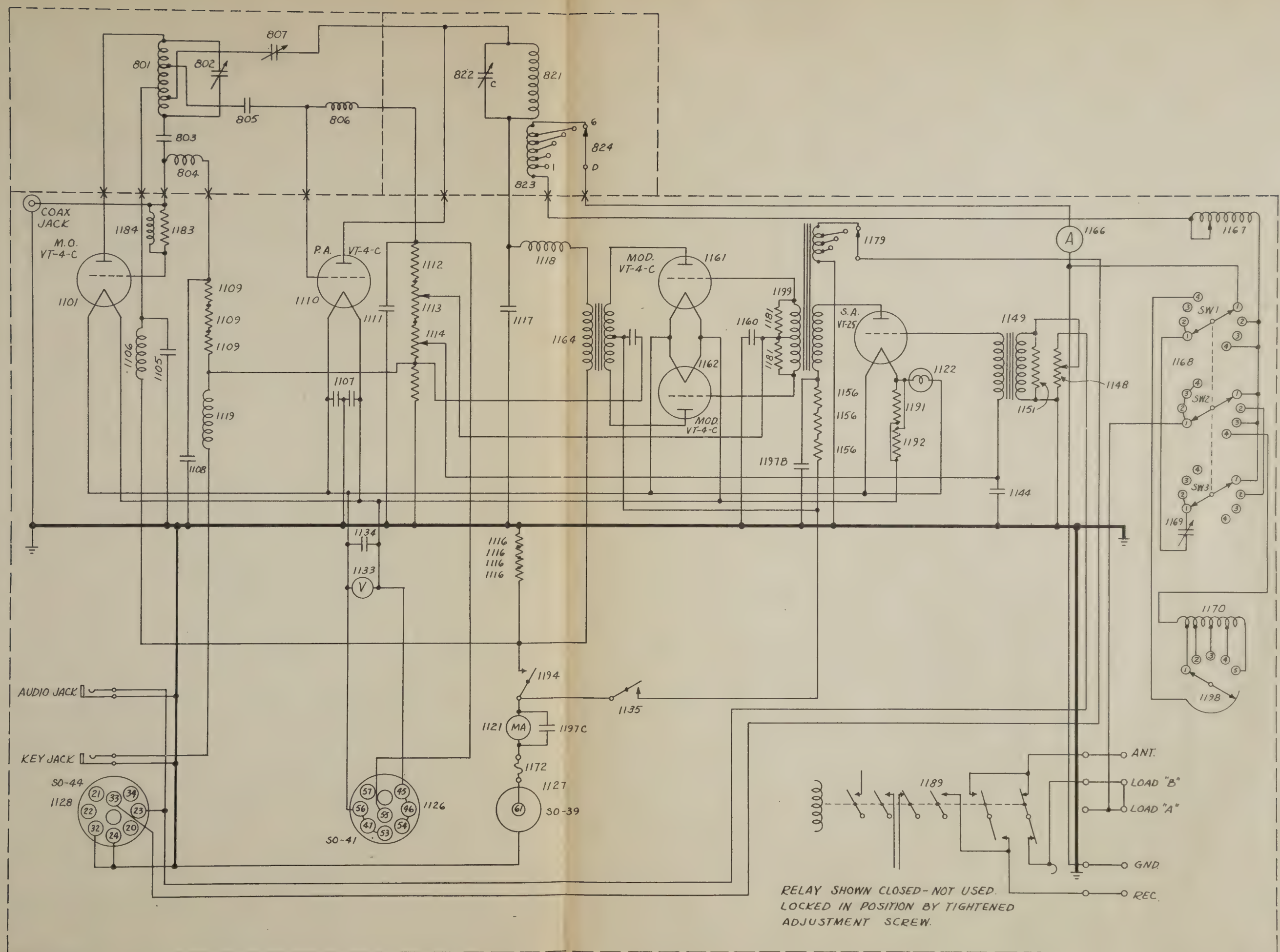

F. G. 3-375

LIST OF DRAWINGS FOR SCR-522

- Figure 1 —Shows connections for using 522 in original wiring for 27 VDC or with Electric motor driving.
- Figure 2 —Same as Figure 1
- Figure 3 A-B—Shows steps in rebuilding 522 band changing motor.
- Figure 2-A —Gives radii and shows how cuts are made in genemotor case to allow reversed genemotor to protrude from one end.
- Figure 4 —A practical wiring diagram for FT-224 showing new connections for use of 522 with 110V AC power pack.
- Figure 5 New locations of parts for converting FT-224 for 110 AC operation.
- Figure 6 —Self explanatory drawings of field windings on genemotor and lead switching for paralleling the fields for 12 volt operation.
- Figure 7. —Original schematic of BC-625 transmitter.
- Figure 8 —Original schematic of BC-624 receiver.
- Figure 9 —Complete original, overall schematic of transmitter-receiver power supply and wiring harness.

SCR-522

Many articles have appeared, to date, in different radio publications offering various means of converting the SCR-522 VHF set. These articles are good and we have tried them, but there is one thought we should like to put forth that no previous article has mentioned. This is, simply use the SCR-522 in its original case and not bother to separate transmitter from receiver and build separator panels, chassis and power supplies. We even find it convenient to leave on the band changing equipment and thus utilize a quick change of bands for the transmitter.

With the receiver and transmitter left in the case and with the rack FT-224 left on to connect to the terminals of them it is only necessary to incorporate the few simple changes given in the following drawings and script and we have a table mount VHF that is small and very convenient.

To convert the SCR-522 for power pack operation and retain the equipment case we need only to modify the rack FT-224. The following plans and descriptions will give a fair idea of how this is done. When the changes are completed a Prestwood panel is installed over the face of the rack with cut-outs over the transmitter crystal sockets and tuning dials, an O-1 millimeter mounted in the panel in the space left by cutting away the body of the ratchet motor. Shaft extensions are brought out to knobs for the receiver tuning controls and gain controls for Receiver and Transmitter. The metering switch of the transmitter is also extended to the panel.

RACK CHANGES FOR 522

1. Open the two hinged covers on the set, by turning with a screw driver, the four DZUS fastens, now remove the four hinge bolts that are at the corners of the frame and lift off the hinge covers. BC-624 and BC-625 are attached to FT-224 (the frame work that holds the two together) by four each, shoulder studs. These are easily found for they are painted red. Before loosening these studs grasp the ratchet motor, which drives the band changing mechanism, and by alternately squeezing and releasing the armature (the movable part of the motor),

identified by the two coil springs attached to one end. Force the mechanism through one cycle, far enough to bring all plungers back to neutral. Now take out the red studs and gently pry the rack FT-224 off the transmitter and receiver. This can be accomplished by slipping a screw driver under the rack and gently prying it up.

2. Lay out FT-224 and take out the two end screws and the four screws around each plug of the center cover and the plate may be lifted off.

3. With wire cutters, snip the leads to the two power and control plugs and remove same, snip leads to the ratchet motors and take out by removing four screws on the back of the rack and on the top, attached to the plunger frame. Next to go are the three relays 411-1, 411-2 and 412 (they have numbers printed beside each one on the frame) the screws holding these are easily found. Next to come out are condensers 401, 402 and switch 426. We also remove antenna plug 416 and its mounting base. The antenna plugs which connect to the transmission and receiver are a part of this assembly and must be put back. Now cut out all the original wiring with the exception of the braid covered leads connected to pins 1 and 2 off transmission plug 418-1. The net result of our labors thus far is a chassis or frame stripped of all it held with the exception of three plugs and the tuning slides.

4. Drill a $\frac{3}{8}$ " hole in the center of the right hand handle grip pocket. When drilled (or routed out with a rat tail file) slip the antenna connector through the hole and with a scribe mark the 4 screw holes and drill with a $\frac{1}{8}$ " drill. Fasten the antenna connector screws before replacing the transmitter receiver plug strip for the bottom screws are impossible to reach if not put in first. Next we install the power plug. This may be most any type of plug or strip which will fit into the width of the side of FT-224. We could of course use the original plug in the original place but this would spoil the appearance and be in the way in front of our panel. There are many types of plugs available. We used a Jones plug of 6 contacts because it was small and flat sided. A terminal strip on the outside would do just as well. At any rate, it is suggested that it be installed on the left side of the rack as close to the bottom as possible without interfering with transmitter plug 418-1.

Cut out the metal bracing strip in the upper left hand corner as marked in 192 as it will be in the way of the shaft extension of the audio control beneath it. As the band changing ratchet motor will not function on AC we must modify this useful piece of equipment. First remove all the screws and bolts until we have all parts removed from the frame. Now with a hacksaw cut the frame in three places as shown in Figure 3A, with cutting done we tap out the shaft hole in the ratchet with an 8-32 tap. This allows one of the red painted studs that formerly held rack FT-224 to transmitter-receiver assembly to be screwed into ratchet wheel shaft thus giving us a shaft to attach a knob to. Cut $\frac{3}{8}$ " from the screw end of the small shaft that formerly went through the ratchet wheel and spread it slightly by tapping with a hammer until it is a force fit into the bottom end of the ratchet wheel shaft. Be sure to allow it to protrude enough to go into the hole punched for it in FT-224 for it serves as a guide pin in aligning the ratchet motor frame. We now have only to ream out the top shaft hole in the motor frame to 5-16" and by reassembling the band control is finished as shown in Figure 3 B.

In the left hand grip pocket drill two $\frac{3}{8}$ " equally spaced holes to receive mike and headset jacks.

522 RECEIVER

The receiver as it stands is crystal controlled and therefore is bound to whatever frequencies the operator possesses crystals for.

This may be rectified in a number of ways. The first suggestion tried by us works out very well but has bad feature of high cost. Four Bliley VFI variable frequency crystals were obtained and plugged into the receiver. Fair coverage was obtained in the two meter band. Tuning is sharp but clumsy because of the complex controls, which made it necessary to check the receiver through the range with a signal generator before using it in order to log the dial positions.

Changing the crystal circuit to a self exciting oscillator did not cure the headaches of tuning, but by using a very small tuning capacity nice coverage over the 2 meter band was obtained by fixing the RF and Harmonic generator first and then tuning by the ex-crystal stage. complete revision of the RF end or the 522 receiver would of course be the ideal solution but to us, and to most others, the challenge was to evolve a usable circuit from the original. Of all the ideas advanced toward this end we find that the best was offered by Ray Frank, Amateur Editor, Radio News in the October 1946 issue of that magazine. This article gives the necessary pertinent data for changing the harmonic generator to an oscillator and reduces the set controls to two knobs. That system has worked out best of all. The control knob of the harmonic generator must be geared 40 or 50 to 1 in order to keep the tuning from being critical. Also the RF line up. To most users the critical point was not noticed in the RF stages as the sets are used for local rag-chewing but the RF is capable of good gain and sharp tuning when properly aligned.

In an effort to spread the 2 meter band across a wider portion of the dial or get away from the high ratio tuning dial and critical alignment of stages the old device of inserting a series condensor in the tuning circuit was tried. National type M-30 trimmer condensers were inserted between the coil and tuning condensor, these have a maximum capacity of 30 MMF. This effectively reduces the capacity of the tuning condensers to the point where the band is spread out appreciably.

TRANSMITTER

One good use for the BC-625 transmitter that has been overlooked by many amateurs is 6 meter band operation. The plate circuit of the oscillator is tuned to the second harmonic of the crystal, this is fed to the first harmonic amplifier whose plate circuit is resonated to the 3rd multiple of the 2nd harmonic or the 6th crystal harmonic. Using a 8.5833 k. c. crystal in the oscillator puts 51.5 m. c. to the grids of the 2nd harmonic amplifier it remains only to wind up new tank coils for the second harmonic amplifier and final tank.

DYNAMOTOR

The SCR-522 is designed to operate from two D. C. sources, 14 and 27 volts. There is a separate motor generator built to operate from each of these voltages, PE-94-A is the 27 volt unit and PE-98-A for 14 volts. PE-98-A for 14 volt operation are scarce for few airplanes had a 14 volt battery system. Most SCR-522 now available come equipped with PE-94-A. There is no difference in the transmitter and receiver for they are in all cases wired for 12 volts filament and relay control. Each genemotor has a low voltage commutator delivering 12 volts for trans-

mitter-receiver. In some instances 12 volt battery operation may be desired and only a PE-94-A is available. By making a number of changes in the field windings of the genemotors and combining the motor action of the 27 volt motor end together and by using battery source for filaments and relays, operation of SCR-522 may be used. This is not satisfactory from a perfection point of view for we loose ampere turns in the field and there is no way to reduce the number of turns or increase the wire size of the motor winding of the armature. New field windings may be wound up and successfully used but this writing will not attempt this for it is doubted that many experimentors will be interested. The following diagrams are given for those who may wish to have on hand an emergency hookup that can be done in a short while and requires nothing more than a few solder connections.

In using the SCR-522 we must have a power supply. The one that came with it originally was designed to operate with a D. C. input of 27 VDC at a current of 13 amperes. To most people this is not an ideal set up for 27 volt storage batteries are not generally found around the average household. However, close examination of the power genemotor supplied with the SCR-522 will reveal that it may be used as a straight generator provided: Some external mechanical means are used to furnish the rotating power. Tests in actual operation have proven that $\frac{1}{4}$ horsepower is needed for the job. The generator is already equipped with $\frac{1}{2}$ inch shaft to fit a standard "V" pulley to and by turning the generator end for end in its mounting the pulley will protrude enough to attach a belt to it.

COLONIAL MODEL

Take out the screws on both ends of the cover. You will find the dynamotor held in position by a steel compression strap. On the low voltage end of the dynamotor you will find three large leads colored green, blue and yellow. On the high voltage end there are three smaller leads colored red, orange and green with a braided ground strap attached to the genemotor case.

The large wires are: yellow, positive 27 volts to field and motor winding, blue, positive 27 volts from carbon file regulators to shunt control field of genemotor. The smaller wires are: red, positive 300 volts plate supply; orange, minus 150 volts bias voltage for transmitter; green (brown, black, white according to model) is 14.5 volts positive for filament and relay supply to SCR-522.

1. Remove the wires from the high and low voltage connections and unscrew the connecting bolt from the compression band that holds the genemotor.

2. Lift the dynamotor from the case and remove the end bell covers from both ends. The low voltage end cover is the shorter of the two and is held by two screws in the end case. The longer cover is held by four screws arranged around the circumference of the dynamotor case.

3. You will find a blower fan on the armature shaft at the high voltage end of the dynamotor. This is held by two allen set screws. Remove the fan.

4. With a circle cutter make a one-and-one half ($1\frac{1}{2}$) inch hole in the end center of the shorter end bell cover.

5. Remove all four screws from the bearing cover at the high voltage end of the dynamotor and put the short end bell cover over this end. Use two screws only to hold the bearing cover plate and end bell cover.

6. The longer end bell cover may be left off for better cooling or slipped on and held by a bank of masking or

adhesive tape, or, better still, drill and tap the low voltage end bell for 6-32 screws so the cover will attach as it did when on the opposite end.

7. As the dynamotor will be placed back in the chassis in a reversed position to allow the shaft end to protrude, the case must be altered slightly to allow for this. Assume that the right hand end of the chassis is when viewed facing the unit with both plugs toward you, with a pair of tin snips cut out the steel mesh screen in the chassis cover on the right hand side also the bottom and back side supports for the screen. Now a small curved section in the top, bottom and back of the right hand end must be removed to allow room for the dynamotor end bell cover to protrude. We do this the easy way by placing the dynamotor in the chassis with the shaft flush with the right end then inscribe with a divider compass a $2\frac{1}{4}$ " radius and cut out the sections of arc that were within the radius. **Figure 2** gives the idea.


8. Now the dynamotor may be put back in its cradle and strapped down. The leads are replaced in this manner. Large yellow lead in its original place on top of 2 of the

start-stop relay. Large green lead under the small bolt that held the braid grounding strap. Remove the short red lead from taps 1 and 3 off the start-stop relay and low volts input filter and using taps 1 and-or, 3 as a terminal place the large blue lead and the smaller blue lead coming from the carbon file regulator together. Replace the red, orange and brown leads going from the high voltage parts of the genemotor in their original positions—it may be necessary to cut a new feed through hole in the firewall separating the generator from the filter compartments due to short length of large leads.

9. We now have a genemotor that will supply the high and low voltages required by the SCR-522. It may be driven by an electric motor or gas engine. The usual $\frac{1}{4}$ horsepower motor will drive this generator if not overloaded. Reading from the manufacturers plate on the dynamotor we find that it originally ran at 4700 RPM. The closer to that speed the generator is run the better regulation is obtained by the carbon file regulator. However, by using a $\frac{1}{4}$ HP motor with a 5" "V" pulley and 2" "V" pulley on the generator sufficient voltage is obtained for good operation.

SOCKET CONNECTIONS

CONTROL HEAD TO TRANSMITTER-RECEIVER

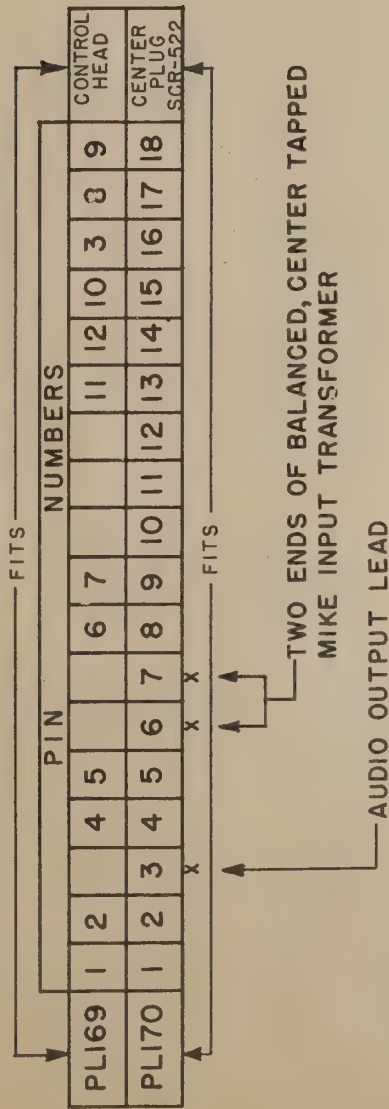


NOTE:
 ALL PLUG PINS IN UPPER BOXES ARE CONNECTED
 TO PINS IN LOWER BOXES, AS AN EXAMPLE
 PIN NO. 7 OF PL169 IS CONNECTED TO PIN NO. 9
 OF PL170.

FIGURE 1


SOCKET CONNECTIONS

POWER SUPPLY TO TRANSMITTER-RECEIVER

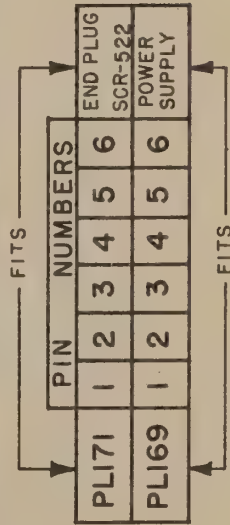

NOTE:
 THESE CONNECTIONS FOR USE OF SGR-522.
 WITH SET UNCHANGED AS TO CIRCUIT.

FIGURE 2-522

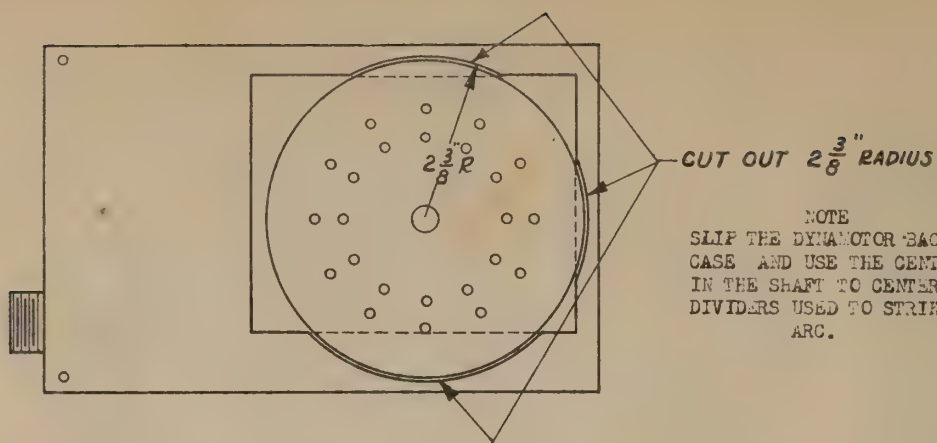

NOTE
SLIP THE DYNAMOTOR BACK IN THE
CASE AND USE THE CENTER HOLE
IN THE SHAFT TO CENTER THE
DIVIDERS USED TO STRIKE THE
ARC.

FIGURE 2 A 522

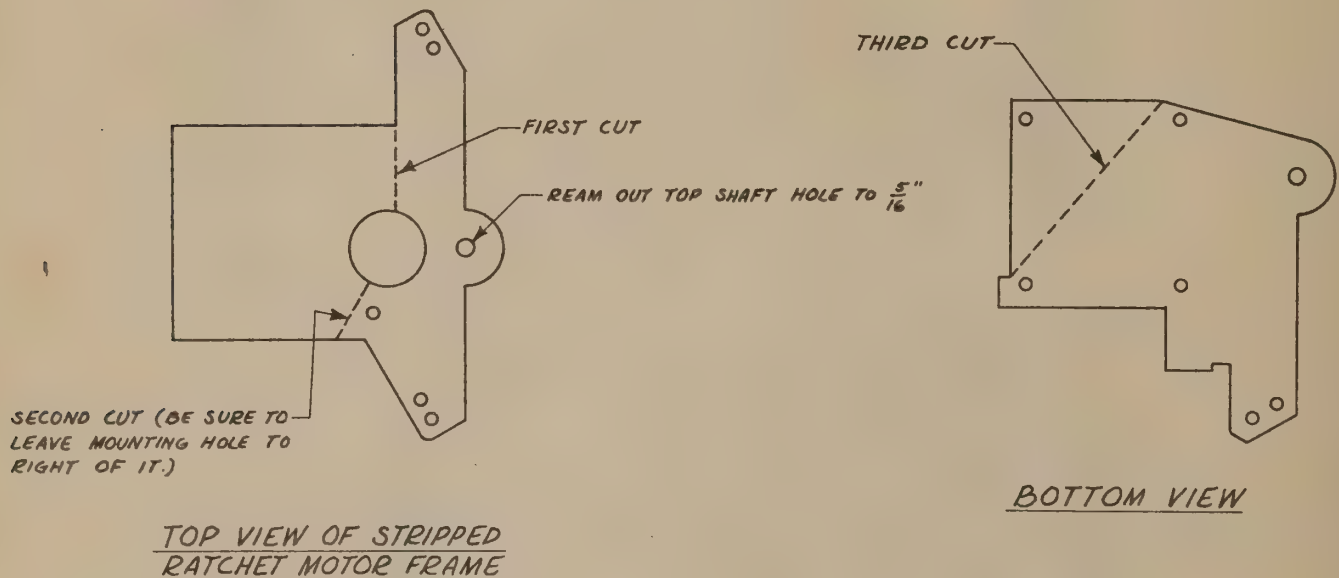


FIGURE 3A

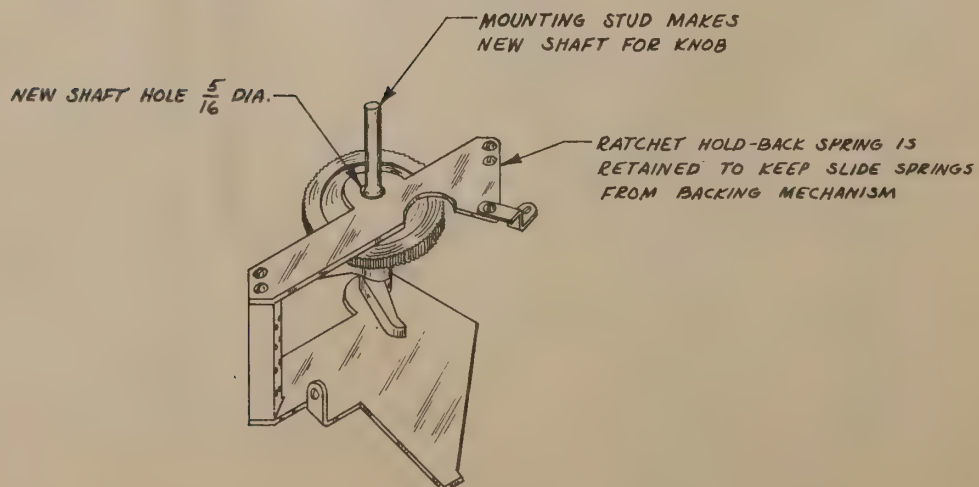


FIGURE 3B-522

CUT TO ALLOW CONTROL SHAFT
TO REACH PANEL


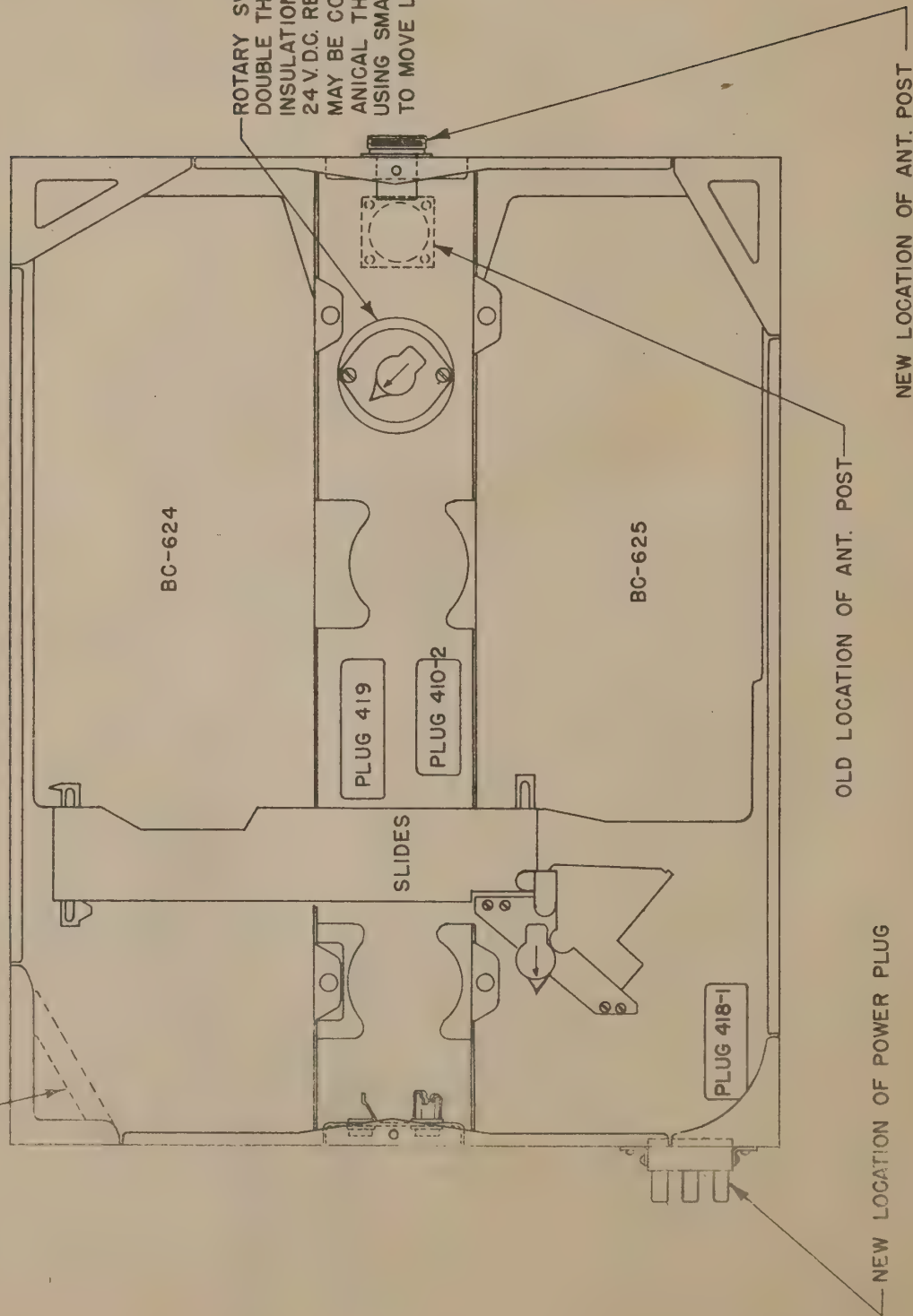


FIGURE 5-522

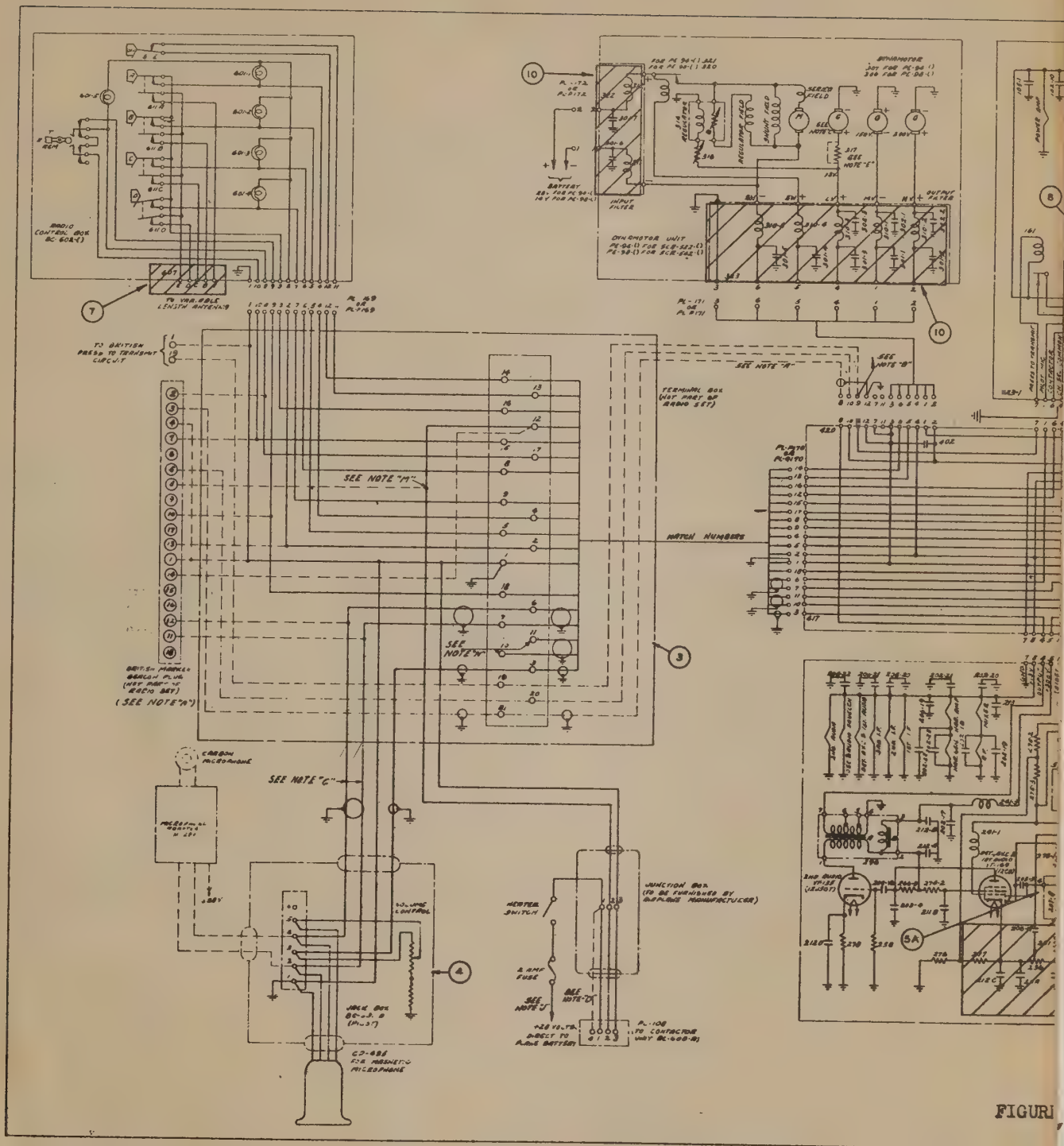

FIGURE

CUT TO ALLOW CONTROL SHAFT
TO REACH PANEL



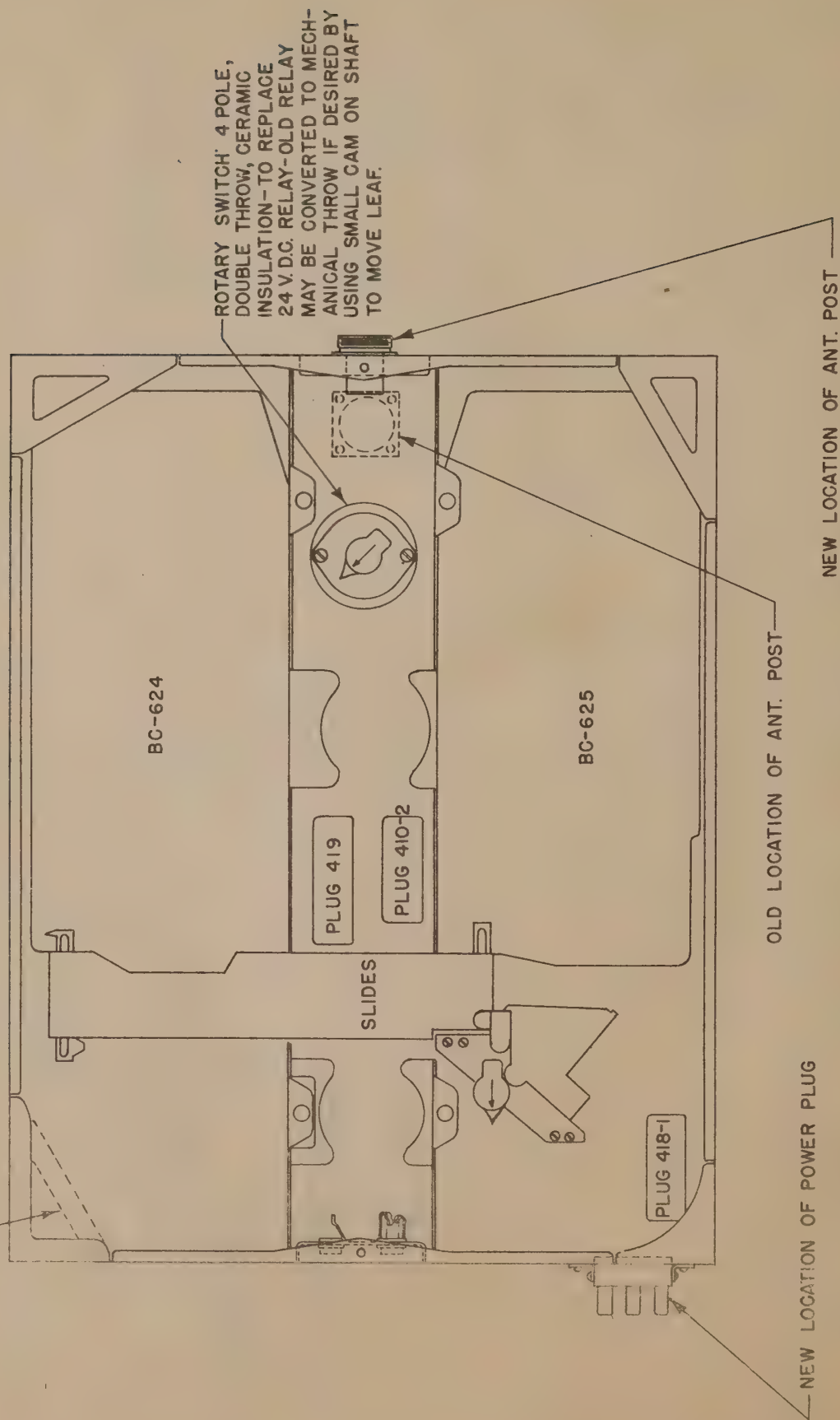


FIGURE 5-522

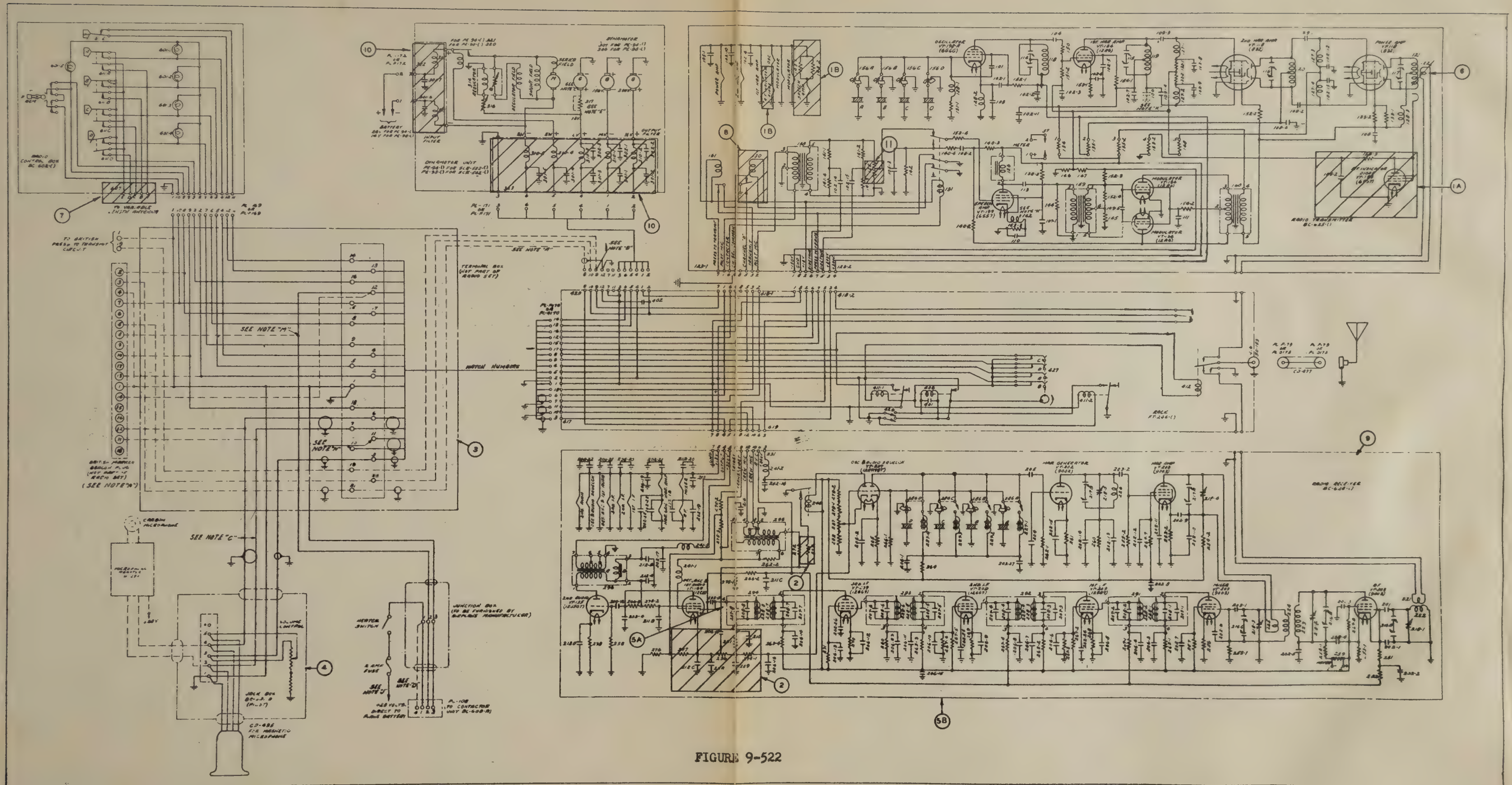

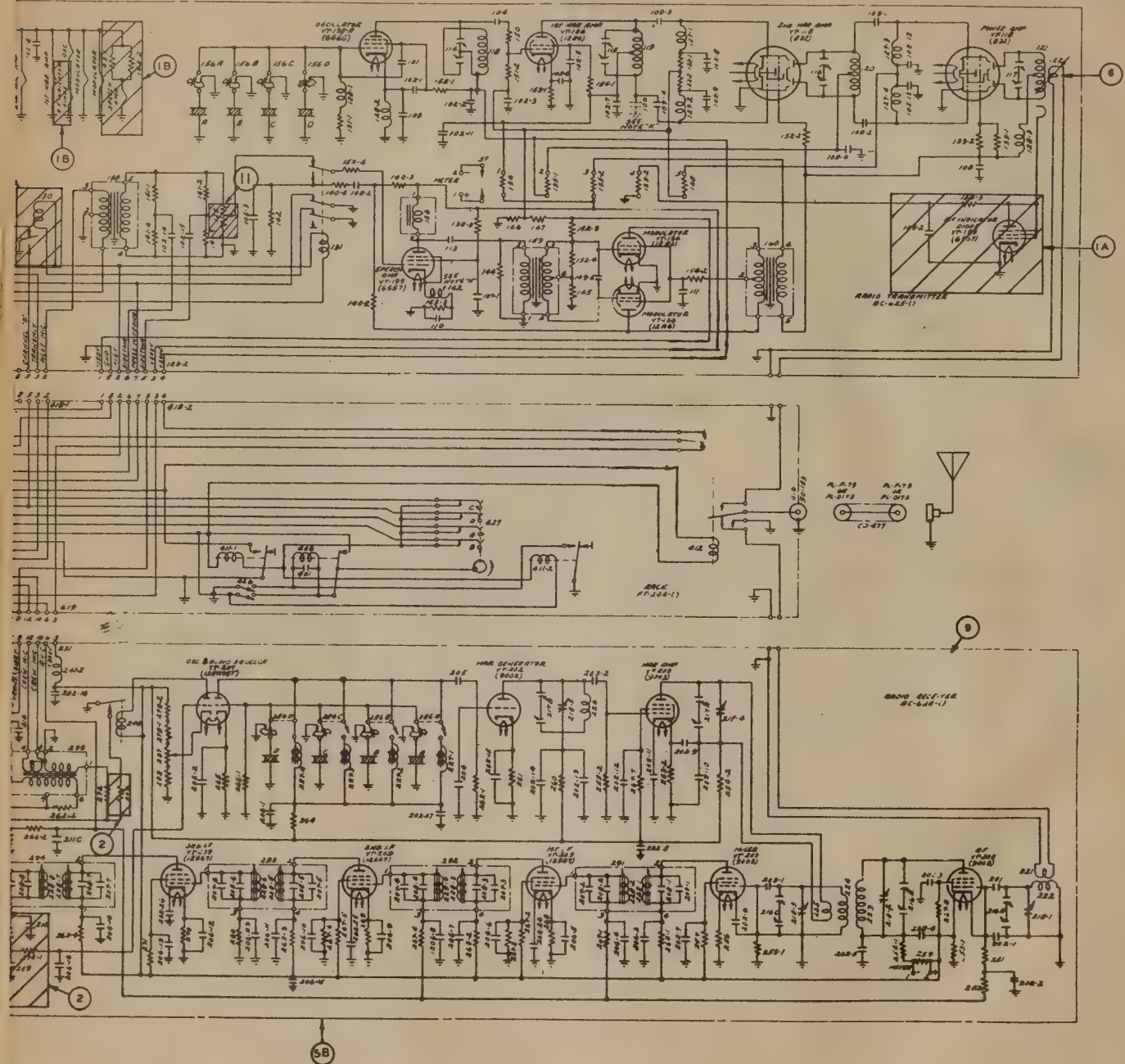

BC625-AM

RCVR

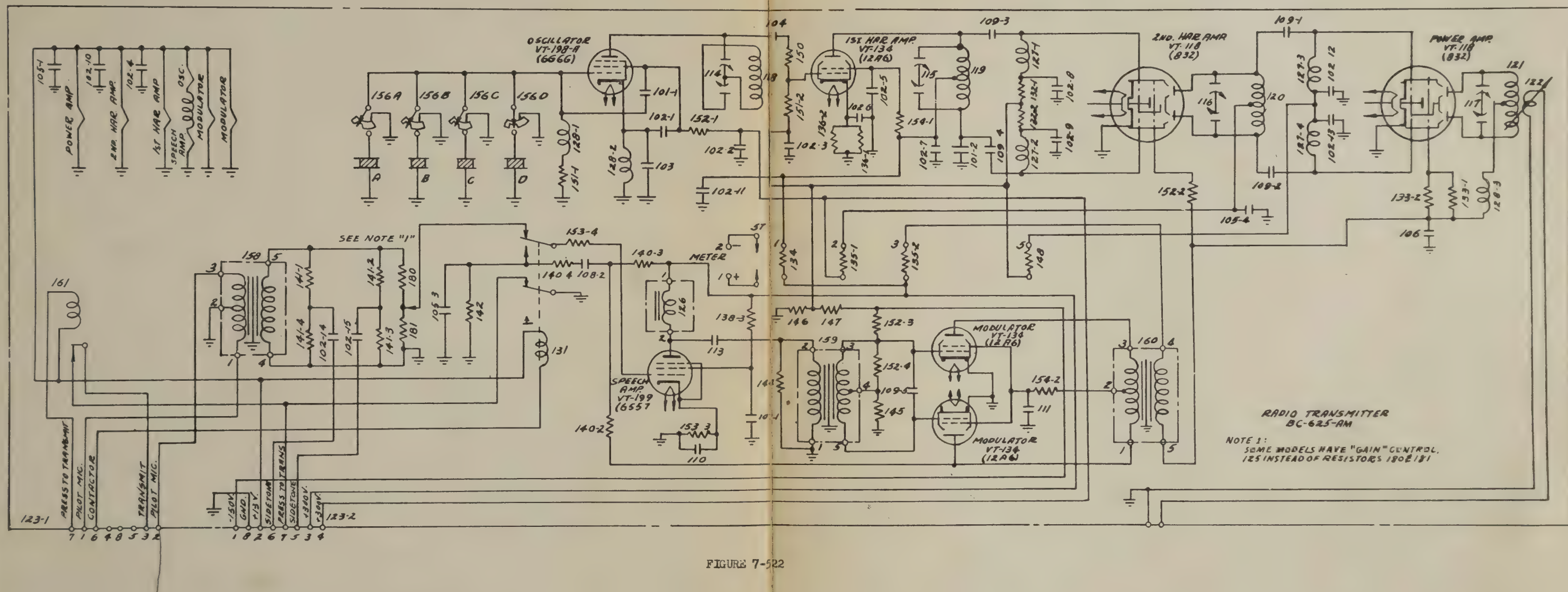


FIGURE 7-522

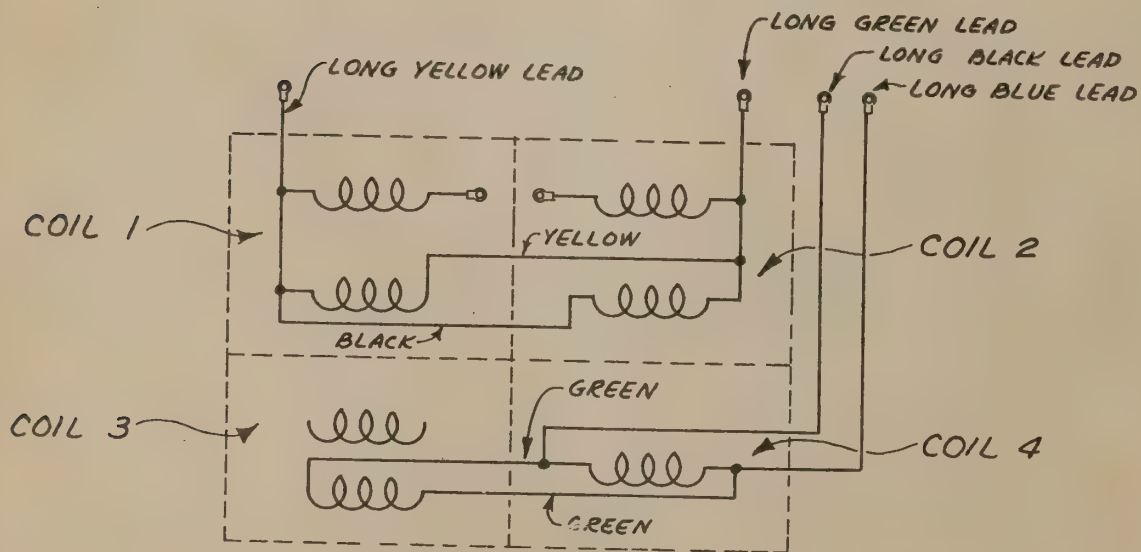
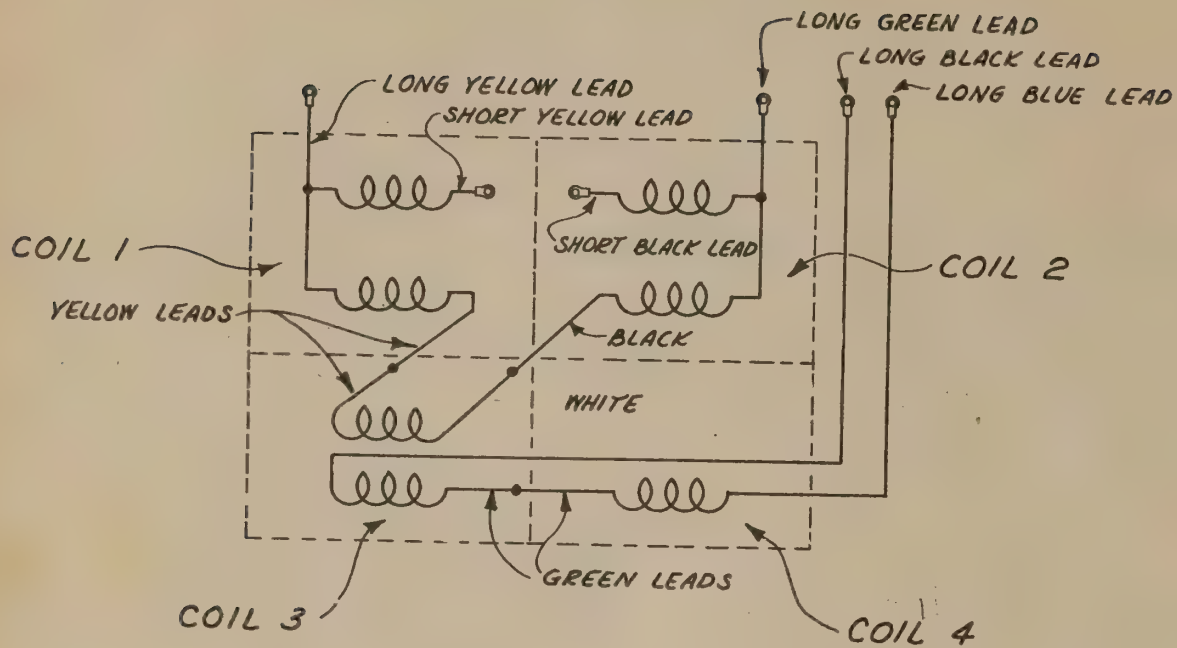


FIGURE 6-522

CRYSTAL FREQUENCY CHART

Carrier f	Crystals	
	Receive	Trans.
100.08	8007.27	5560.0
100.26	8023.64	5570.0
100.44	8040.00	5580.0
100.62	8056.36	5590.0
100.80	8072.73	5600.0
100.98	8089.09	5610.0
101.16	8105.45	5620.0
101.34	8121.82	5630.0
101.52	8138.18	5640.0
101.70	8154.55	5650.0
101.88	8170.91	5660.0
102.06	8187.27	5670.0
102.24	8203.64	5680.0
102.42	8220.00	5690.0
102.60	8236.36	5700.0
102.78	8252.73	5710.0
102.96	8269.09	5720.0
103.14	8285.45	5730.0
103.32	8301.82	5740.0
103.50	8318.18	5750.0
103.68	8334.55	5760.0
103.86	8350.91	5770.0
104.04	8367.27	5780.0
104.22	8383.64	5790.0
104.40	8400.00	5800.0
104.58	8416.36	5810.0
104.76	8432.73	5820.0
104.94	8449.09	5830.0
105.12	8465.45	5840.0
105.30	8481.82	5850.0
105.48	8498.18	5860.0
105.66	8514.55	5870.0

F M
Broadcast

Carrier f	Crystals	
	Receive	Trans.
105.84	8530.91	5880.0
106.02	8547.27	5890.0
106.20	8563.64	5900.0
106.38	8580.00	5910.0
Facsimile 106.56	8596.36	5920.0
106.74	8612.73	5930.0
106.92	8629.09	5940.0
107.10	8645.45	5950.0
107.28	8661.82	5960.0
107.46	8678.18	5970.0
107.64	8694.55	5980.0
107.82	8710.91	5990.0
108.00	8000.00	6000.0
108.18	8015.00	6010.0
108.36	8030.00	6020.0
108.54	8045.00	6030.0
108.72	8060.00	6040.0
108.90	8075.00	6050.0
Air 109.08	8090.00	6060.0
Navigation 109.26	8105.00	6070.0
(Localizer) 109.44	8120.00	6080.0
109.62	8135.00	6090.0
109.80	8150.00	6100.0
109.98	8165.00	6110.0
110.16	8180.00	6120.0
110.34	8195.00	6130.0
110.52	8210.00	6140.0
110.70	8225.00	6150.0
110.88	8240.00	6160.0
111.06	8255.00	6170.0
111.24	8270.00	6180.0
111.42	8285.00	6190.0
111.60	8300.00	6200.0
111.78	8315.00	6210.0
111.96	8330.00	6220.0
112.14	8345.00	6230.0
112.32	8360.00	6240.0
112.50	8375.00	6250.0
Air 112.68	8390.00	6260.0
Navigation 112.86	8405.00	6270.0
(Range) 113.04	8420.00	6280.0
113.22	8435.00	6290.0
113.40	8450.00	6300.0
113.58	8465.00	6310.0
113.76	8480.00	6320.0

CRYSTAL FREQUENCY CHART


Carrier f	Crystals		Carrier f	Crystals	
	Receive	Trans.		Receive	Trans.
113.94	8495.00	6330.0	121.86	8450.77	6770.0
114.12	8510.00	6340.0	122.04	8464.62	6780.0
114.30	8525.00	6350.0	122.22	8478.46	6790.0
114.48	8540.00	6360.0	122.40	8492.31	6800.0
114.66	8555.00	6370.0	122.58	8506.15	6810.0
114.84	8570.00	6380.0	122.76	8520.00	6820.0
115.02	8585.00	6390.0	122.94	8533.85	6830.0
115.20	8600.00	6400.0	123.12	8547.69	6840.0
115.38	8615.00	6410.0	123.30	8561.54	6850.0
115.56	8630.00	6420.0	123.48	8575.38	6860.0
115.74	8645.00	6430.0	123.66	8589.23	6870.0
Air 115.92	8660.00	6440.0	123.84	8603.08	6880.0
Navigation 116.10	8007.69	6450.0	124.02	8001.43	6890.0
116.28	8021.54	6460.0	124.20	8014.29	6900.0
116.46	8035.38	6470.0	124.38	8027.14	6910.0
116.64	8049.23	6480.0	124.56	8040.00	6920.0
116.82	8063.08	6490.0	124.74	8052.86	6930.0
117.00	8076.92	6500.0	124.92	8065.71	6940.0
117.18	8090.77	6510.0	125.10	8078.57	6950.0
117.36	8104.62	6520.0	125.28	8091.43	6960.0
117.54	8118.46	6530.0	125.46	8104.29	6970.0
117.72	8132.31	6540.0	125.64	8117.14	6980.0
117.90	8146.15	6550.0	125.82	8130.00	6990.0
118.08	8160.00	6560.0	126.00	8142.86	7000.0
118.26	8173.85	6570.0	126.18	8155.71	7010.0
118.44	8187.69	6580.0	126.36	8168.57	7020.0
118.62	8201.54	6590.0	126.54	8181.43	7030.0
Aeronautical 118.80	8215.38	6600.0	126.72	8194.29	7040.0
(Airport) 118.98	8229.23	6610.0	126.90	8207.14	7050.0
119.16	8243.08	6620.0	127.08	8220.00	7060.0
119.34	8256.92	6630.0	127.26	8232.86	7070.0
119.52	8270.77	6640.0	127.44	8245.71	7080.0
119.70	8284.62	6650.0	127.62	8258.57	7090.0
119.88	8298.46	6660.0	127.80	8271.43	7100.0
120.06	8312.31	6670.0	127.98	8284.29	7110.0
120.24	8326.15	6680.0	128.16	8297.14	7120.0
120.42	8340.00	6690.0	128.34	8310.00	7130.0
120.60	8353.85	6700.0	128.52	8322.86	7140.0
120.78	8367.69	6710.0	128.70	8335.71	7150.0
120.96	8381.54	6720.0	128.88	8348.57	7160.0
121.14	8395.38	6730.0	129.06	8361.43	7170.0
121.32	8409.23	6740.0	129.24	8374.29	7180.0
121.50	8423.08	6750.0	129.42	8387.14	7190.0
121.68	8436.92	6760.0	129.60	8400.00	7200.0

CRYSTAL FREQUENCY CHART

Carrier f	Crystals	
	Receive	Trans.
129.78	8412.86	7210.0
129.96	8425.71	7220.0
130.14	8438.57	7230.0
130.32	8451.43	7240.0
130.50	8464.29	7250.0
130.68	8477.14	7260.0
130.86	8490.00	7270.0
131.04	8502.86	7280.0
131.22	8515.71	7290.0
131.40	8528.57	7300.0
131.58	8541.43	7310.0
131.76	8554.29	7320.0
131.94	8567.14	7330.0
132.12	8008.00	7340.0
132.30	8020.00	7350.0
132.48	8032.00	7360.0
132.66	8044.00	7370.0
132.84	8056.00	7380.0
133.02	8068.00	7390.0
133.20	8080.00	7400.0
133.38	8092.00	7410.0
133.56	8104.00	7420.0
133.74	8116.00	7430.0
133.92	8128.00	7440.0
134.10	8140.00	7450.0
Aeronautical 134.28	8152.00	7460.0
(Fixed) 134.46	8164.00	7470.0
(Government) 134.64	8176.00	7480.0
134.82	8188.00	7490.0
135.00	8200.00	7500.0
135.18	8212.00	7510.0
135.36	8224.00	7520.0
135.54	8236.00	7530.0
135.72	8248.00	7540.0
135.90	8260.00	7550.0
136.08	8272.00	7560.0
136.26	8284.00	7570.0
136.44	8296.00	7580.0
136.62	8308.00	7590.0
136.80	8320.00	7600.0
136.98	8332.00	7610.0
137.16	8344.00	7620.0
137.34	8356.00	7630.0
137.52	8368.00	7640.0



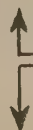

Carrier f	Crystals	
	Receive	Trans.
137.70	8380.00	7650.0
137.88	8392.00	7660.0
138.06	8404.00	7670.0
138.24	8416.00	7680.0
138.42	8428.00*	7690.0
138.60	8440.00	7700.0
138.78	8452.00	7710.0
138.96	8464.00	7720.0
139.14	8476.00	7730.0
139.32	8488.00	7740.0
139.50	8500.00	7750.0
139.68	8512.00	7760.0
139.86	8524.00	7770.0
140.04	8002.50	7780.0
140.22	8013.75	7790.0
140.40	8025.00	7800.0
140.58	8036.25	7810.0
140.76	8047.50	7820.0
140.94	8058.75	7830.0
141.12	8070.00	7840.0
141.30	8081.25	7850.0
141.48	8092.50	7860.0
141.66	8103.75	7870.0
141.84	8115.00	7880.0
142.02	8126.25	7890.0
142.20	8137.50	7900.0
142.38	8148.75	7910.0
142.56	8160.00	7920.0
142.74	8171.25	7930.0
142.92	8182.50	7940.0
143.10	8193.75	7950.0
143.28	8205.00	7960.0
143.46	8216.25	7970.0
143.64	8227.50	7980.0
143.82	8238.75	7990.0
144.00	8250.00	8000.0
144.18	8261.25	8010.0
144.36	8272.50	8020.0
144.54	8283.75	8030.0
144.72	8295.00	8040.0
Amateur 144.90	8306.25	8050.0
145.08	8317.50	8060.0
145.26	8328.75	8070.0
145.44	8340.00	8080.0



Amateur

CRYSTAL FREQUENCY CHART

	Carrier f	Crystals			Carrier f	Crystals	
		Receive	Trans.			Receive	Trans.
Amateur	145.62	8351.25	8090.0		150.84	8167.06	8380.0
	145.80	8362.50	8100.0		151.02	8177.65	8390.0
	145.98	8373.75	8110.0		151.20	8188.24	8400.0
	146.16	8385.00	8120.0		151.38	8198.82	8410.0
	146.34	8396.25	8130.0		151.56	8209.41	8420.0
	146.52	8407.50	8140.0		151.74	8220.00	8430.0
	146.70	8418.75	8150.0		151.92	8230.59	8440.0
	146.88	8430.00	8160.0		152.10	8241.18	8450.0
	147.06	8441.25	8170.0		152.28	8251.76	8460.0
	147.24	8452.50	8180.0		152.46	8262.35	8470.0
	147.42	8463.75	8190.0		152.64	8272.94	8480.0
	147.60	8475.00	8200.0		Railroad. 152.82	8283.53	8490.0
	147.78	8486.25	8210.0		Press Relay. 153.00	8294.12	8500.0
	147.96	8497.50	8220.0		Urban Telephone. 153.18	8304.71	8510.0
	148.14	8008.24	8230.0		153.36	8315.29	8520.0
	148.32	8018.82	8240.0		Police. 153.54	8325.88	8530.0
	148.50	8029.41	8250.0		Fire 153.72	8336.47	8540.0
	148.68	8040.00	8260.0		Maritime 153.90	8347.06	8550.0
Government (Fixed) (Aero)	148.86	8050.59	8270.0		Geophysical 154.08	8357.65	8560.0
	149.04	8061.18	8280.0		154.26	8368.24	8570.0
	149.22	8071.76	8290.0		Experi- mental. 154.44	8378.82	8580.0
	149.40	8082.35	8300.0		154.62	8389.41	8590.0
	149.58	8092.94	8310.0		154.80	8400.00	8600.0
	149.76	8103.53	8320.0		154.98	8410.59	8610.0
	149.94	8114.12	8330.0		155.16	8421.18	8620.0
	150.12	8124.71	8340.0		155.34	8431.76	8630.0
	150.30	8135.29	8350.0		155.52	8442.35	8640.0
	150.48	8145.88	8360.0		155.70	8452.94	8650.0
	150.66	8156.47	8370.0		155.88	8463.53	8660.0

MODIFICATIONS OF MAJOR ASSEMBLIES OF RADIO SET SCR-522-A

Previous Model Number	Latest Model Number	Modification
Radio Transmitter BC-625-A	Radio Transmitter BC-625-A (modified)	1. R.F. indicator diode removed; filament circuits rewired.
Radio Transmitter BC-625-A	Radio Transmitter BC-625-AM	1. Slow release relay, 130, removed.
Radio Receiver BC-624-A	Radio Receiver BC-624-AM	1. Field modified to include tube JAN-12H6, noise suppressor and AVC delay. 2. Factory modified to include tube JAN-12H6, noise suppressor and AVC delay.
	BC-624-C	1. Tube JAN-12AH7GT added as first audio and AVC delay. 2. Squelch audio tube JAN-12AH7GT now furnishes squelch bias to the grid of the first audio tube JAN-12AH7GT instead of operating the squelch relay. 3. Third audio tube JAN-12A6 added. 4. Tube JAN-12C8 changed to AVC and second audio circuit. 5. New output transformer added.

**CHANGEOVER TO 110 VAC POWER SUPPLY
INSTRUCTIONS FOR BC-348-E-M-O-P-S SERIES
USE SCHEMATICS 1, 2 AND 3**

1. Lift the center lead from resistor 501 A-B and connect to lead coming from dynamotor terminal 3.
2. Run a lead from ground lug to pin 1 of tube A
3. Run lead from pin 7 of C to pin 7 of B.
4. Lift lead from pin 2 of C and solder to pin 7 of C.
5. Solder pin 1 and 2 of C together.
6. Place a jumper between pins 1 and 2 of tube B.
Now go to the R. F. shelf and using Schematic 3
7. Place a jumper between pin 2 and 1 of tube D.
8. Place jumper between pins 1 and 2 of tube F and snip out the old lead attached to pin 2 of tube F.
9. Run jumper between pin 7 of D and pin 7 of E.
10. Lift lead from contact 1 of switch 107, section 1, front. Solder to pin 7 of tube C.
11. Put a jumper across resistor 503 which is behind the front panel of the receiver. Take off the dial cover and change the dial lights wiring from series to parallel.

**BC-348-J-Q-N
USE SCHEMATICS 4 AND 5**

1. Snip out resistor 84 which connects pin 2 of socket D to pin 1 of the terminal board. Connect pin 1 to pin 2.
2. Run a lead from pin 7 of socket D to the terminal board pin that resistor 84 was taken from.
3. Put jumper from pin 7 socket C to pin 7 socket B.

4. Solder jumper between pin 8 and pin 1 of socket B.
5. Run lead from pin 1 to pin 3 of terminal board 126.
6. Run a lead from pin 2 of socket E to pin 7 of socket F and pin 7 of socket G, first removing the leads originally on these last two.
7. Connect pin 7 to pin 8 of socket E.
8. Connect pin 2 of socket F to ground lug just below it.
9. Trace down and snip off the block lead from the dial light to the AVC-OFF-MC switch 169. Solder lead removed from switch to pin 7 of socket B.
10. Change the dial lights to parallel in place of the series wiring they now have and short out the sixty ohm resistor in series with the dimmer control.

Diagram 6 is included to show proper connections for 110 VAC operation. The power pack is built on the dynamotor mounting base after it has been completely stripped of its original parts complement. A few of the power transformers that will fit into the small space are listed on the drawing. On testing the power pack make sure the plate voltage is not over 300 volts or so. If the voltage is too high remove the input condensor. No attempt to list the numbers of chokes has been made, for the amateurs junk box usually contains a small one that will do. Use a GT tube if possible to conserve space.

Noticé that the B- is put into the receiver through a filter choke. Don't make this connection to ground. Be careful that the dial lights are fed from the 6 VAC filament source. If left on the on-off switch it will short the 115 VAC.

VT-91 1 DET.

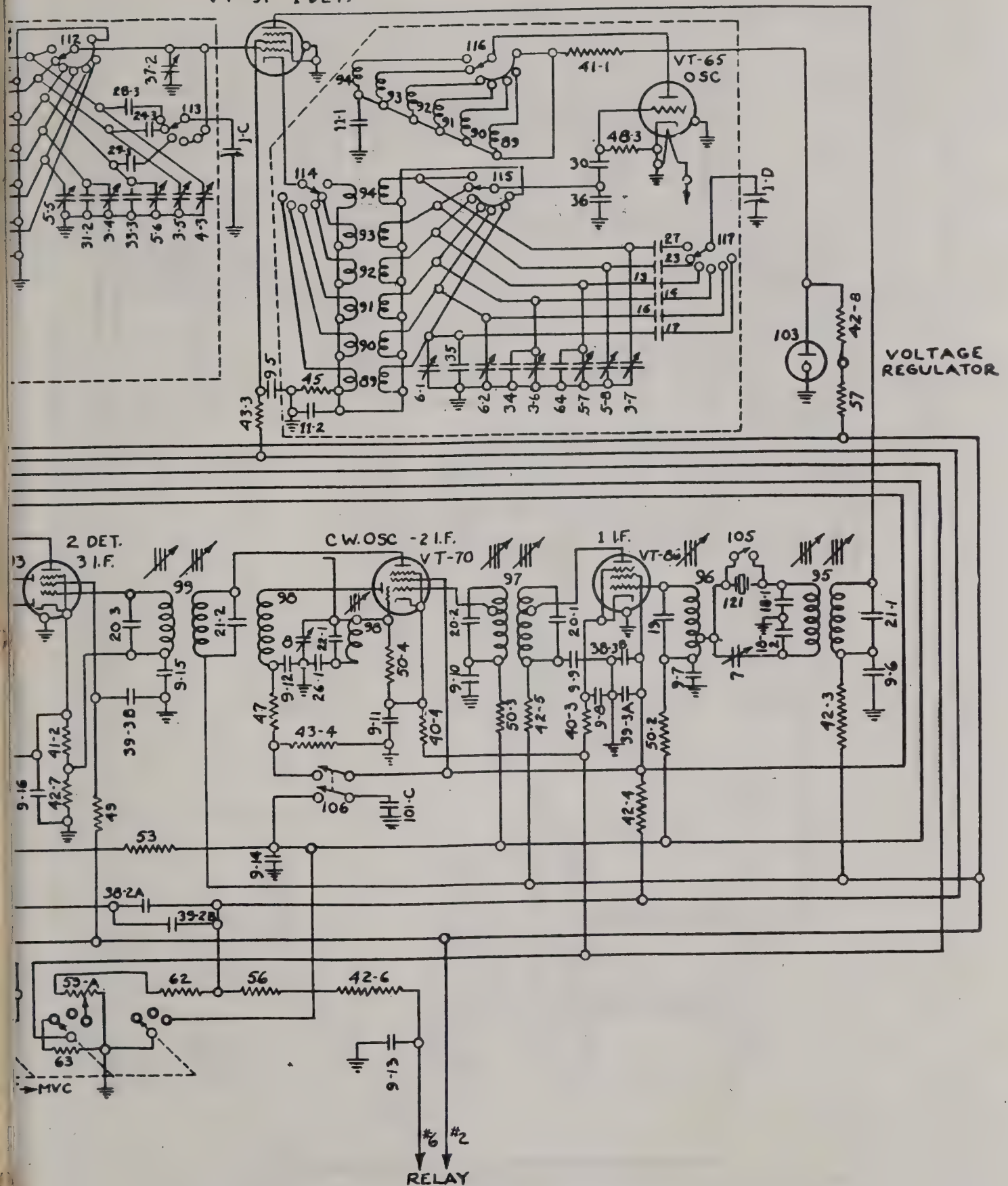


FIGURE 1-348

Radio Receiver BC-348-E, BC-348-M or BC-348-P, Schematic Circuit Diagram

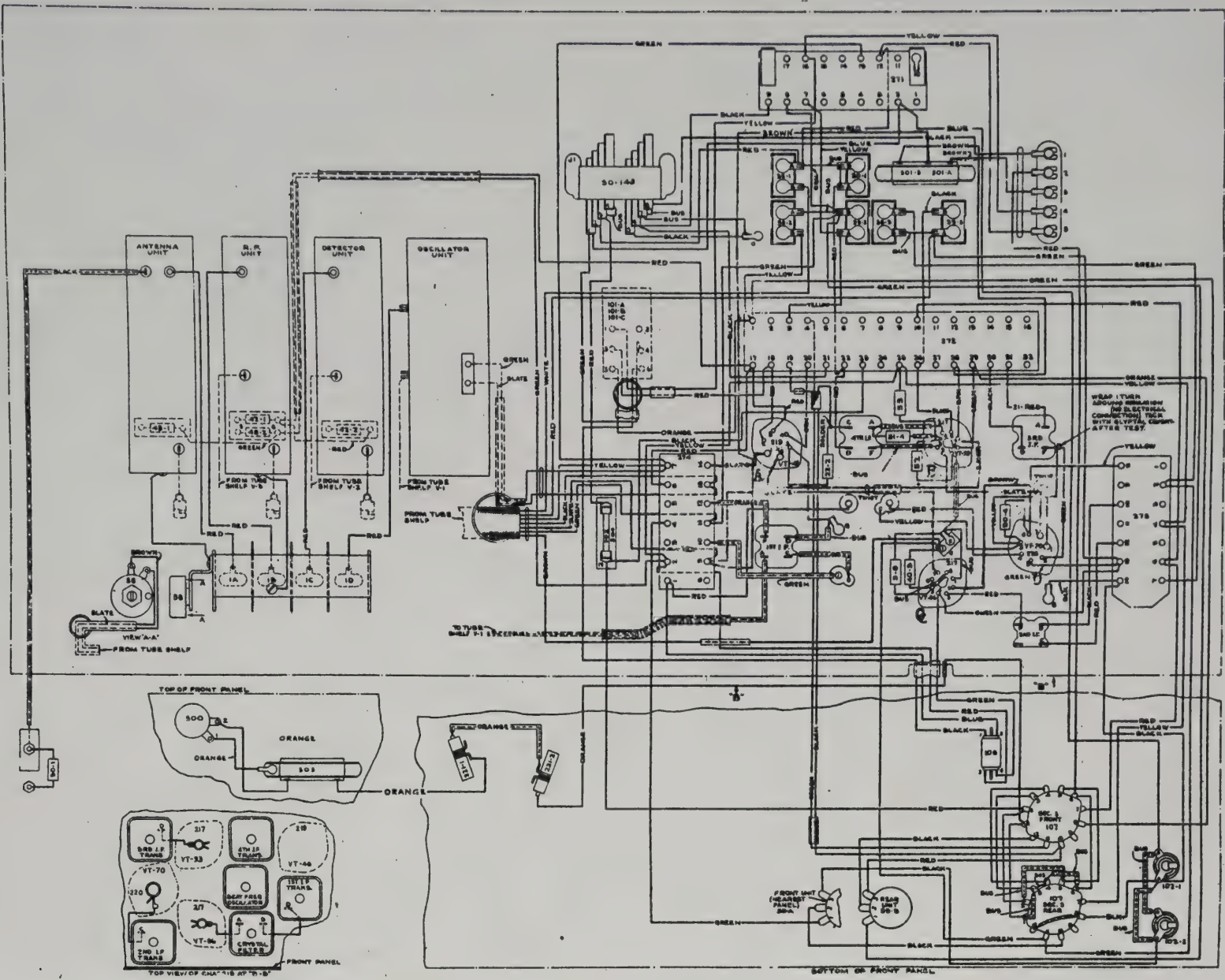


FIGURE 2-348

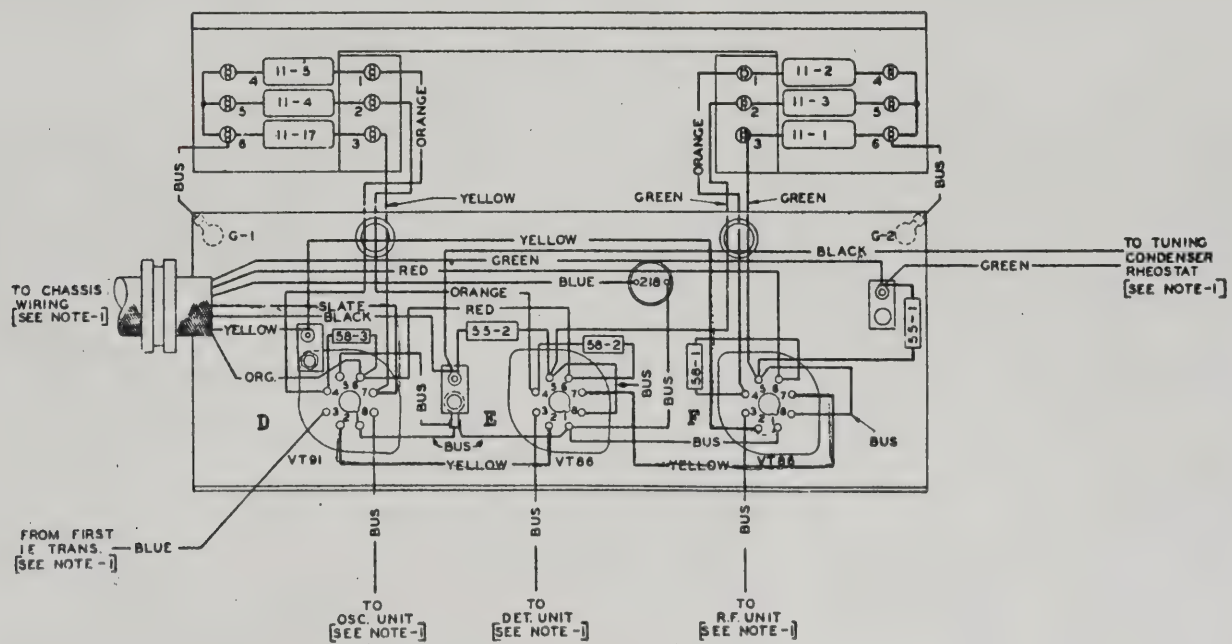


FIGURE 3-348

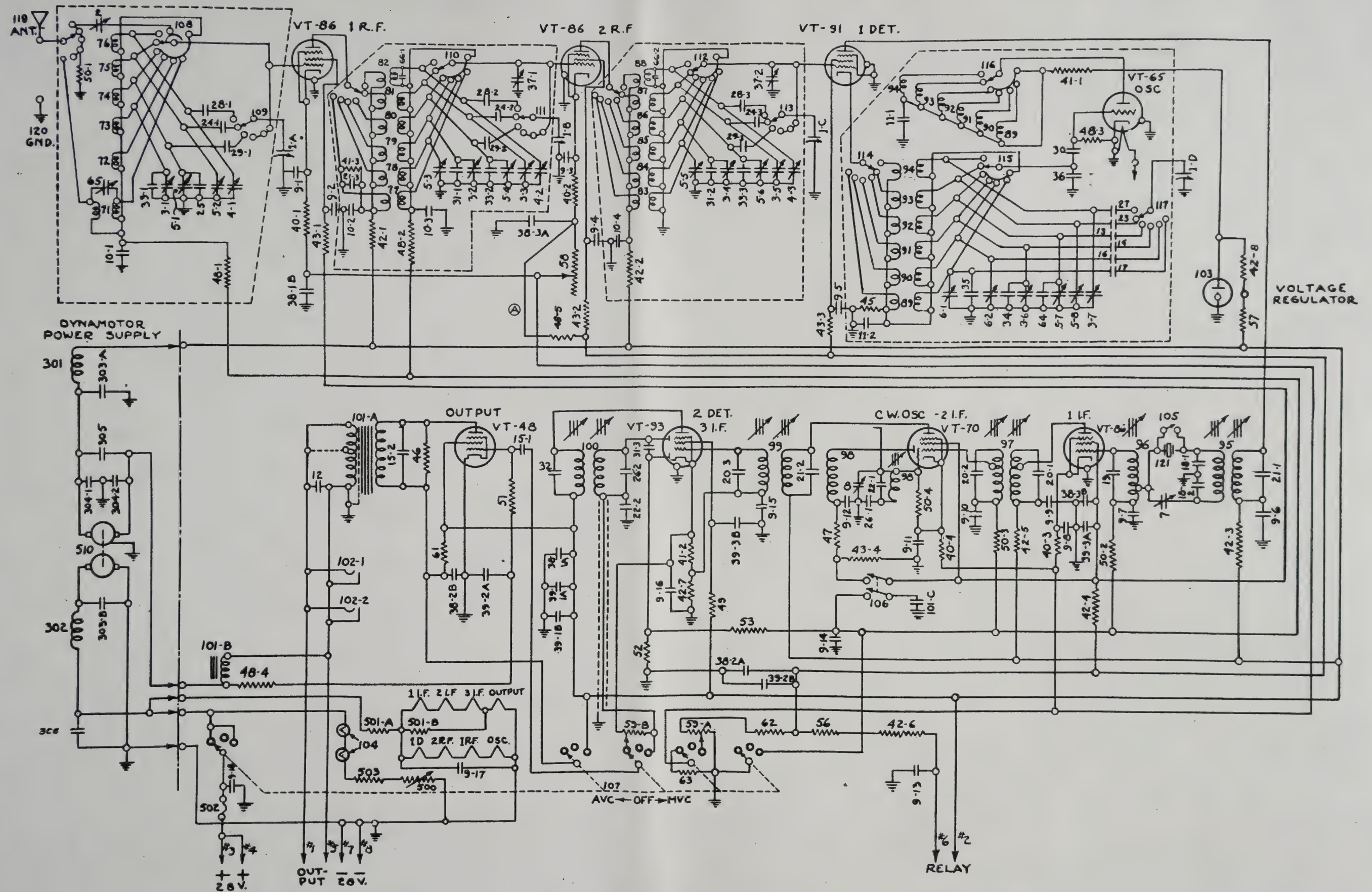


FIGURE 1-348

Radio Receiver BC-348-E, BC-348-M or BC-348-P, Schematic Circuit Diagram

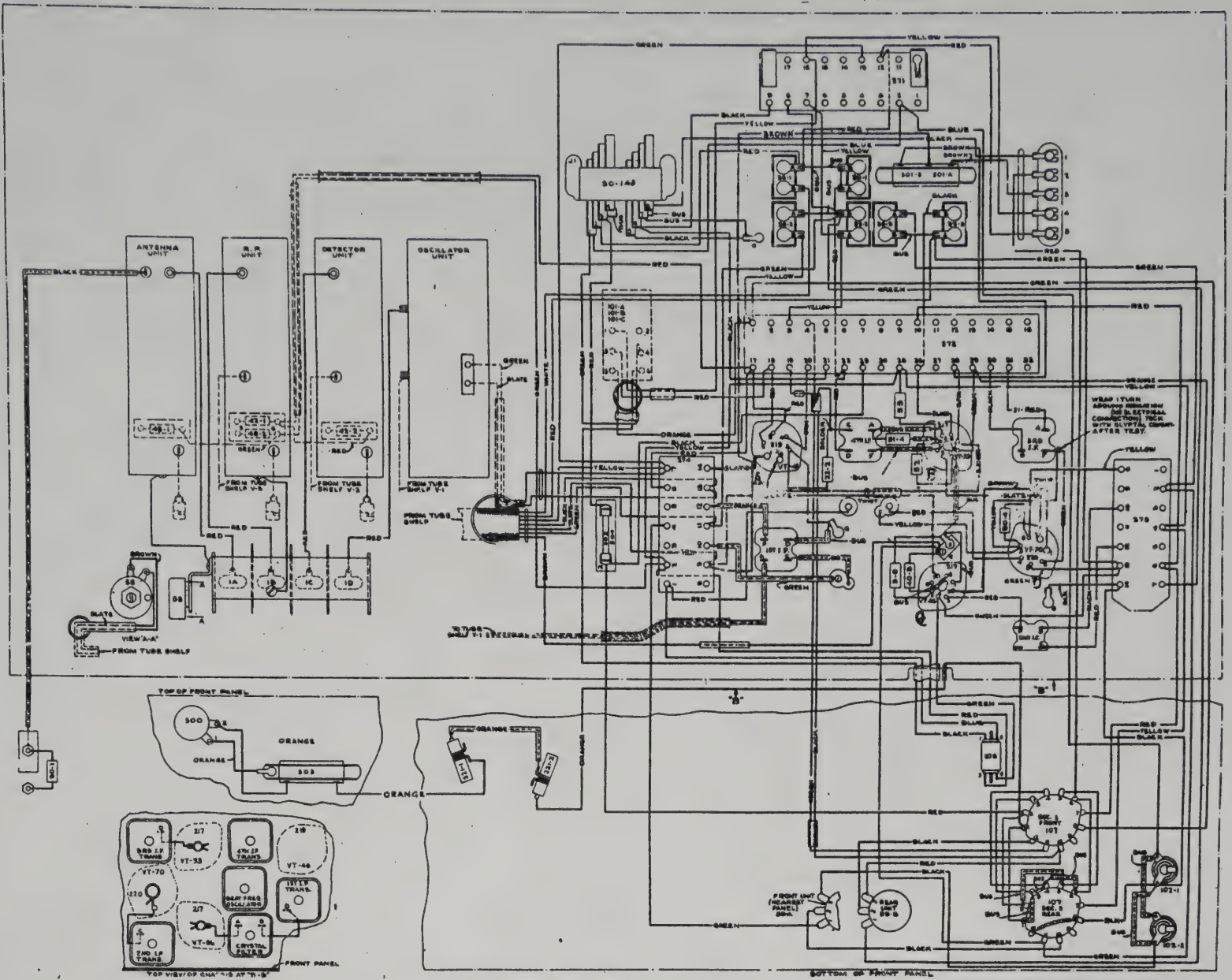


FIGURE 2-348

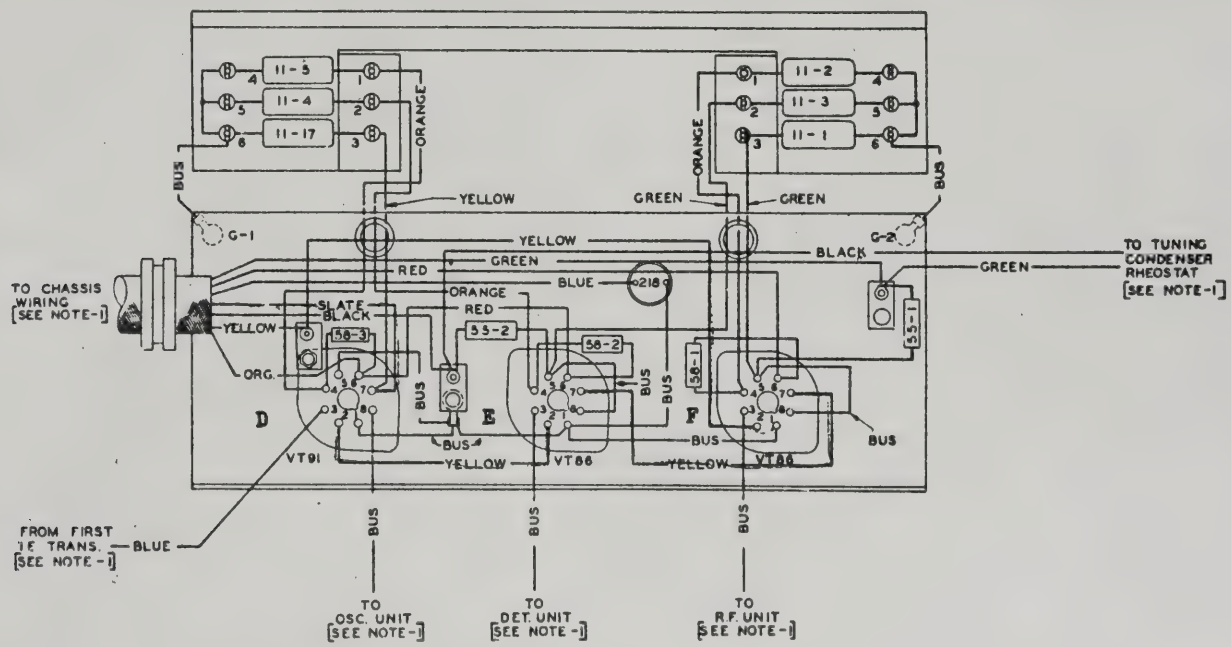


FIGURE 3-348


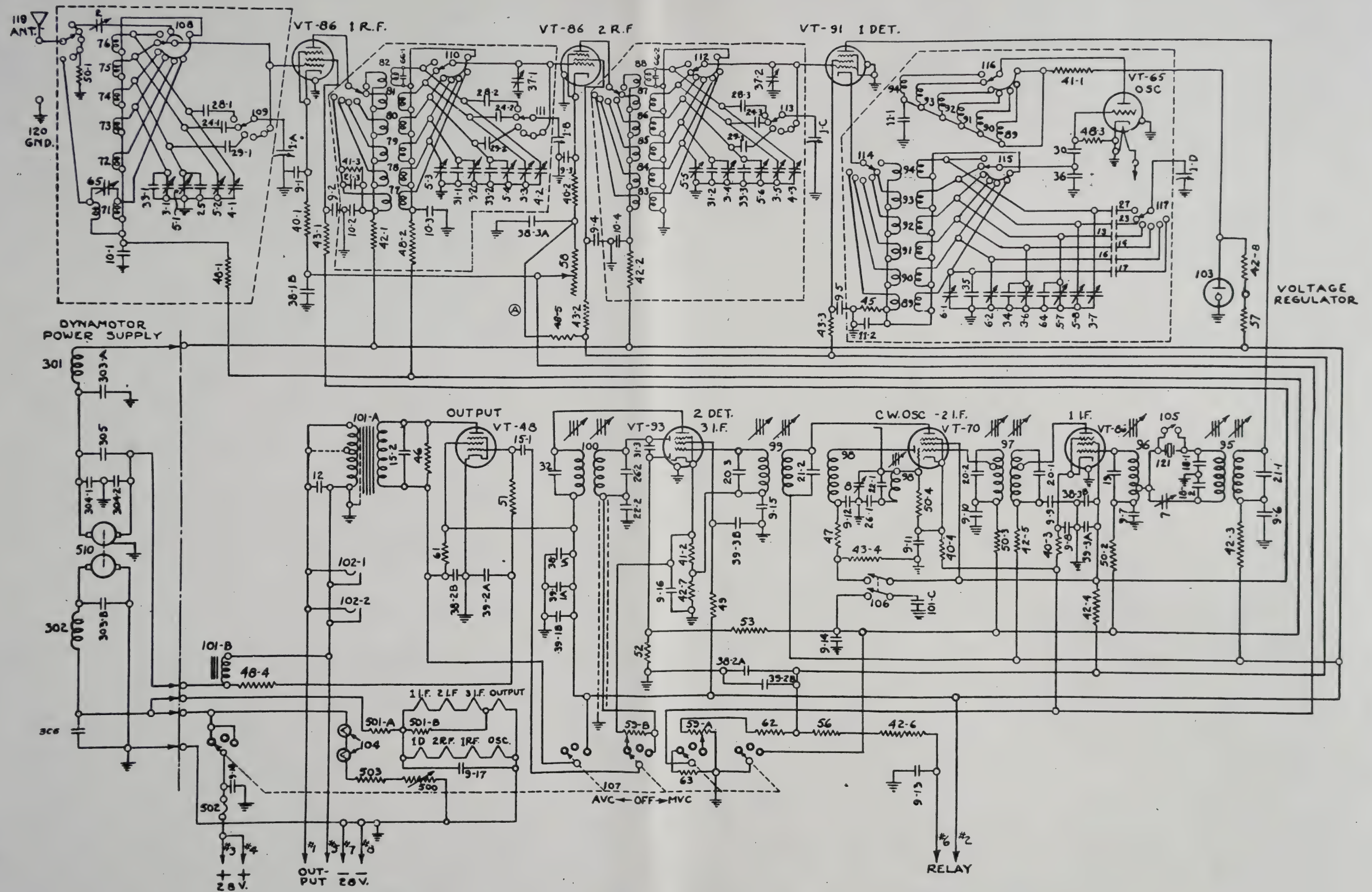
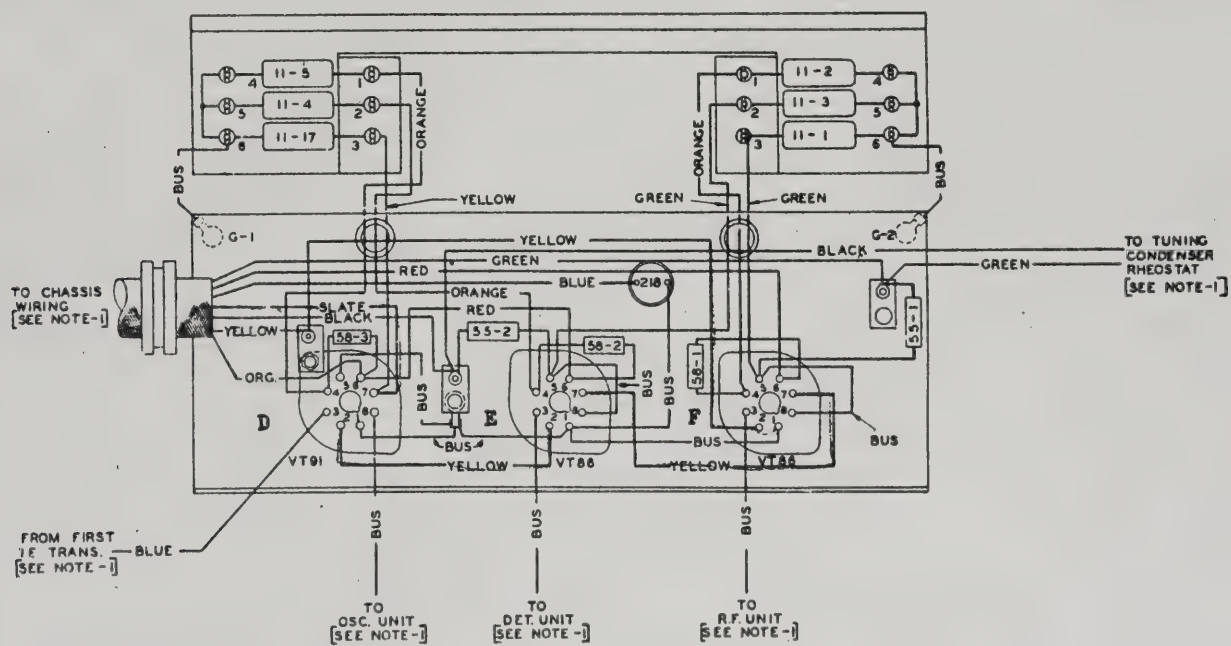


FIGURE 1-348

Radio Receiver BC-348-E, BC-348-M or BC-348-P, Schematic Circuit Diagram

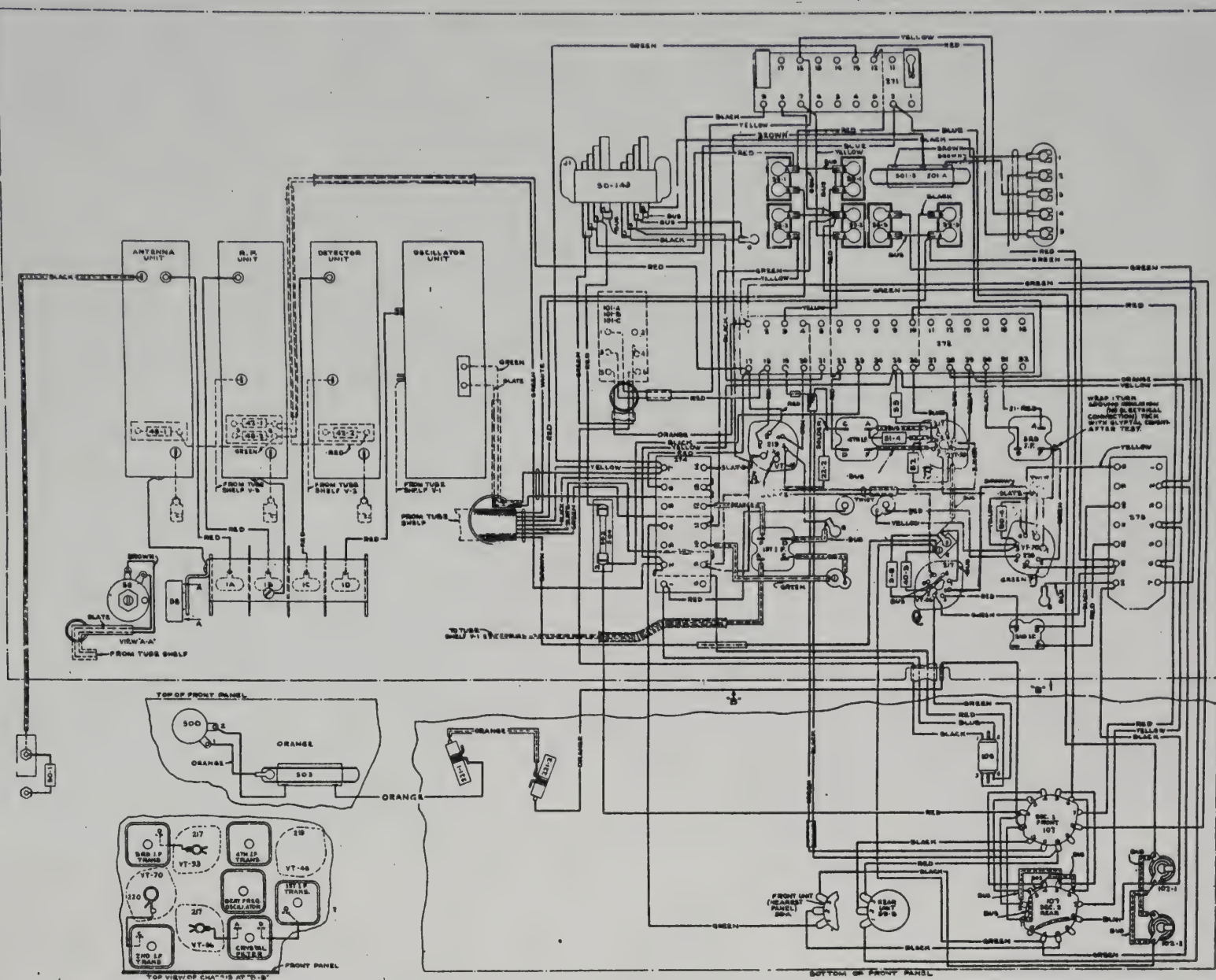

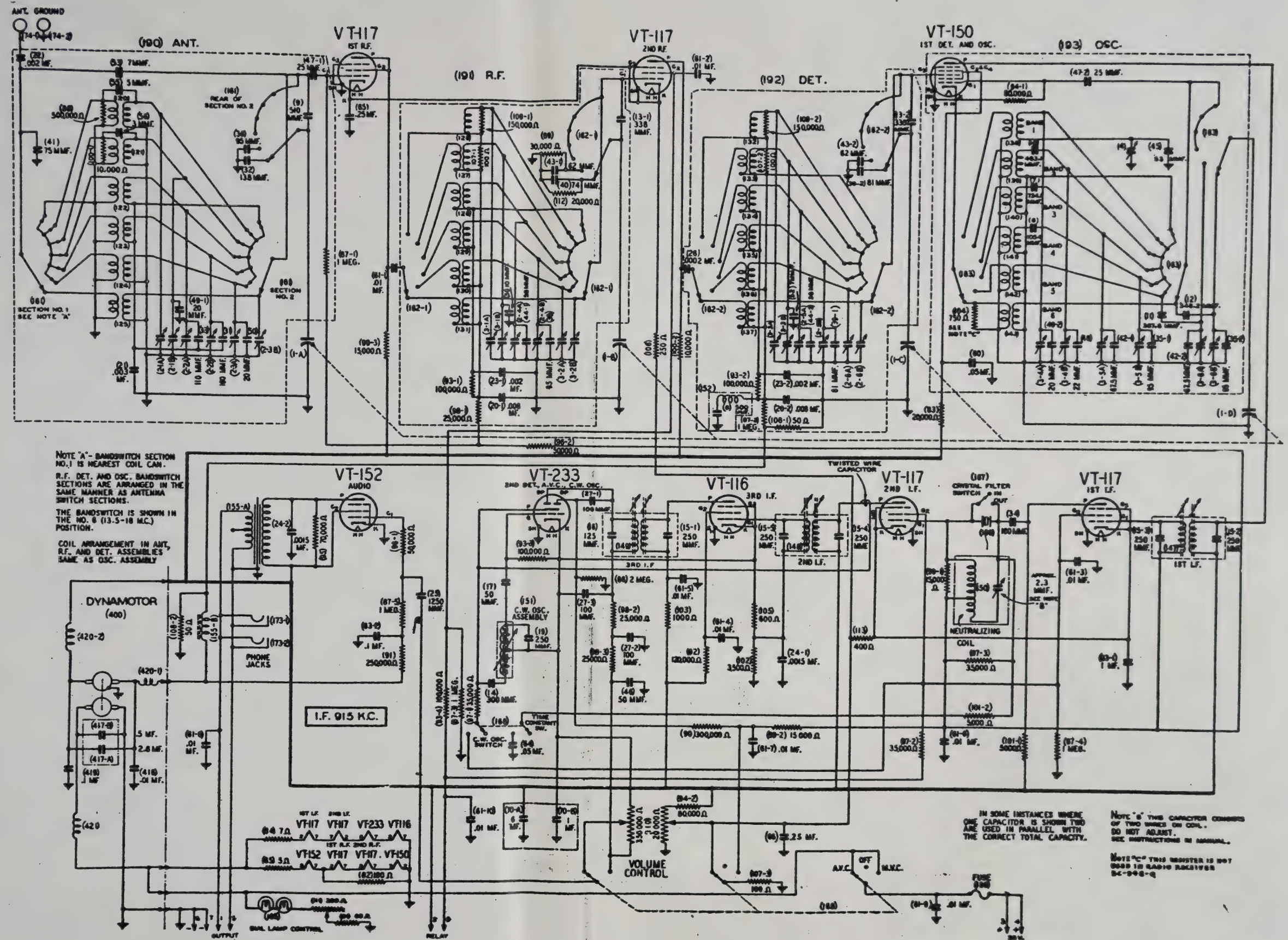


FIGURE 4-348

Radio Receiver BC-348-J, Schematic Diagram

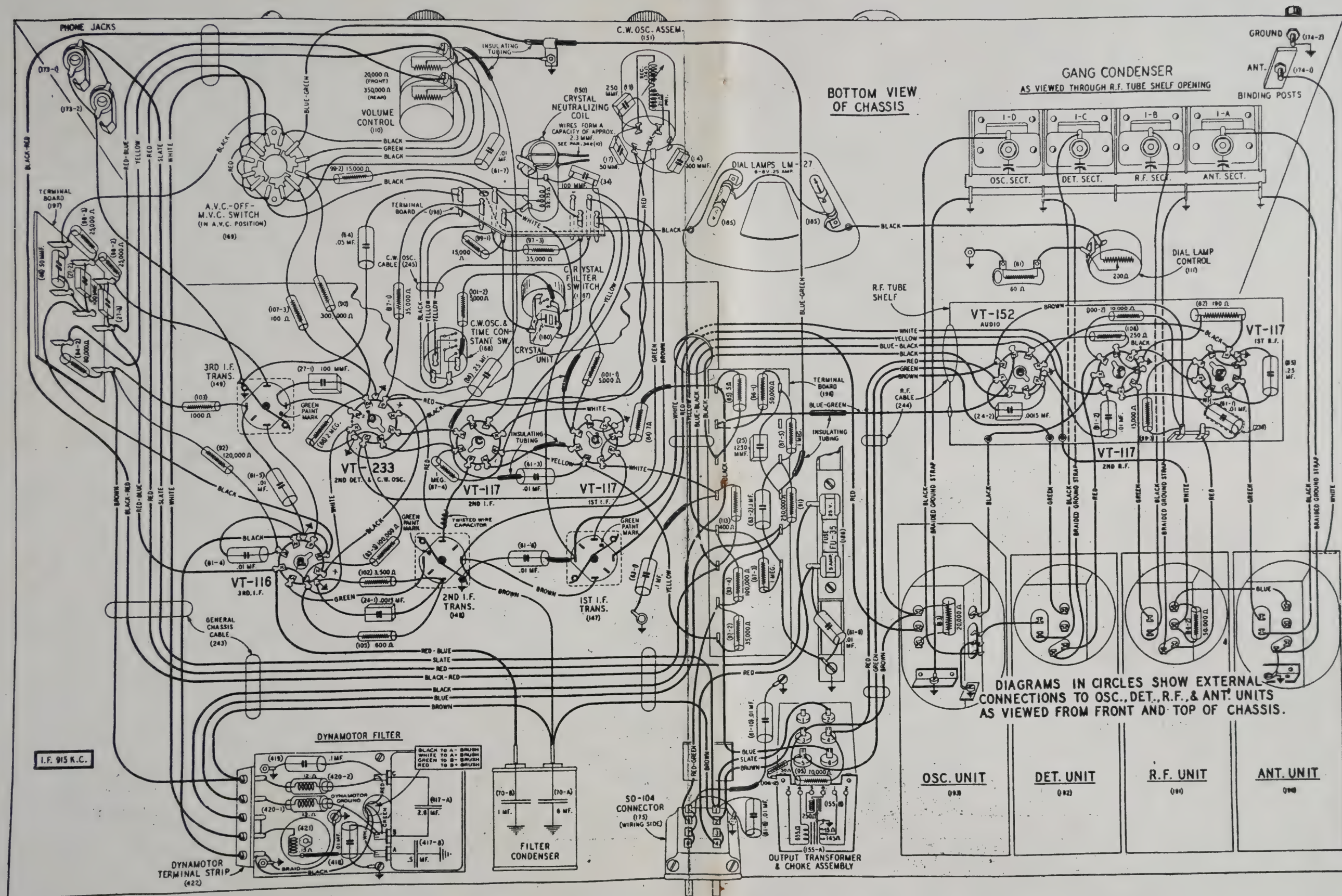


FIGURE 5 -348.
Radio Receiver BC-348-J, Wiring Diagram of Chassis

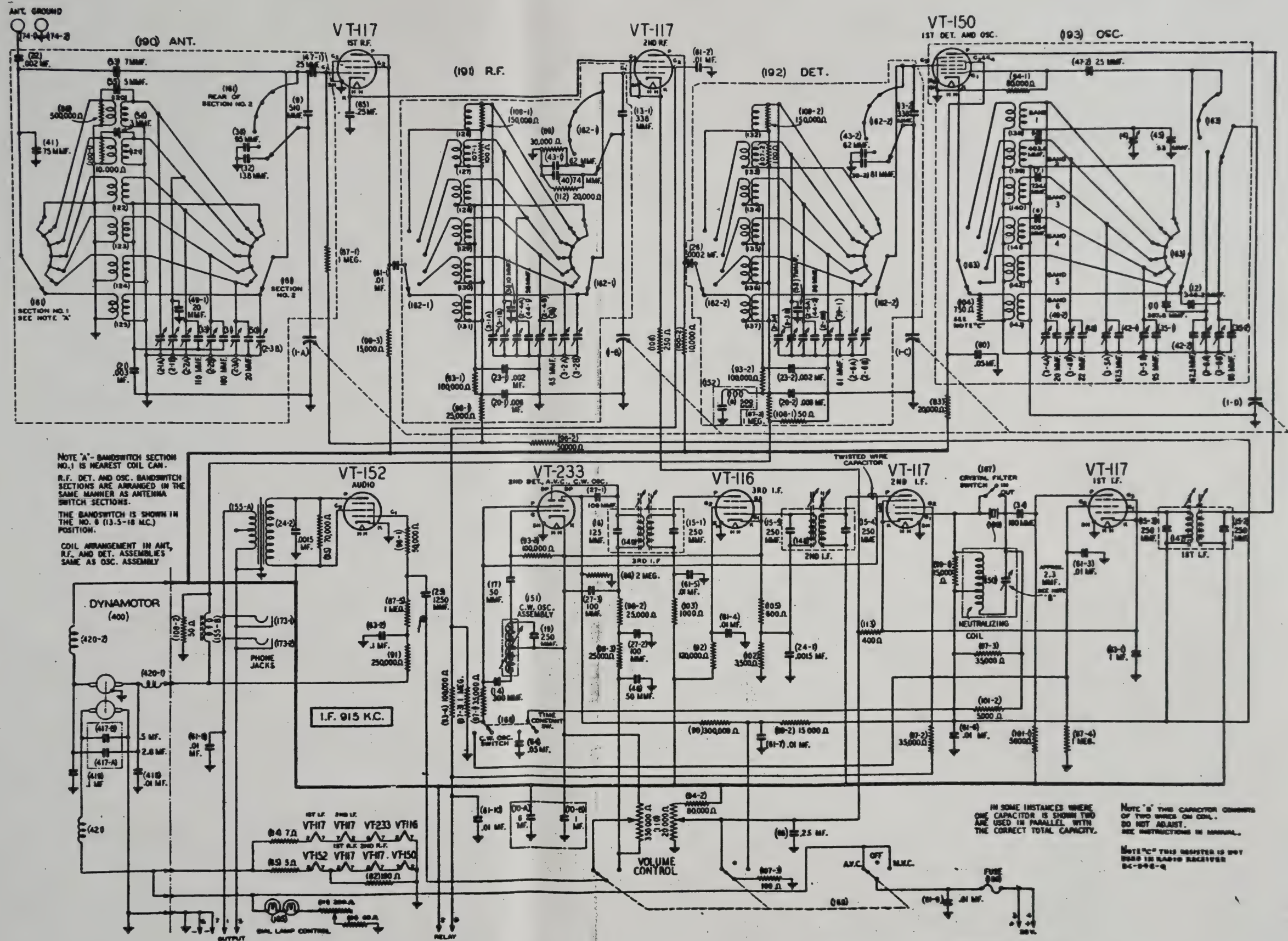


FIGURE 4-348
Radio Receiver BC-348-J, Schematic Diagram

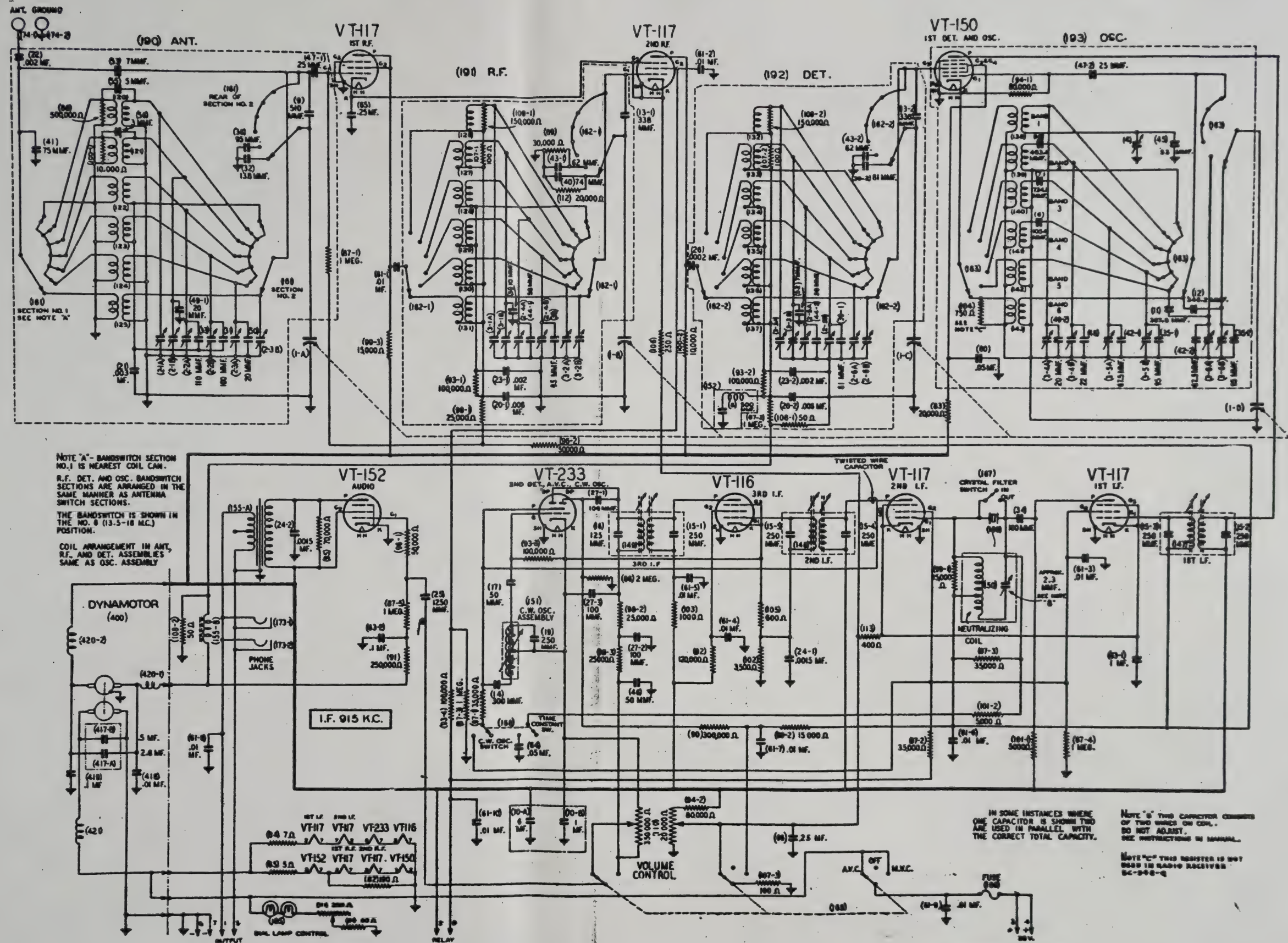


FIGURE 4-348
Radio Receiver BC-348-J, Schematic Diagram

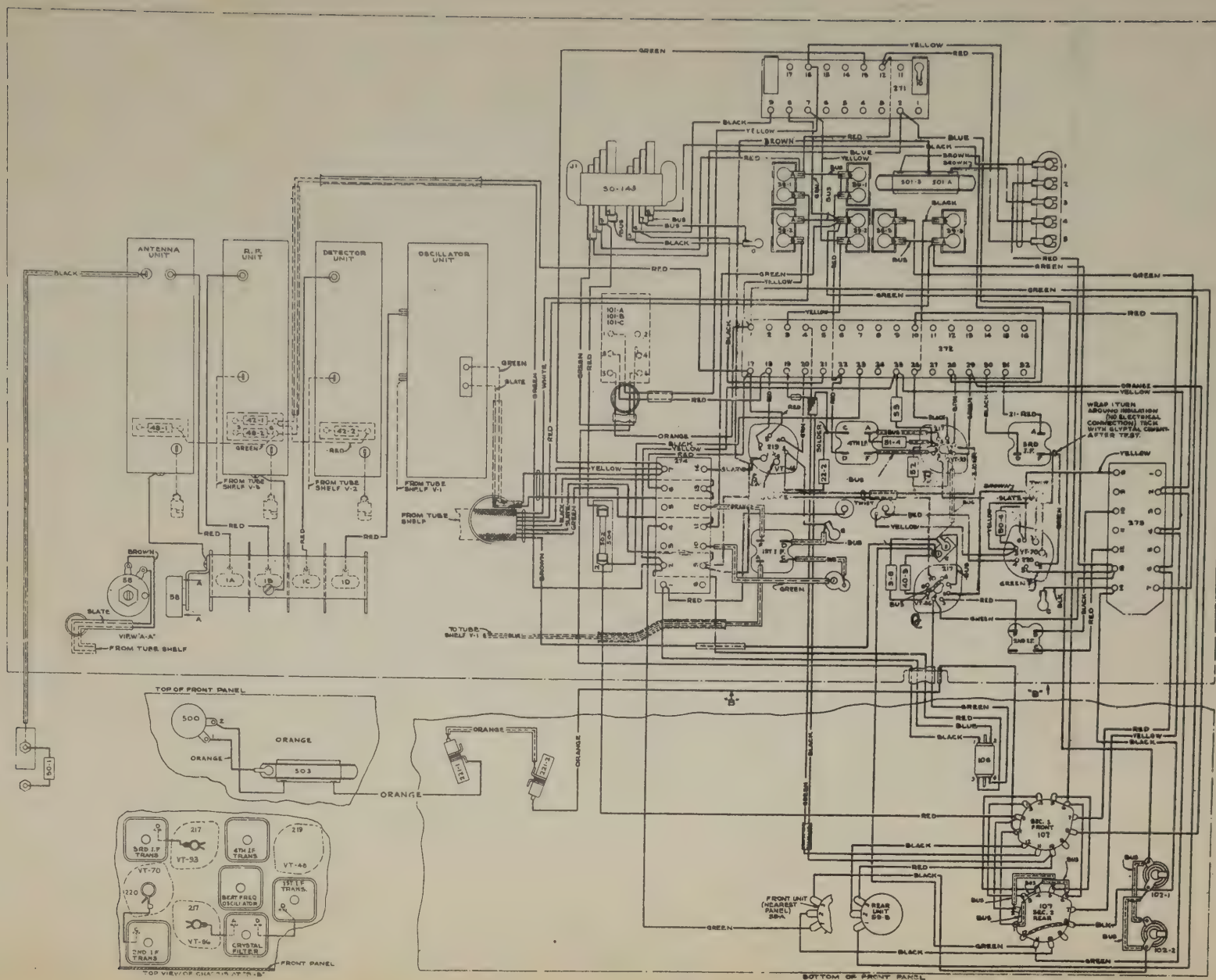


FIGURE 2-348

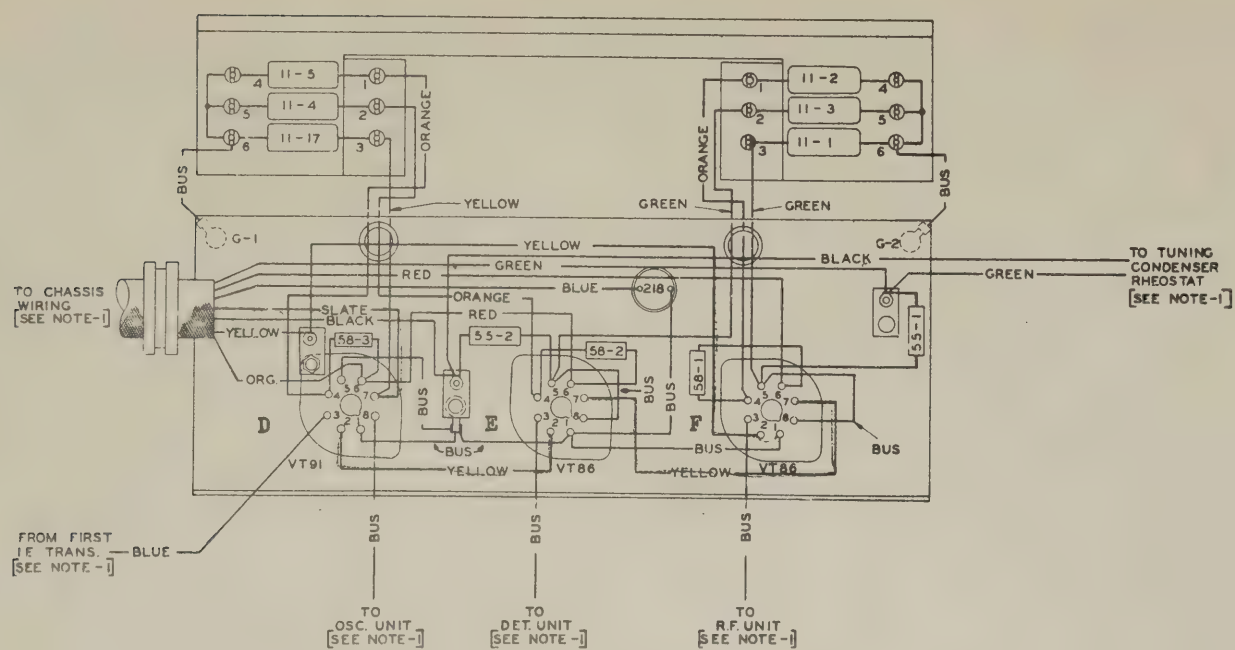


FIGURE 3-348

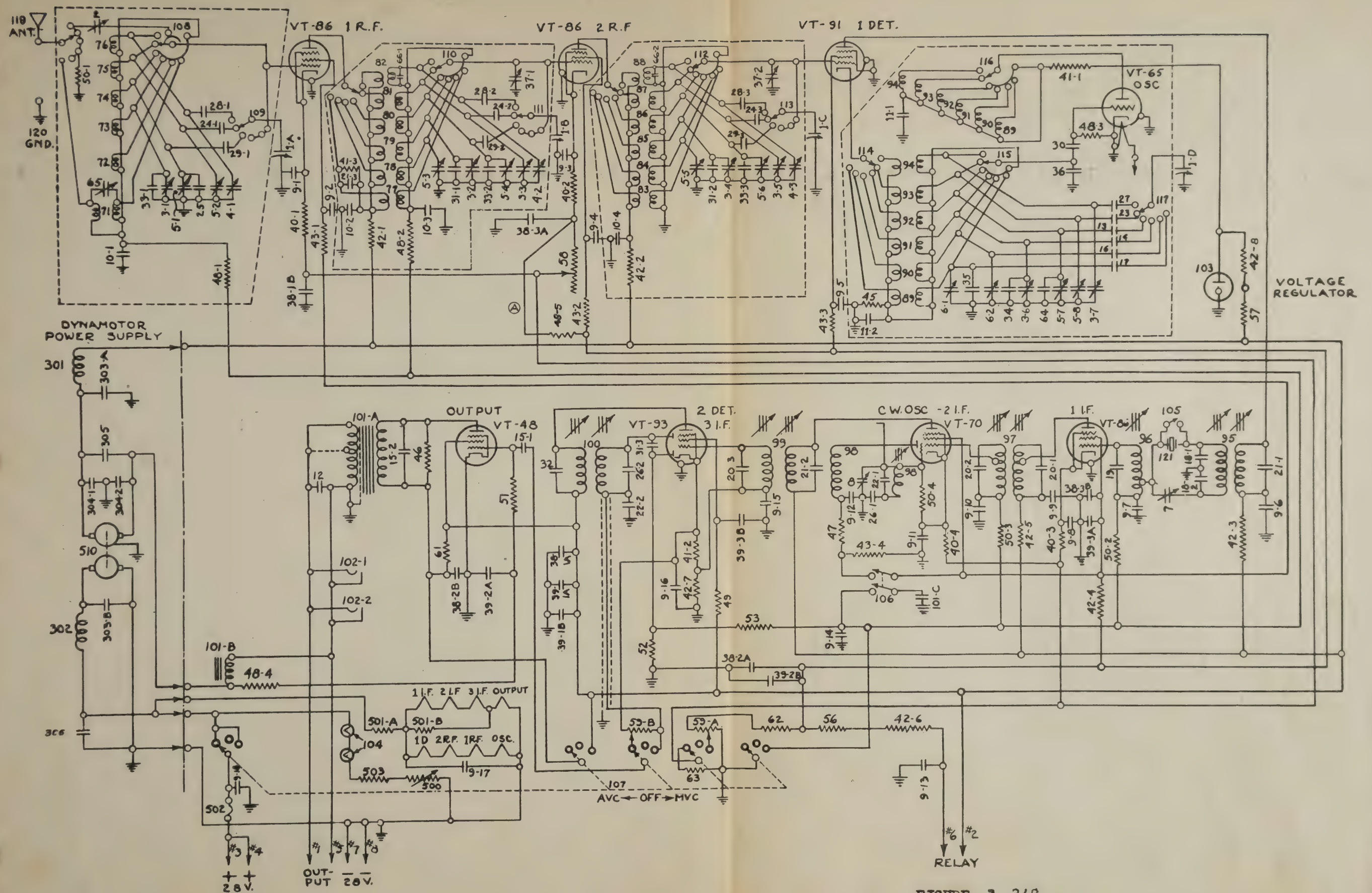


FIGURE 1-348

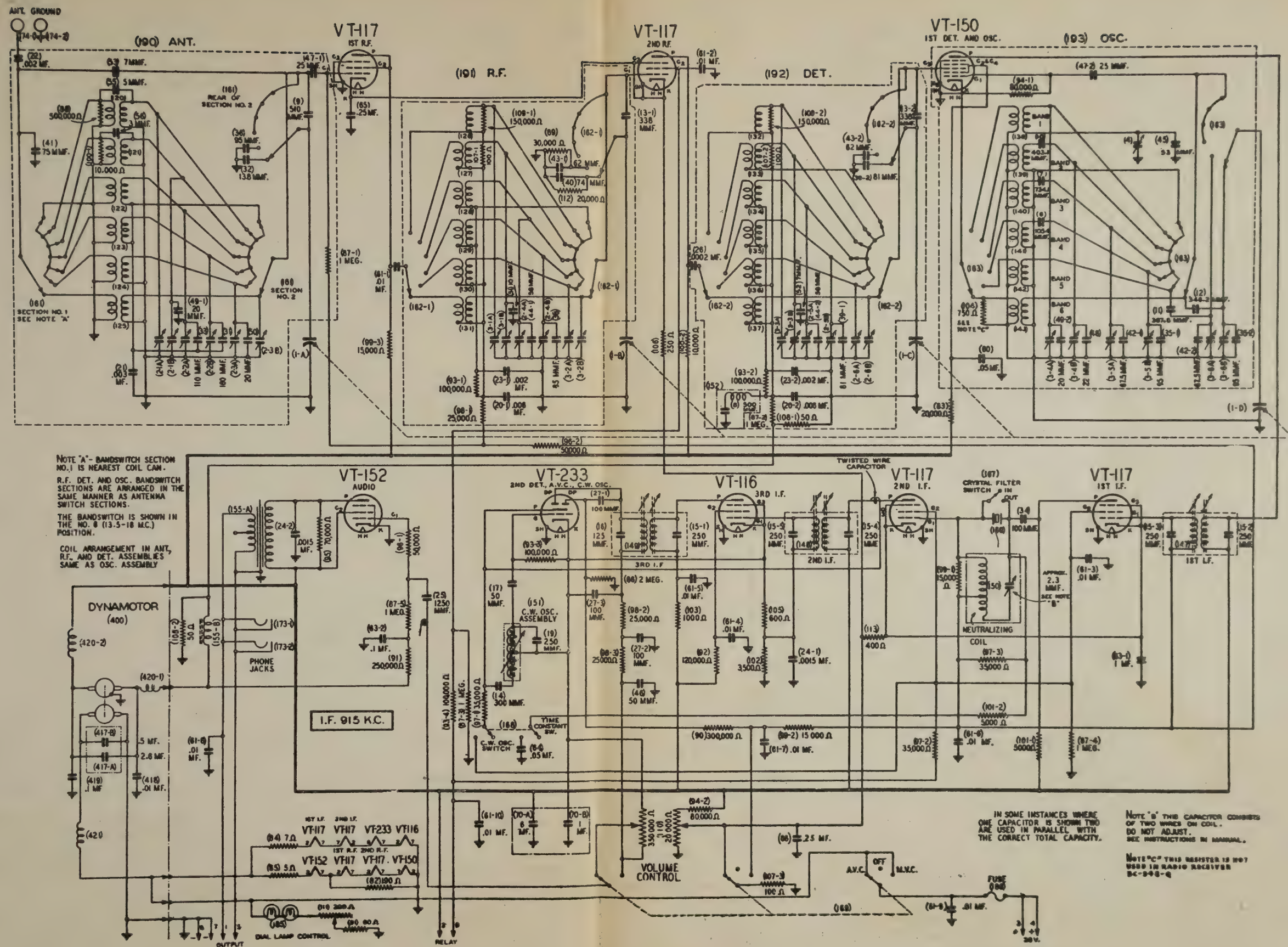


FIGURE 4-348

Radio Receiver BC-348-J, Schematic Diagram

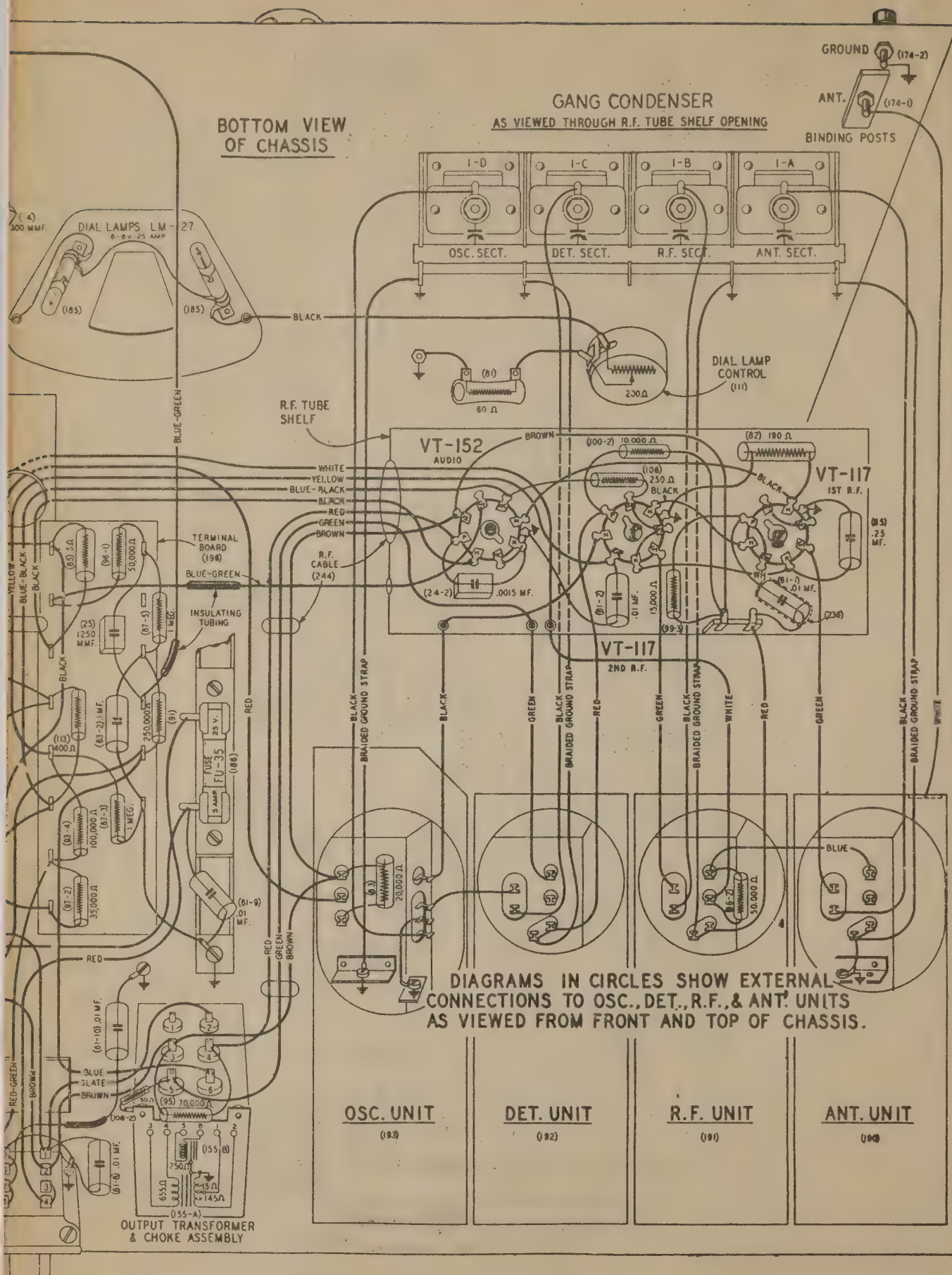


FIGURE 5 -348
Radio Receiver BC-348-J, Wiring Diagram of Chassis

ten
the




(X) WATCH FOR THIS CONNECTION ON SOME MODELS AS IT CONNECTS AT THE SWITCH AND WILL PLACE 110V A.C. ACROSS PANEL L

NOTE:
TERMINALS #6 & #2 ARE
SHORTED BY JUMPER OR
SEND-REC. RELAY.

FIGURE 6

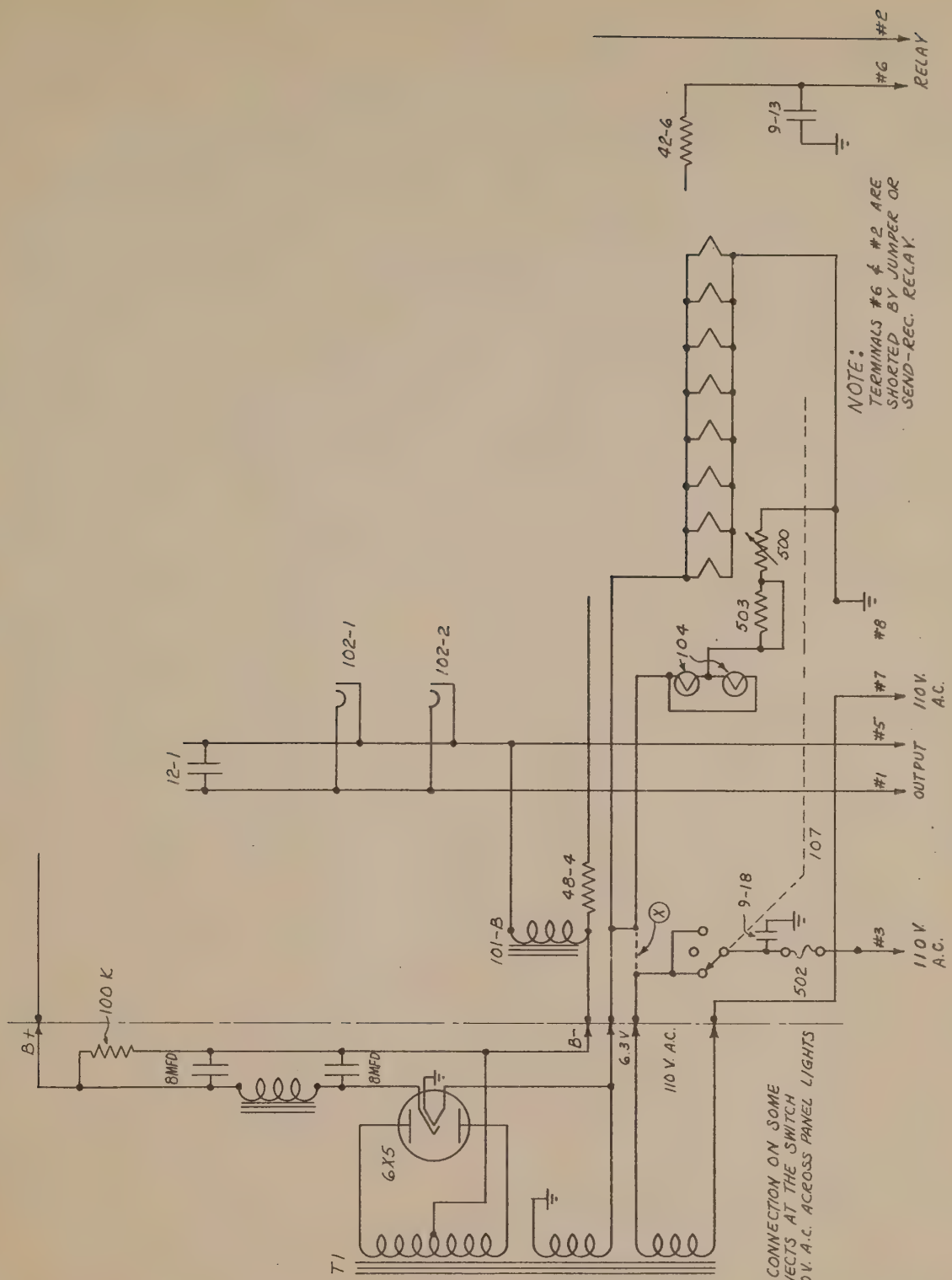NOTE:
T1 MAY BE ANY OF THE
FOLLOWING: STANCO P6120
THORNDARSON 17R36
THORNDARSON 70R18
UTC R2
UTAH Y660



NOTE:
TERMINALS #6 & #2 ARE
SHORTED BY JUMPER OR
SEND-REC. RELAY.

(X) WATCH FOR THIS CONNECTION ON SOME
MODELS AS IT CONNECTS AT THE SWITCH
AND WILL PLACE 110V. A.C. ACROSS PANEL LIGHTS

FIGURE 6

10 METER MOBILE TRANSMITTER AND RECEIVER

ten, the
The SCR-274-N transmitter and receivers were originally made for portable use. The transmitters are light, compact, and powerful. The receivers are light, compact, and sensitive. Above all they are economical as current market prices bring them within the reach of everyone.

With these facts in mind we changed the power supplies and wiring of the units to accommodate the use of six volts as a primary source.

We gave consideration of the use of V. F. O. but decided against this for several reasons, including: the necessity of climbing out to retune, drift caused by voltage variation, etc.

The final analysis resulted in the inclusion of one of our favorite circuits to combine with the SCR-274-N Transmitter. The harmonic generating crystal oscillator of the SCR-522 transmitter BC-625. It works well with any tetrode tube and combines the better qualities of the old Tritet and still older Pierce. This gave plenty drive for the 1625s and left only the coil pruning in two inductances to finish the job.

We used the original modulator with wiring revisions to accommodate the familiar PE-103, in place of the dynamotor which comes with the equipment. The PE-103 gives us 12 volts for the filaments of the transmitter and 500 VDC for plate. Of course, any power delivering these voltages may be used.

By rewinding the antenna relay coils for twelve or six volts and installing two more ceramic feed-through insulators for the receiver antenna connection, we are practically ready to go on the air.

Of course, it's not that simple, but with the following information it won't take long to get that portable mobile working.

LET'S START, BY MODIFYING THE TRANSMITTER.

Remove the covers from the oscillator coil and the bottom of the transmitter. Remove the oscillator padding condenser. Remove the oscillator coil and pull up on it till the leads are exposed and snip them off. Take off the antenna loading coil by removing the four small screws that are in the transmitter face and hold the bracket ends. Remove the coil contactor. Take out the screws that hold the angle brackets at the foot of the final amplifier coil and the three flat fillister screws adjacent to it, which releases the final padder condenser. Now turn the set bottom up and clean off the wiring from the oscillator tube base and all but the filament and ground leads from the target tube base. Remove the ballast resistor which parallels the target tube filament and drop the leads from the plus end down to pin No. 2 of the same tube. Remove the flexible shaft between the two tuning condensers and by removing the screws from the top, drop out the oscillator tuning condenser. Remove the antenna relay.

To start rebuilding, get a mounting terminal, or build one, with four mounting studs as shown in cut No. 10-274-N and mount the circuit components as shown. Then tuck it into the corner of the transmitter as suggested. Solder a length of stiff bus wire to the stator of the oscillator condenser on the drive shaft side and bend it so that when the condenser is replaced the bus wire will come up between the two 1625 bases and the oscillator condenser frame. Replace the condenser. Put a small mounting strip on the side as also shown in cut No. 10-274-N for the final grid choke and resistor and drill a hole for the shaft bushing in the front panel in the opposite corner from the tuning knob. This shaft is approximately 6½ inches of flexible cable plus the solid fittings.

Remove the meter and thermal unit from the antenna relay BC-442. The thermal unit is mounted on the deck

of the transmitter between the antenna coupling coil shaft and the cover. One of the holes which formerly held the loading coil contactor will give the location for drilling the other mounting hole.

The crystal supplied with the transmitter is mounted in a sealed unit with octal base contacts. The contacts used for this crystal are three and seven. The same socket was utilized for the 7 mc crystal since it was mounted in an FT-243 holder. If only old type crystals are available an adapter may be made from an octal tube base.

Now let's get to the coils. The oscillator coil you will notice, has an inner coil suspended on cross wires. If you possess cutters that will reach in the coil, cut out the soldered chunk in the center and gently (that ceramic cracks if you rough it) pull the cross wires out. Not having the cutters for the job, put the coil in a clamp or vise and heat the cross until it is good and hot, clear to the outside, and pull the pins out using a pair of pliers and much speed and dexterity. Clean off all the old winding, being careful to keep the heavy primary winding in good shape. Bend the grounding lug at the base out of the way and cut it off.

When ready, take the old primary and wind it back on for 5 turns, spacing the wire one-half wire diameter or, if using transmitter BC-457, use the groove as in the original. Start at the bottom and wind counter-clockwise; tuck your top turn into the hole about midway up the coil. The hole faces the oscillator tube when the coil is in position. Bring the free end down inside the coil and attach it to coil pin No. 8 (pin numbers are shown in transmitter figure 5-274-N diagram). Solder a lead from the start of the winding to coil pin No. 1.

After stripping the final tank T-54 of all but the coupling loop (that includes the parasitic suppressors) get into the bottom and reduce the winding on the coupling loop by at least one turn.

Now, working with a soldering iron and needlenose pliers, remove the lug that was used to anchor the parasitic suppressors. When free, use the same finger burning process to reinsert in the hole at the back of the coil nearest the tubes. This allows the coil ending to be as close as possible to the 1625's plate caps and offers an anchor spot for the plate leads. Starting from the bottom solder lug of the coil, wind counter-clockwise up the form, at such an angle as to cause the first quarter turn of the wire to pass through the angle slot on the coil body, and then wind three turns of No. 12 bare tinned copper wire, spacing the turns about ¼ inch and ending on the top lug.

Neither coil has any use for the slug unless someone would like to make the two circuits track. This would be handy in a small way, but for the sake of simplicity, we decided against this.

The circuit capacities in the final amplifier pile up due to construction details, and this, at first, caused the tuning to be most critical and in the minimum extreme of the condenser. Rather than remove the condenser plates, we tapped down the lead, from condenser C65 to plate, three-fourths of a turn and gave ourselves a little room on the tuning dial. Tuning is not critical as far as divisions go, due to the large geared-down ratio of knob to shaft, and because of the tapped down connection. The parasitic suppressors originally on the coil will not do, for they absorb 28 mc with enough gusto to burn themselves up. With misgivings, we cut them out and found no trace of parasitics, and so, did not replace them. It may well be that others will not have that much blind luck, but any of the usual type in general use for those frequencies should do.

The antenna relay poses a question for the user. In the test setup the relay supplied was removed, taken apart, the windings removed and rewound with No. 26 SCC wire. Reassembled, it worked with fair snap at six volts. To be sure of positive action, it was later replaced with a standard

Leach relay. A coaxial connector (Jones 101), was fitted into the transmitter front in place of the original feed through, and another further down, to the side, for a lead to the receiver. In either case, twelve or six volts may be used to activate the relay, depending on which type is at hand, for the relay is activated from a contactor in relay 3-E-6 in the PE-103.

If the original antenna relay is kept, the left hand bracket of the loading coil must be retained, for the contactor it holds is part of the antenna relay. The bottom contact may be changed to a feed-through bushing and used for the receiver antenna post. The transmitter relay, K-53, under the chassis is not essential and rather in the way. This was removed entirely and leads from it, soldered direct.

Due to the new location of the final grid resistor, the old connection to pin two of J-64 was not used. This connected to the grid resistor and allowed voltage impressed across it to be read when a certain type of test gear was used. As there are no metering jacks in the rig, this may be connected by a lead to the grid connection in mention and used to tune up with, using a voltmeter. This is difficult, however, and in our model, two closed circuit jacks were mounted in insulated bushings in the side of the transmitter above and forward of that portion covered by the mounting rack. One of these was used in the final grid circuit to read grid current, and the other in the plate circuit. These jacks may be installed, if desired, in the mounting rack, and would then read plate current of the oscillator and final. We preferred to read the final grid current for check purposes and so installed the jacks in the set.

Now some word about the antenna current indicator. In our model, the thermocouple from the separate antenna relay was mounted in the transmitter proper and the ground lead from the coupling coil was piped through the R. F. end of the thermocouple to ground. By grounding the negative side of the thermocouple output and running a lead from the positive, back through and under the chassis deck to pin No. 2 of J-64 which, as we above stated, is not used, we then had a connection back through the system to the control head utilizing one of the selector wires which is not in use. This enabled us to mount the indicator from relay BC-442 on a small plate affixed to the transmitter remote control and serves at all times to tell whether no answer from a call is due to skip, QRM, or no output from the transmitter.

A 12A6 tube was used for the oscillator as it was at hand in one of the 274N receivers. It works nicely with plenty of output.

For those inclined to fine detail work the modulating equipment may be stripped out of case and mounted either in the transmitter or on the transmitter rack. As there is an unused tube socket in the transmitter, this would accommodate a tube for the modulator. 6L6s would do the job nicely. Put the filaments in series. One for the crystal oscillator and one for modulation.

MODULATOR

The modulator will have to undergo some alteration; not in changing circuits but in eliminating them. Number one item is the tone oscillator and its associated components. This tube may be used if any other type mike is wanted, but if the old faithful carbon mike is retained, there is no use for it. The relays are 24 volt and difficult to rewire, so were eliminated by using those in the PE-103.

Taking out this one tube looks simple and is, but the difficulty lies in finding the right wire to snip out. A practical wiring diagram is supplied, along with the schematic, and to save reams of paper and you, hours of time, we suggest you turn the modulator to a good light, and by studying the schematic, and locating the part in question by the practical drawing, put in the changes given in drawing No. 11-274-N. Briefly touched on, the changes are as follows:

The off-on switch originally supplied filament current to all heaters. The plus lead to the heaters has been lifted from J-54, pin 15, and a ground put to pin 15 instead. Pin 18 of that plug now goes to pin No. 1, J-52, and serves to complete the circuit through the genemotor energizing relay of PE-103—PL-148 and J-53 is now unused.

The grid lead which carries the audio from the junction of R-56 and R-55, which bridge the secondary of the mike transformer, is moved up to its new position of the top of R-56. This increases the drive of the audio tube just enough to overcome the loss of higher voltage in the microphone.

C-54-B which has a value of 20 mfd is cut out of the circuit because of the 12 volts feeding the filament is now negative. This is cured by placing a standard electrolytic, cathode by-pass, condenser in its place observing proper polarity.

R-65 is a portion of the voltage divider in the modulator that supplies the oscillator voltage. It should be replaced with a 10 K. 10 watt resistor.

POWER SUPPLY PE-103

In considering the various ways to use the PE-103 Power Supply two questions arose. The first, would the wiring be left as it was originally? Two, what input was most likely to be used? Both questions can be answered at once. Few amateurs will have a twelve volt battery and the original wiring will seldom, if ever, be just what is needed. Therefore, we changed the wiring as shown on plate No. 12-274-N.

No particularly drastic revisions were attempted. When pin No. 1 of the output plug (a PL-51 and socket from the receiver—as no one seems to have the plug that goes with the PE-103) is grounded through the off-on switch of the remote control, the main contactor 3-E-2 from six volts source is closed, starting the dynamotor. Six volts was wired into the double pole single throw relay No. 3-E-6 and when the output lead from this coil is grounded through the mike push-to-talk button, 500 volts for the plates is cut into the modulator and six volts for the trans-receiver relay goes to the transmitter. The circuit breaker No. 3-E-4 and 3-E-3 are in the start-stop line and release the main contactor on any overload either in input or output.

Care must be exercised to determine what type of dynamotor is in your PE-103. There seems to be two types which differ mainly in which side of the low voltage input is connected to plus twelve volts of the generator. Without attention to this it is quite easy to get 18 volts DC across your filaments.

RECEIVER

To make the receiver function on ten meters is relatively simple. The only necessary changes can be done in two steps. The first, is the coil rewinding. Remove the bottom plate and all covers. To get the inner cover which is over the tuning condensers, off, it is necessary to pull the tubes and IF transformers. Two screws each hold the IF transformers on their sockets.

Now remove the RF coils, which are in the bottom front of the receiver. Two small screws hold the coils in. They may be found on the outside of each end of the RF coil assembly. The strip pulls out and coils may be separately removed when the four screws holding them in the can are removed. Each coil has a powdered iron slug mounted on a screw and held in place by fiber tab sprung across the inside of the form. For our purpose of quick change to 10 meter we simply removed the slug and forgot them. Not that they would not be useful but our business concerned only the pulling of turns from the original windings. This leaves the coils unbalanced for proper slug setting so it was simpler to do without.

In pulling coil turns, pull from the bottom (towards the socket) in the RF coils and the top in the oscillator coil.

In the antenna coil, notice that the method of input coupling has changed. The small series condenser in the antenna lead has been removed and lead run straight from the antenna post to the low impedance tap on the coil. The small condenser (C-1) is hidden behind the tuning condenser bank. There is an unused tap on the antenna coil which is used for the new antenna lead. By following drawing 8-274-N the coil dope should be easy to duplicate.

No particularly fine attempt was made to make tracking 100% across the dial. When the tracking was sufficient to fully cover the 10 meter band (from 8.3 to 9, on the dial), we started the second stage of conversion. The stator leads and the lead to the oscillator series padder condenser were disconnected. The dial was removed from the front of the receiver and the four screws holding the main condenser were removed. Then by rocking the condenser back it may be removed from the chassis. With the sidecutters snip off the long narrow tail from each rotor plate. This gives us room to mount a series condenser marked CX in drawing No. 8-274-N on the inside bottom of each of the three sections of the main tuning condenser. These series jobs are made by the Erie Resistor Co. and are designated as ceramicon trimmer, type TS2A and have a value of 7 to 45 mmf. The trimmer stator lug projects straight along the main condenser stator plates and was soldered tight to them. Be careful in placing them to prevent the ceramicons from shorting on the RF coil plug base leads. Now put the tuning condenser back in place and hook up as it was before, using the ceramicons as the new stator leads.

With the coils complete and in place, turn the antenna and RF ceramicons to full capacity and the oscillator section about 30 degrees out. All of the original trimmers are left just slightly engaged. Now by means of a signal generator or by tuning and trimming till a strong signal is found, the set may be lined up. As individuals will vary in methods and ways to convert this receiver; our treatment, outlined above, is but a rough sketch of what may be accomplished. Our guiding thought in making these changes was to find the easiest and least expensive method to convert to 10 meters. No particular time was spent in evolving fine detail or procedure. The net result of these experiments was a transmitter with plenty of output and ease of operation and a receiver with fair sensitivity with the 10 meter band spread out over three major divisions of receiver remote tuning dial.

We suggest that user build into the receiver one of the simpler type noise limiting circuits, preferably one using 1N34 crystals for diodes, for ignition noise can be quite a problem with this receiver.

RECEIVER FILAMENT CONVERSION

For 12 (6) volt operation it will be necessary to re-wire the tube filaments in parallel. In making these changes consult the practical wiring diagram for the receiver.

First remove the screws, by means of which, the by-pass condensers are mounted on each side of the chassis and pull up these condensers so that the tube sockets are exposed. Filament connections are made to pins 2 and 7 except tube VT-133(V7), which are made to pins 7 and 8.

Beginning with V8, remove the lead from pin 7 and re-connect it to pin 2. Ground pin 7. Remove the lead from pin 2 of V5 and connect it to pin 7. Ground pin 2. Remove lead from pin 2 of V4 and connect it to pin 7. Ground pin 2 which completes this modification.

The rack which the SCR-274-N transmitter slides into has places for two transmitters. As only one is needed, we suggest, and have used, that space for receiver.

The receiver rack has places for three receivers. We sawed free one rack complete with plugs, clamps and inter-connection housing and bolted this unit in the unused transmitter place. While sawing we also cut one end or one

complete section from the triple receiver remote control, which mounted with the transmitter remote control makes a neat small control installation.

For receiver power, several schemes were devised to obtain B+ voltage from the PE-103 but all were discarded because of the high current drawn by this unit. For listening over the band there is no sense wasting that much juice. We ended up by paralleling the receiver filament circuits and replaced the tubes in the receiver with equivalent six volt tubes. B+ is obtained from a Mallory six volt vibropack type VP-522. By using spacing washers between the vibropack and the old dynamotor mounting base we have a demountable vibropack held on the rubber shock mounts by snap-slides.

OPERATING NOTES FOR THE 10 METER MOBILE TRANSMITTER

In operation the crystal oscillator draws approximately 21 mills plate and screen. At this current 7 mills drive may be realized in the grids of the amplifier. This will seem high but for the use of tubes in parallel that double in the plate, it may be necessary.

Final plate current at no load is also high; somewhere between 45 and 60 mills, but this condition is not unusual in tetrodes, doubling at 28 mc. The amplifier may be loaded up to 120 mills by the usual quarter wave, whip antenna.

Some difficulty may be experienced with downward modulation unless all load factors are carefully controlled. Please remember that screen grid modulation is easy to abuse. Unlike some modulation methods the screen grid voltage must be carefully handled. The amount of drive, the amount of load and the amount of modulation voltage is critical. A modulation percentage of about 80 may be expected from this transmitter without trouble. Do not remove resistor R-62 from the modulator transformer secondary in an effort to get more signal. Without it the screen voltage runs wild on peaks. One of the principal reasons for using the antenna current indicator is to check for downward modulation which is almost sure indication of improper screen operation. Bias voltages must be high, above one hundred volts, before the modulation settles down to good work.

Twenty meters can be reached in the same manner as the ten meter conversion with the exception of the coils and crystal used.

The oscillator coil will have seven turns and the amplifier coil will have five. For twenty meters, the parasitic suppressors may be left in and there is no need to shorten the plate leads by putting the solder lug in the back of the coil. An 80 meter crystal is used in this version.

For those who possess the BC-459, 20 meter operation is simple to the extreme. This unit tunes from 7 to 9.1 mc. The oscillator gives enough drive to allow doubling in the amplifier plate circuit by rewinding the coil in that stage to hit 14 mc and separating the tuning condensers (don't forget the main dial drive is connected to the amplifier condenser first) tuning shafts. Full power cannot be realized but twenty watts peak can be extracted and that's plenty for exciting a following stage.

For those who have not been able to obtain the BC-459 we have included in these pages an outline of the steps necessary to convert the BC-458 to cover the 7 to 7.4 mc range as it normally covers 5.3 to 7. (We also include the data for changing the BC-457, 4 to 5.3 mc to cover the 80 meter range.) The revamping did not change the frequency stability enough to notice.

For those who will want 40 meter CW operation there are several ways of keying the transmitter. In aircraft installation the transmitters are keyed by using antenna relay unit BC-442 and letting the transmitter run continuously. This is not good practice for amateur use and we suggest

revising the bias system of the amplifier for bias keying. We have seen and heard some stations that use relay K-53 for keying but in most cases there was a noticeable chirp on the signal. Please note that bias resistor R-75 is not a keying aid. It serves only to self bias the amplifier to nearly cut-off when relay K-53 is open.

INSTRUCTIONS FOR CONVERTING THE BC-458-A (5.3-7 mcs.) TO 40 METER USE

If the transmitter is to be used with a 24 volt supply no changes are necessary. If a 12 volt supply is to be used the tube filaments must be wired in parallel. The relays should be closed or removed entirely. If the unit is to be used as a V.F.O., the antenna loading coil may be removed and the variable link on the final tank coil terminated in a suitable low impedance jack mounted on the side or face of the unit.

There are two methods for changing the frequency range of the transmitter. The simplest is as follows:

Set the dial at 7.0 and remove the shield can from the oscillator section. Loosen the locking set screw and reduce the capacity of the oscillator padding condenser. With the aid of a calibrated receiver or frequency meter, adjust the capacity of the padder to the highest frequency (7.3 or 7.4 mcs.). Place a milliammeter in the high voltage lead of the final amplifier and adjust the amplifier padder for minimum plate current.

This method is satisfactory if one is not interested in the dial being calibrated and wishes to set his frequency on the frequency of the station to be called. This is accomplished by tuning the V.F.O. to the frequency to which the receiver is tuned. If dial calibration is desired, the following method should be used:

Remove the oscillator shield can and short out exactly one turn at the top of the oscillator coil; screw the iron cord to within one turn of being all the way in, and replace the shield can. Be sure to replace the can in the final position as any change in the tightness of the shield will change the frequency. Adjust the trimmer for the highest frequency (7.4) with the dial set at 7.0. After this frequency has been set at exactly 7.0 on the dial set the dial to 5.8 mcs. which is 6200 kcs. (the frequency of the crystal) and trim with the iron core slug until resonance is indicated by the magic eye. Retune to 7.0 on the dial and retune the oscillator padder. It may be necessary to repeat the procedure several times to insure proper tracking. After the oscillator is tracking properly the same procedure is followed with the amplifier. Short one turn on the amplifier tank coil and screw the slug down to within two turns of being all the way in. Tune the amplifier trimmer and the iron cord slug for minimum plate current which should be within four milliamperes of the same value at both ends of the dial.

It may be desirable to cover the numbers on the dial with a decal but the unit can be operated very easily by marking the dial settings with the corresponding frequencies on the small plate on the front of the unit as shown in the example below:

Dial	Frequency
5.8	6.2 mcs.
6.6	7.0
6.7	7.1
6.8	7.2
6.9	7.3
7.0	7.4

INSTRUCTIONS FOR CONVERTING THE BC-457-A (4-5.3 mcs.) TO 80 METER USE

If the transmitter is to be used with a 24 volt supply no changes are necessary. If a 12 volt supply is to be used the tube filaments must be wired in parallel. The relays should be wired closed or removed entirely. If the unit is


to be used as a V.F.O. the antenna loading coil may be removed and the variable link on the final tank coil terminated in a suitable low impedance jack mounted on the side or face to the unit.

First remove the shield can over the oscillator section and add four turns to the top of the oscillator coil. This may be done easily by using a small C clamp fastened to the top turn so the coil will not unwind and soldering a length of bell wire or hook-up wire to the end of the winding. After winding four turns, re-solder the end to the condenser lead and remove the C clamp. Insulated wire is suggested since it is necessary to close space the turns. Set the dial to approximately 5.1 which corresponds to 4.6 mcs. (the crystal frequency) and adjust the tuning slug until the magic eye indicates resonance. Set the dial at 4.0 which should be 3.5 mcs. This can be checked by means of a calibrated receiver or frequency meter. If the 3.5-4.6 range falls outside the dial readings 4.-5.1 decrease the capacity of the padder. If this range falls inside these settings, increase the capacity. It will be necessary to make these adjustments several times to make the unit track properly.

After the oscillator is tracking correctly the amplifier must be adjusted. Add four turns to the top of the amplifier tank coil and insert a milliammeter in the plate circuit. Adjust the amplifier padder for minimum plate current which should be within three milliamperes for the two ends of the band. If the difference is greater the capacity should be adjusted to give an almost constant value between 3.5 and 4 mcs. as the 4.6 mcs. frequency will be used only to check the calibration and higher current at that frequency is of no consequence. If desired, the unit can be made to track over the entire band.


It may be desired to cover the dial settings with a decal but the unit can be operated very easily by marking the dial settings with the corresponding frequencies on the small plate on the front of the unit as shown in the example below:

Dial	Frequency
4.0	3.5
4.1	3.6
4.2	3.7
4.3	3.8
4.4	3.9
4.5	4.0

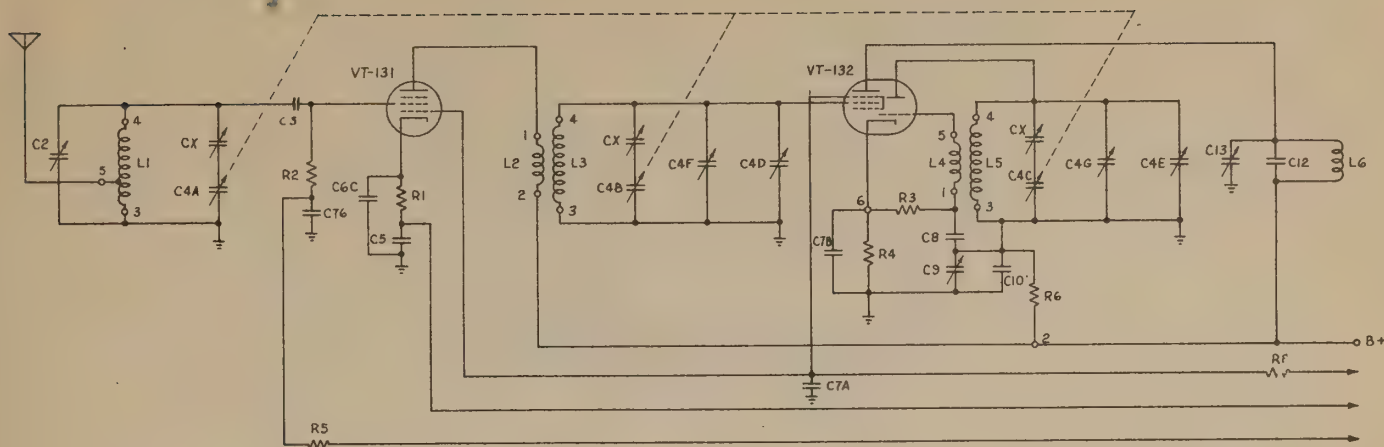


ANTENNA COIL

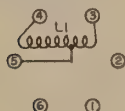L1 - 5 1/2 TURNS
ANTENNA TAP 1 1/2 TURNS
FROM BOTTOM




R.F. COIL

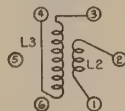L2 - 4 1/2 TURNS CLOSE WOUND
L3 - 6 TURNS
1/16" SPACING BETWEEN COILS



OSCILLATOR COIL

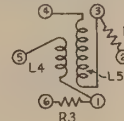L4 - 3 1/2 TURNS CLOSE WOUND
L5 - 5 TURNS
1/16" SPACING BETWEEN COILS



THE R.F. SECTION REMAINS UNCHANGED WITH THE EXCEPTION OF THE ANTENNA COIL AND THE ADDITION OF SERIES CONDENSER C X WHICH IS A VARIABLE CERAMIC TRIMMER CONDENSER, 7 TO 45 MMFD

FIGURE 8-274N

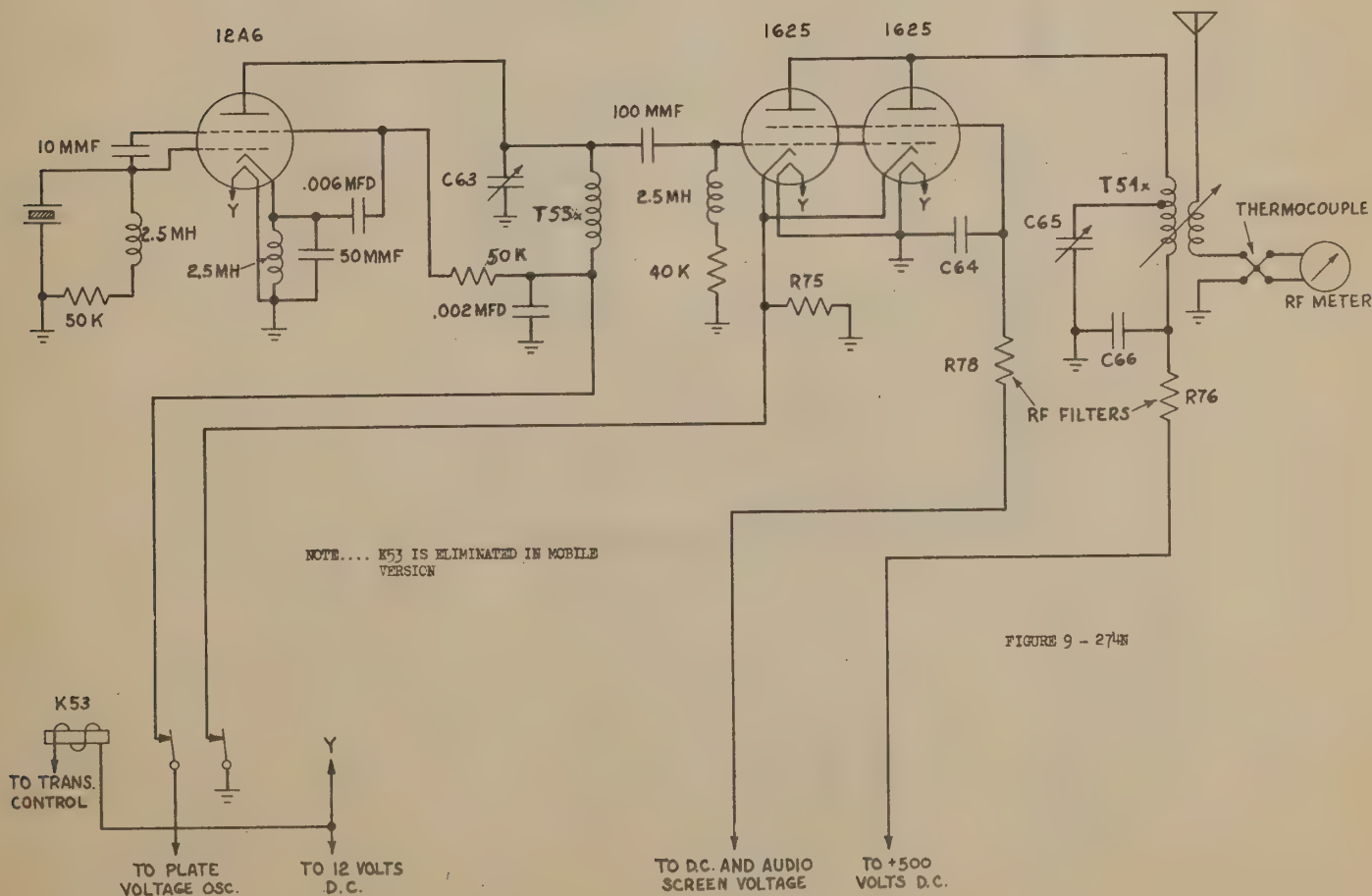


FIGURE 9 - 274N



FIGURE 10-274N

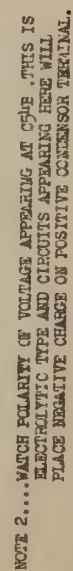


FIGURE 11 - 274M


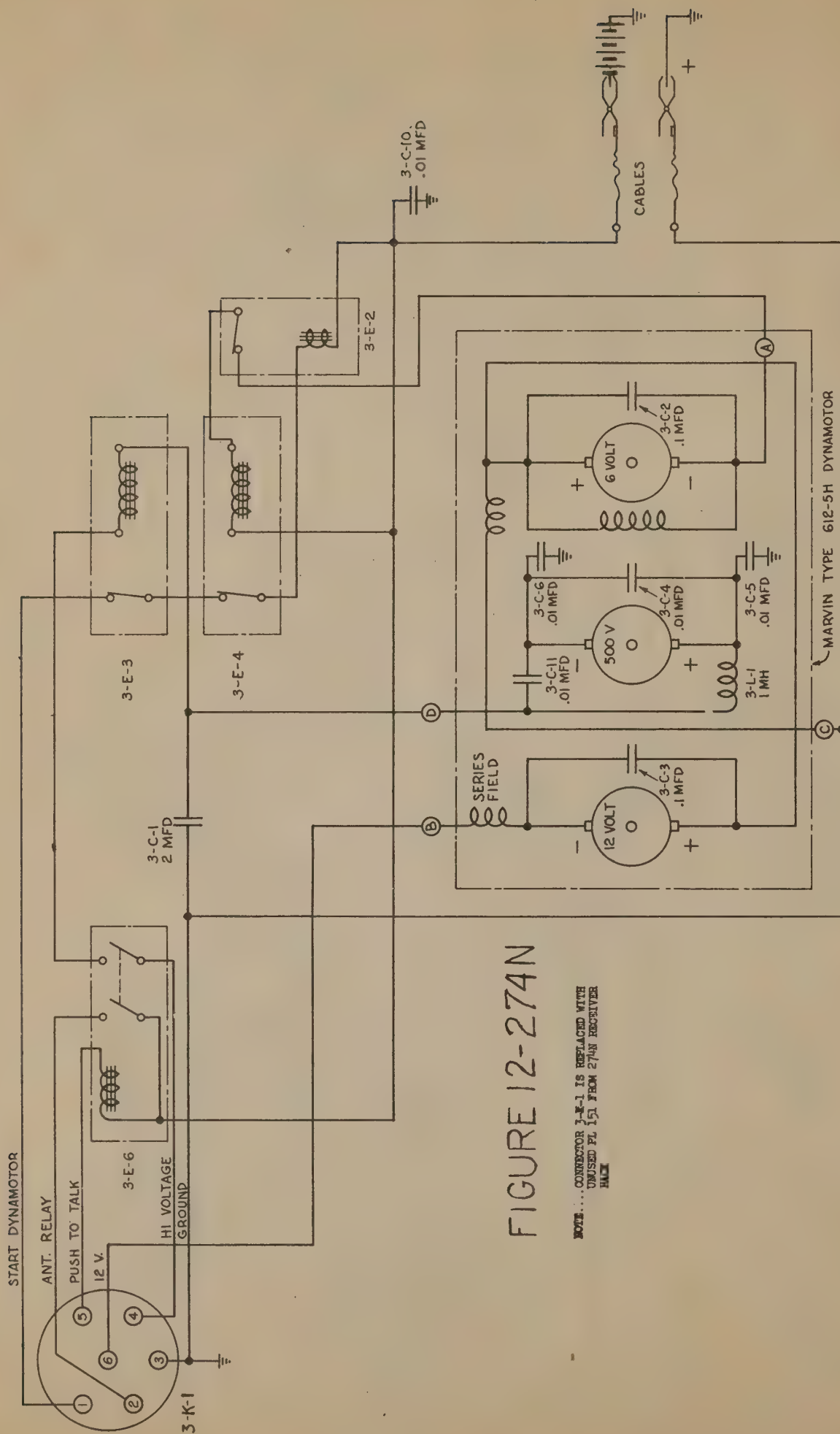



FIGURE 12-274N

NOTE... CONNECTOR 3-E-1 IS REPLACED WITH
UNUSED PL 151 FROM 274N RECEIVER


APN-1

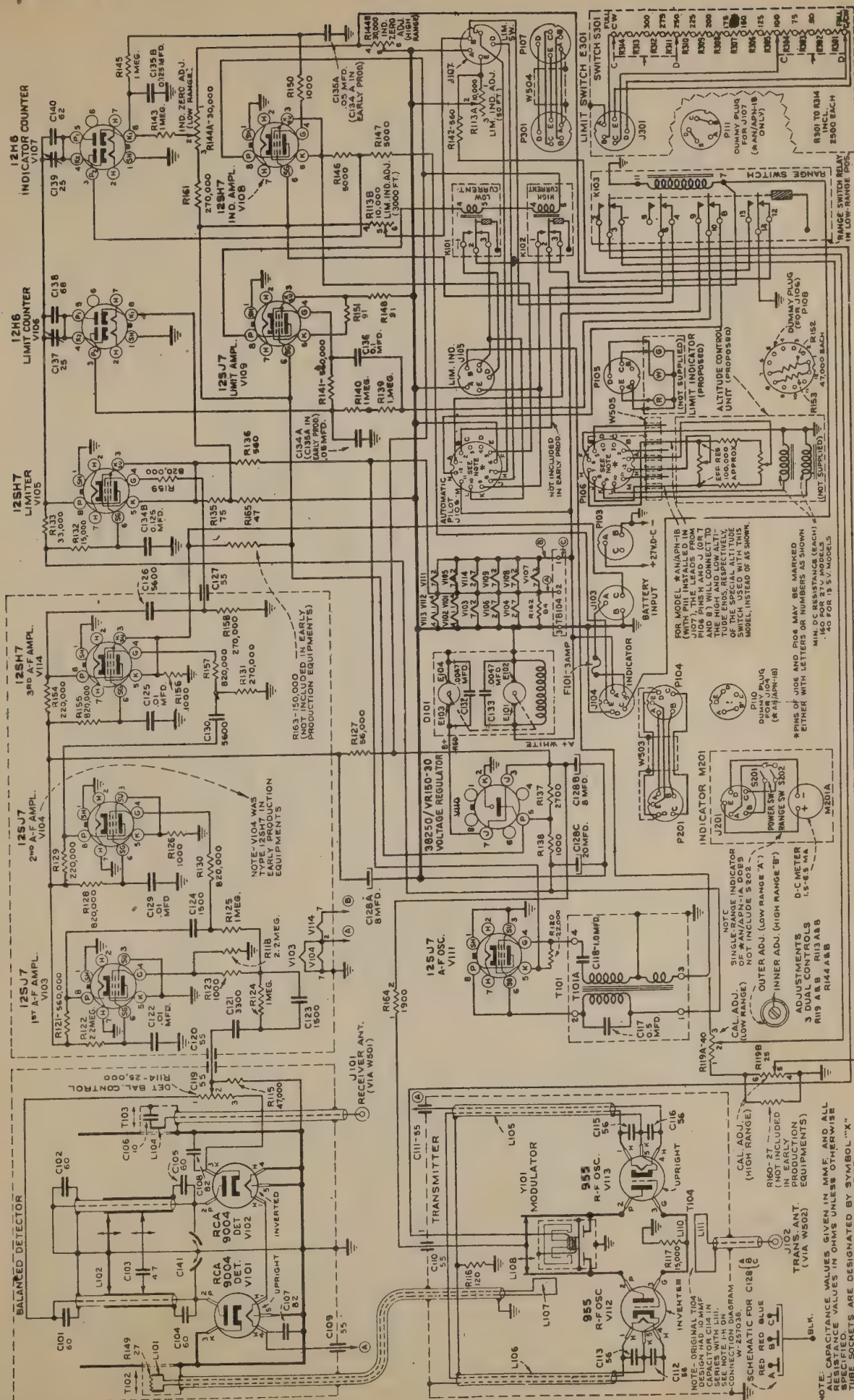

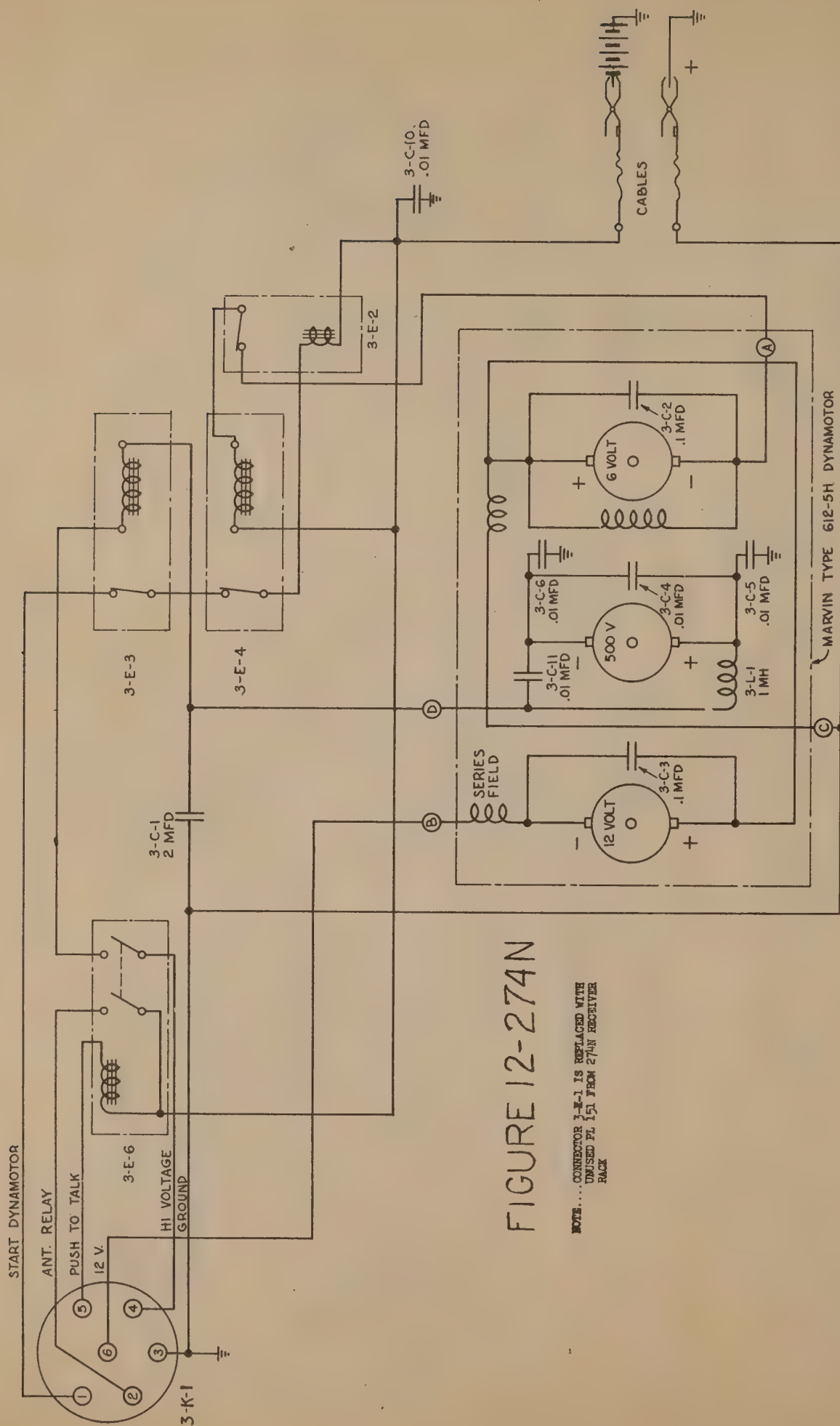REAR (TERM.) VIEW OF ALL PLUGS & SOCKETS SHOWN.
FIGURE 1 - APN-2



NOTE...CONNECTOR 3-K-1 IS REPLACED WITH
UNUSED PL 151 FROM 274N RECEIVER
RACK

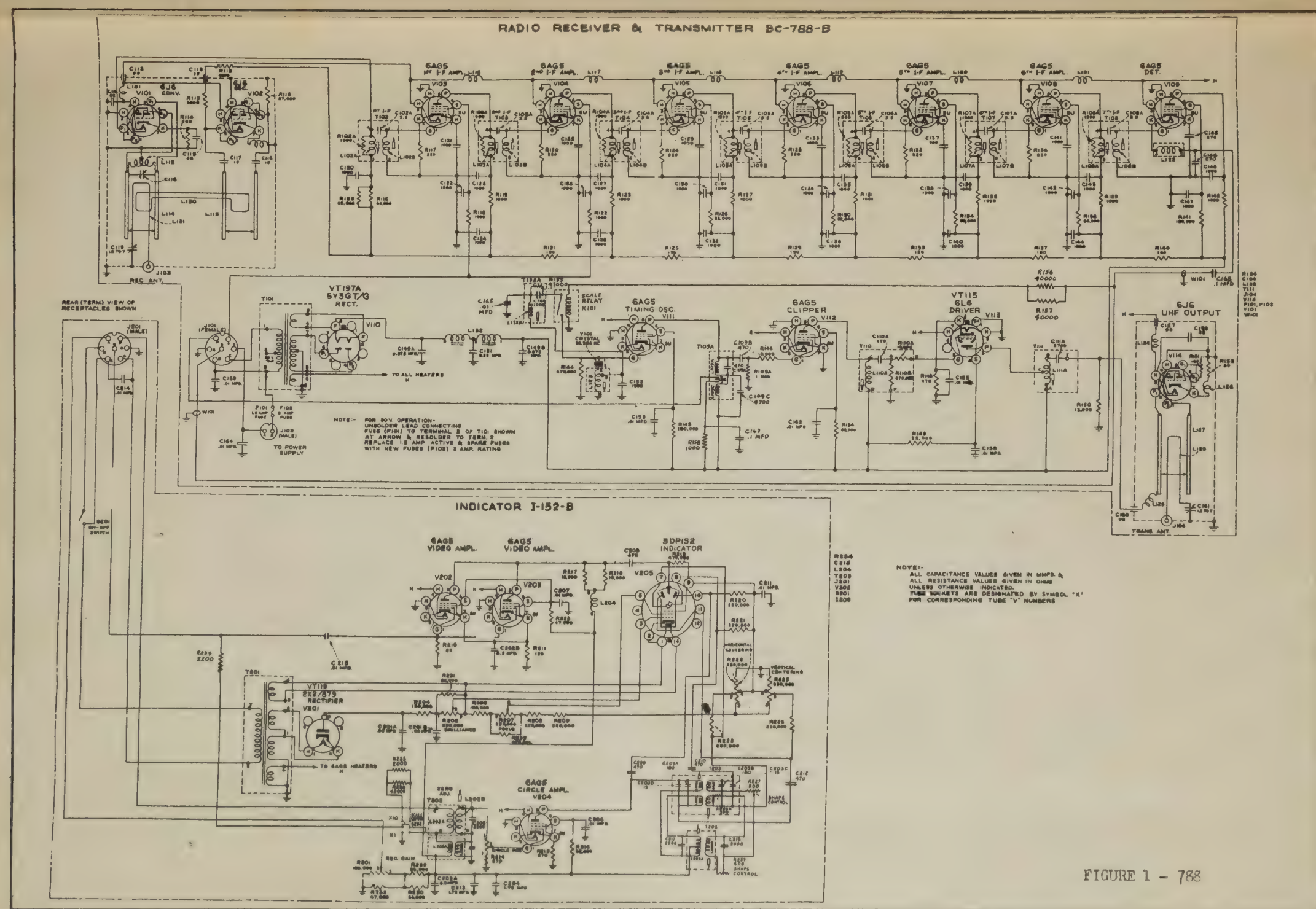



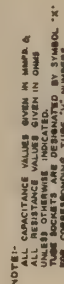



FIGURE 1 - 788

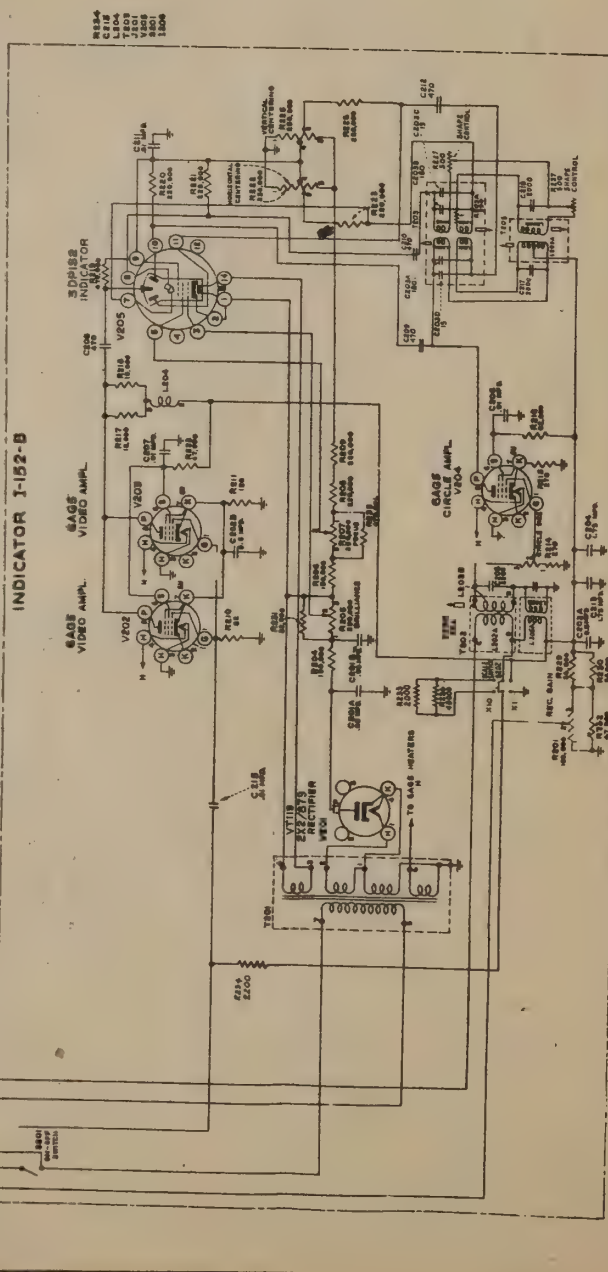

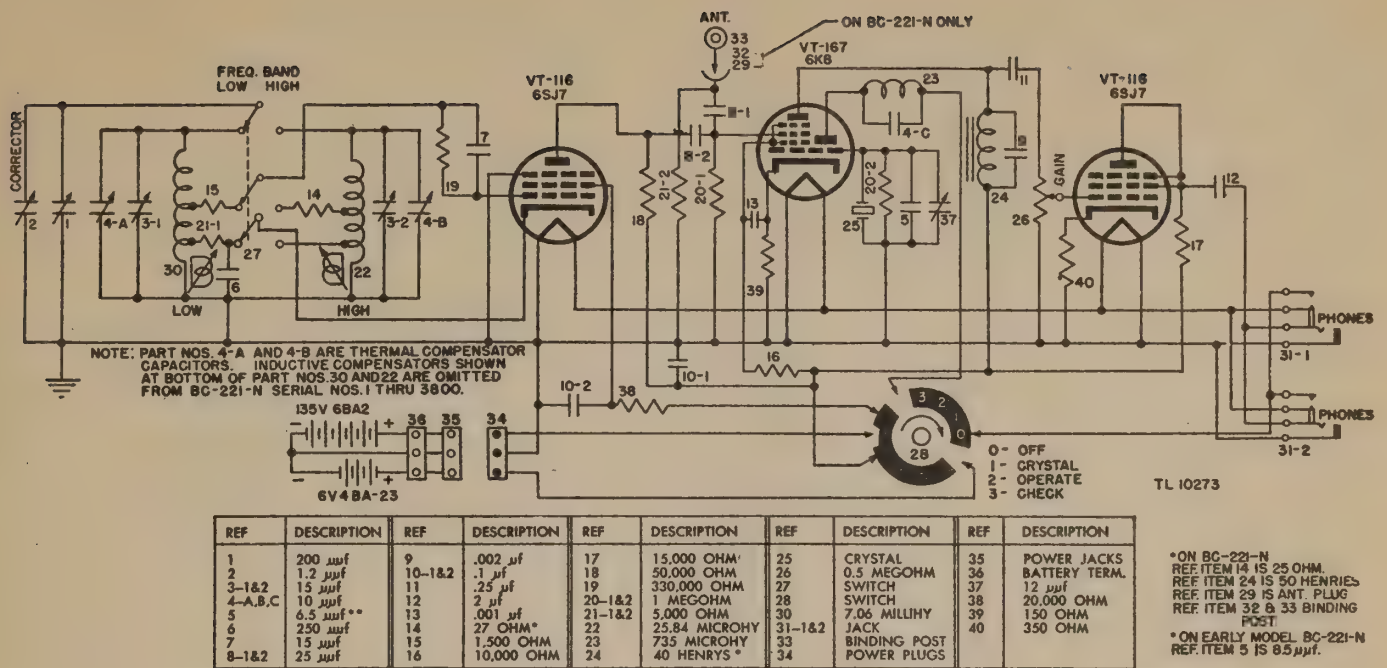


Frequency Meters BC-221-N and BC-221-AA, schematic diagram.


FIGURE 1 - 221

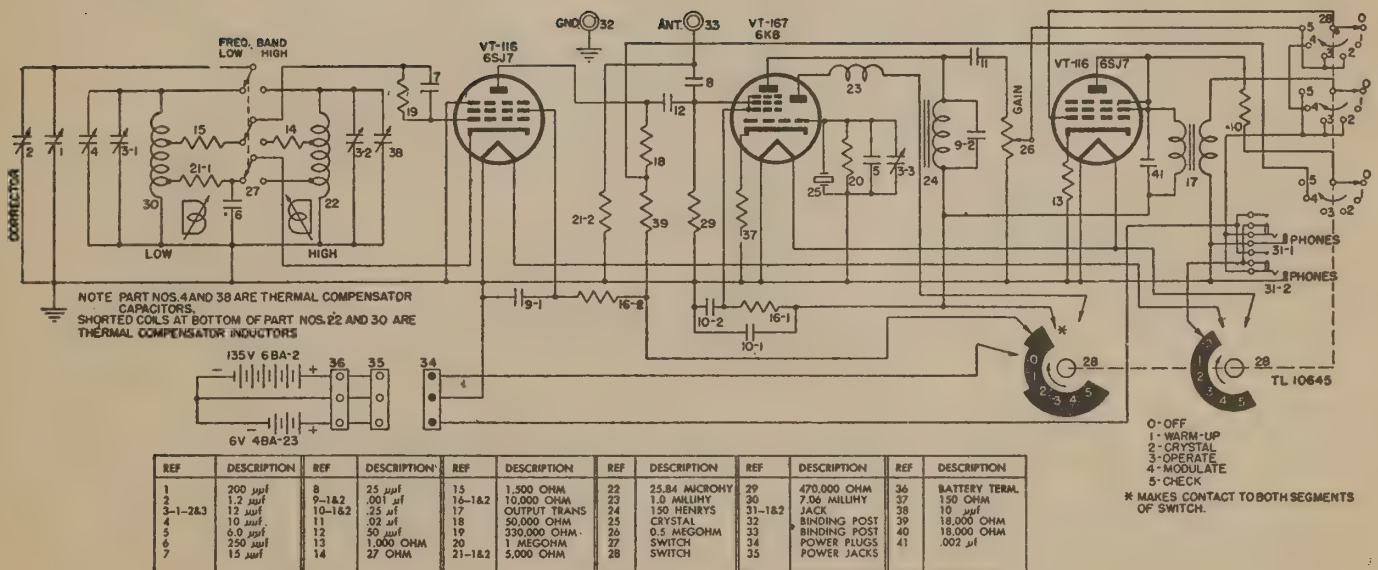

Frequency Meter BC-221-AK, schematic diagram.

FIGURE 2 - 221

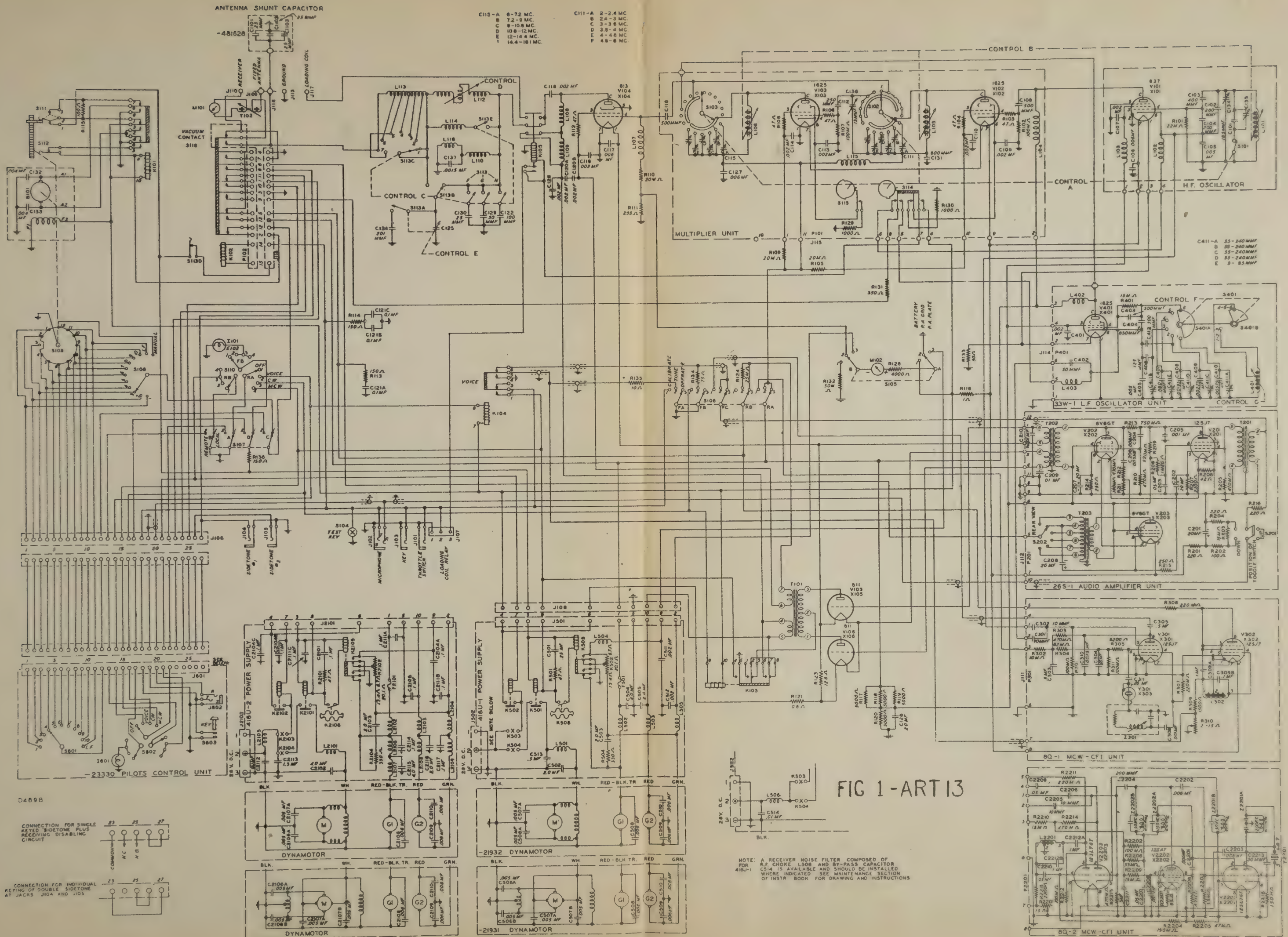

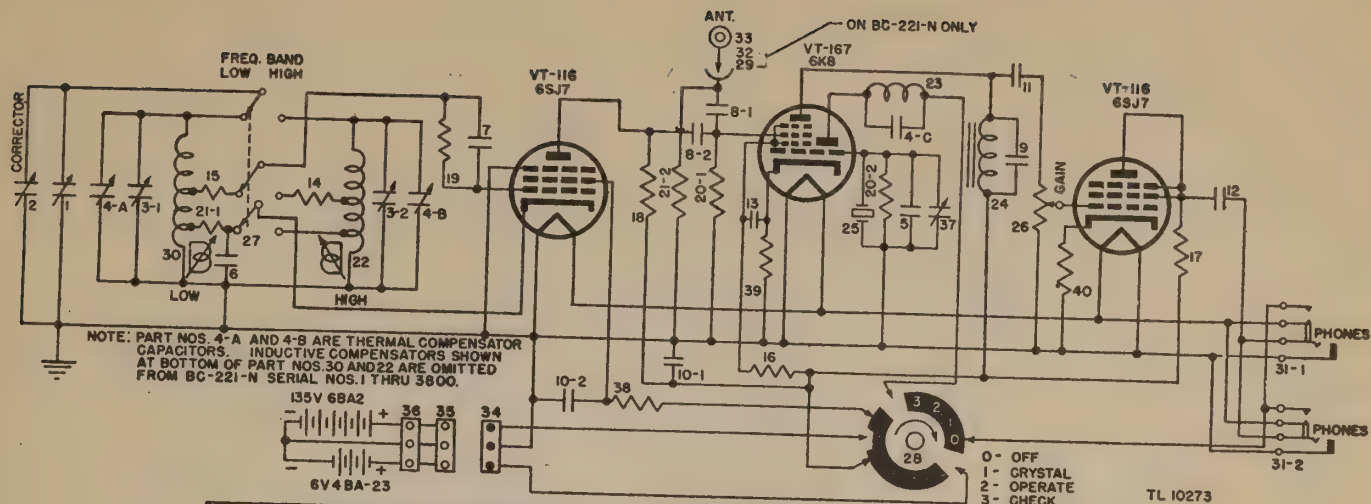


REF	DESCRIPTION	REF	DESCRIPTION	REF	DESCRIPTION	REF	DESCRIPTION	REF	DESCRIPTION
1	200 μ mf	9	.002 μ f	17	15,000 OHM*	25	CRYSTAL	35	POWER JACKS
2	1.2 μ mf	10-1&2	.1 μ f	18	50,000 OHM*	26	0.5 MEGOHM	36	BATTERY TERM.
3-1&2	15 μ mf	11	.25 μ f	19	330,000 OHM	27	SWITCH	37	12 μ f
4-A,B,C	10 μ mf	12	2 μ f	20-1&2	1 MEGOHM	28	SWITCH	38	20,000 OHM
5	6.5 μ mf**	13	.001 μ f	21-1&2	5,000 OHM	30	7.06 MILLIHY	39	150 OHM
6	250 μ mf	14	27 OHM*	22	25.84 MICROHY	31-1&2	JACK	40	350 OHM
7	15 μ mf	15	1,500 OHM	23	735 MICROHY	33	BINDING POST		
8-1&2	25 μ mf	16	10,000 OHM	24	40 HENRY*	34	POWER PLUGS		

*ON BC-221-N
REF ITEM 14 IS 25 OHM.
REF ITEM 24 IS 50 HENRIES
REF ITEM 29 IS ANT. PLUG
REF ITEM 32 & 33 BINDING POST.
*ON EARLY MODEL BC-221-N
REF ITEM 5 IS 8.5 μ mf.

Frequency Meters BC-221-N and BC-221-AA, schematic diagram.

FIGURE 1 - 221

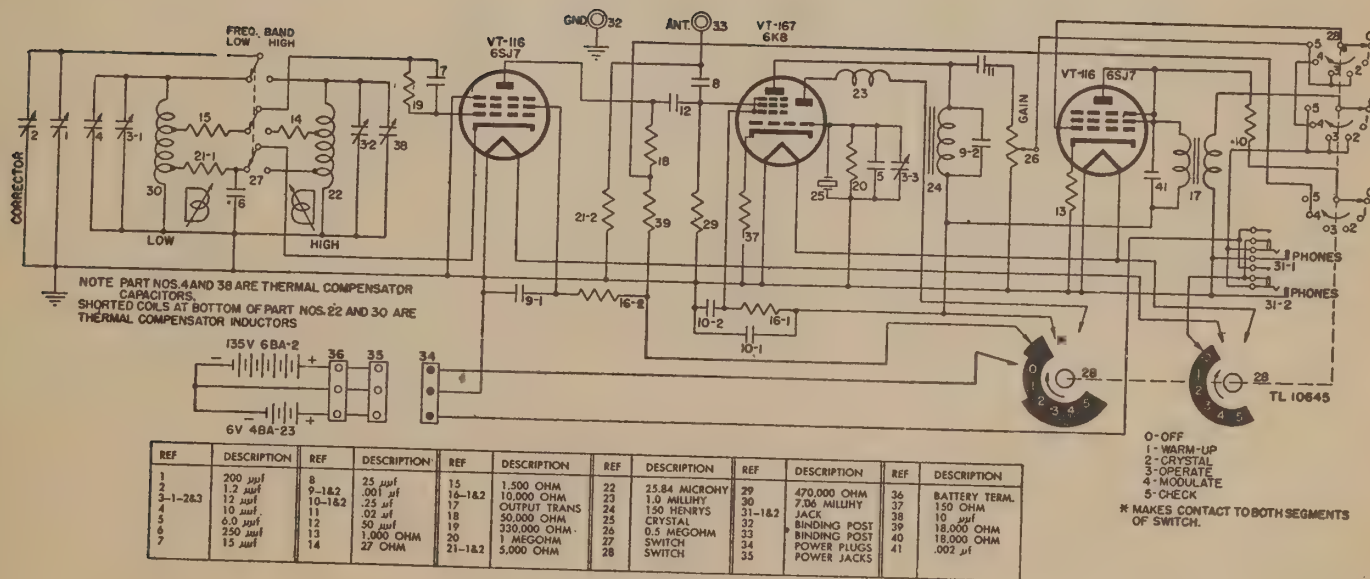

REF	DESCRIPTION	REF	DESCRIPTION	REF	DESCRIPTION	REF	DESCRIPTION	REF	DESCRIPTION
1	200 μ mf	8	25 μ mf	15	1,500 OHM	22	25.84 MICROHY	29	470,000 OHM
2	1.2 μ mf	9-1&2	.001 μ f	16-1&2	10,000 OHM	23	1.0 MILLIHY	30	7.06 MILLIHY
3-1-2&3	12 μ mf	10-1&2	.25 μ f	17	OUTPUT TRANS	24	150 HENRY	31-1&2	JACK
4	10 μ mf	11	.02 μ f	18	50,000 OHM	25	CRYSTAL	32	BINDING POST
5	6.0 μ mf	12	50 μ mf	19	330,000 OHM	26	0.5 MEGOHM	33	BINDING POST
6	250 μ mf	13	1,000 OHM	20	1 MEGOHM	27	SWITCH	34	POWER PLUGS
7	15 μ mf	14	27 OHM	21-1&2	5,000 OHM	28	SWITCH	35	POWER JACKS

Frequency Meter BC-221-AK, schematic diagram.

FIGURE 2 - 221

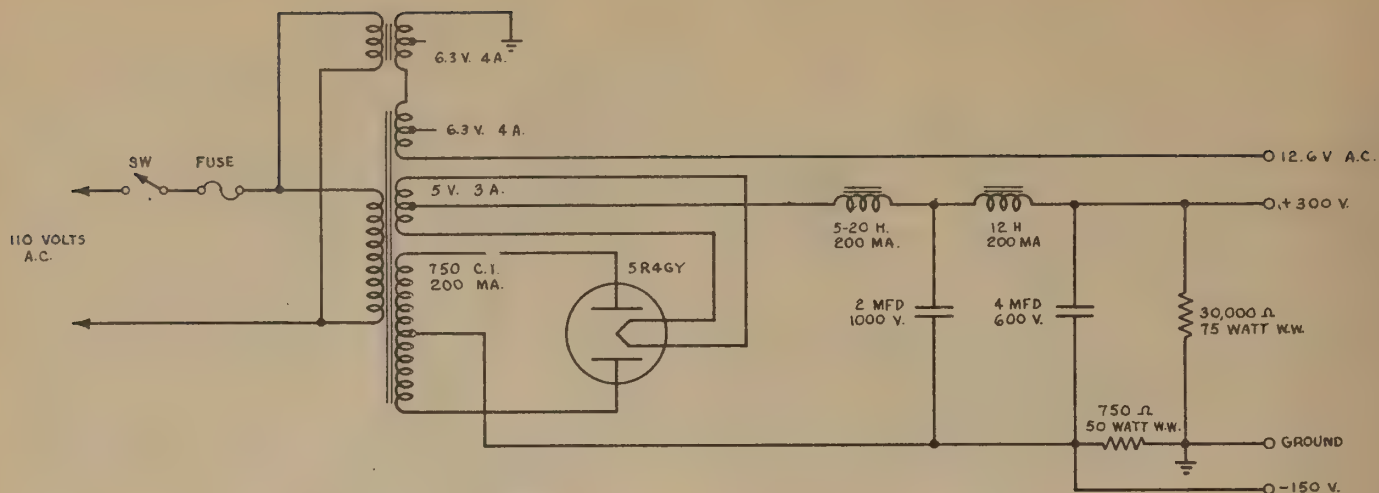


FIGURE 10 - 522

POWER SUPPLY SCR-522


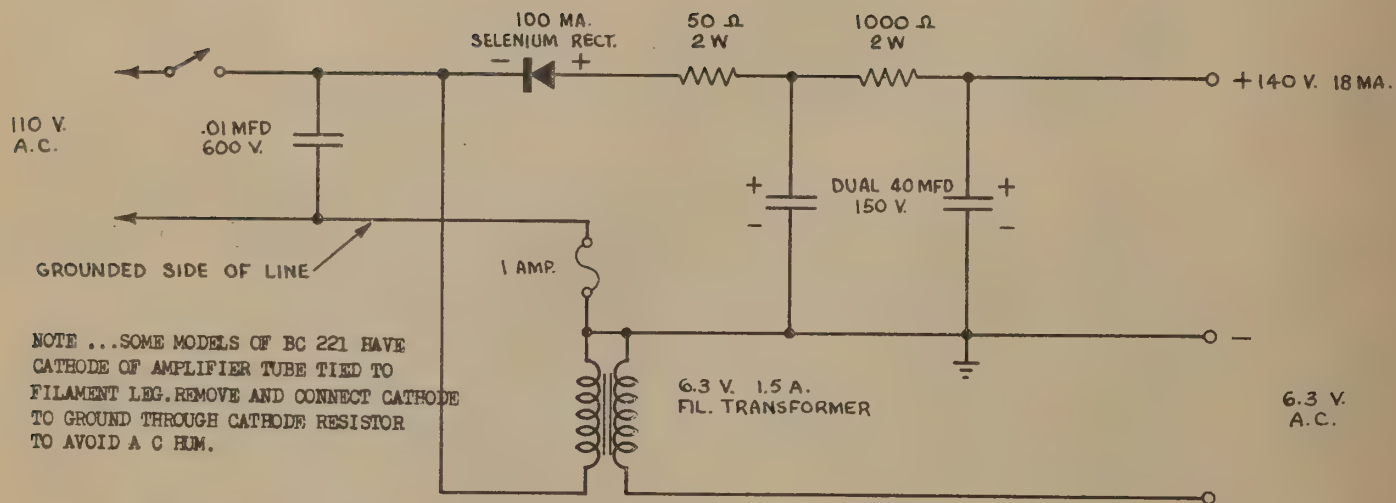


FIGURE 3 - 221

A.C. POWER SUPPLY FOR BC-221

PN-

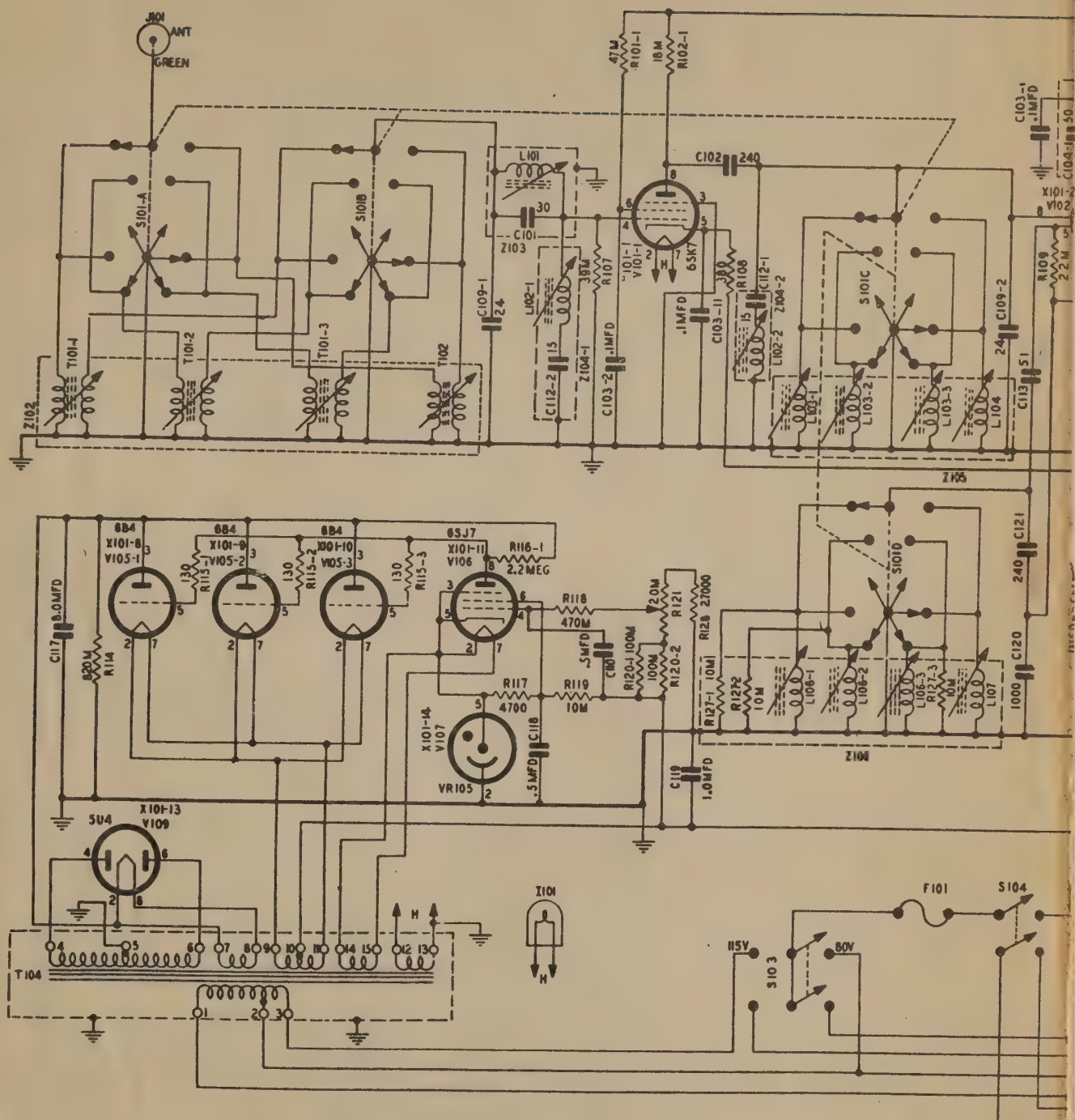

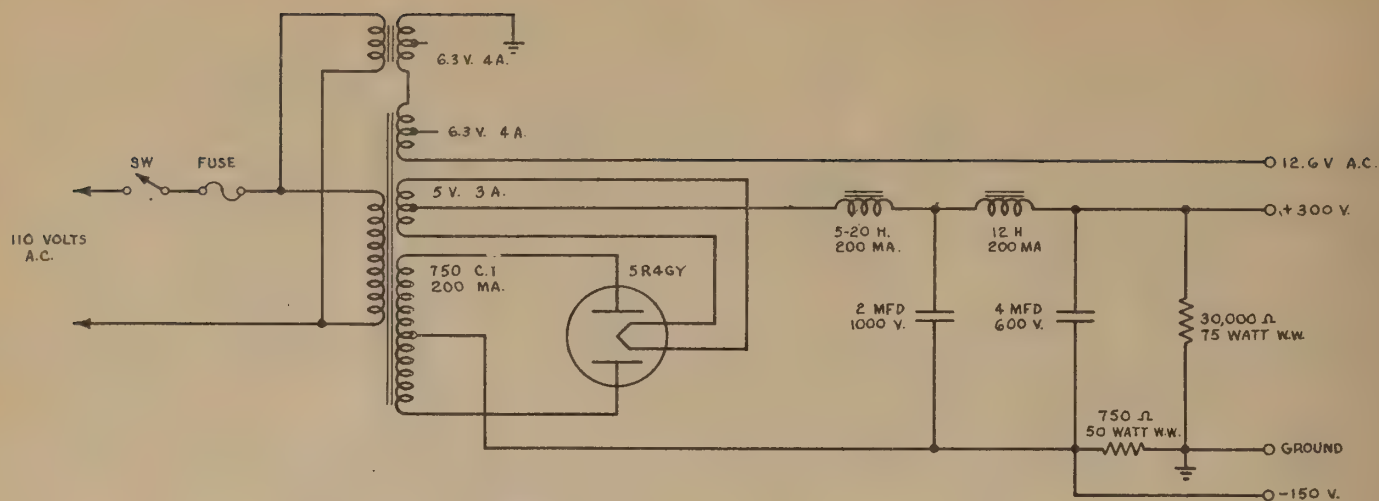


FIGURE 10 - 522

POWER SUPPLY SCR-522


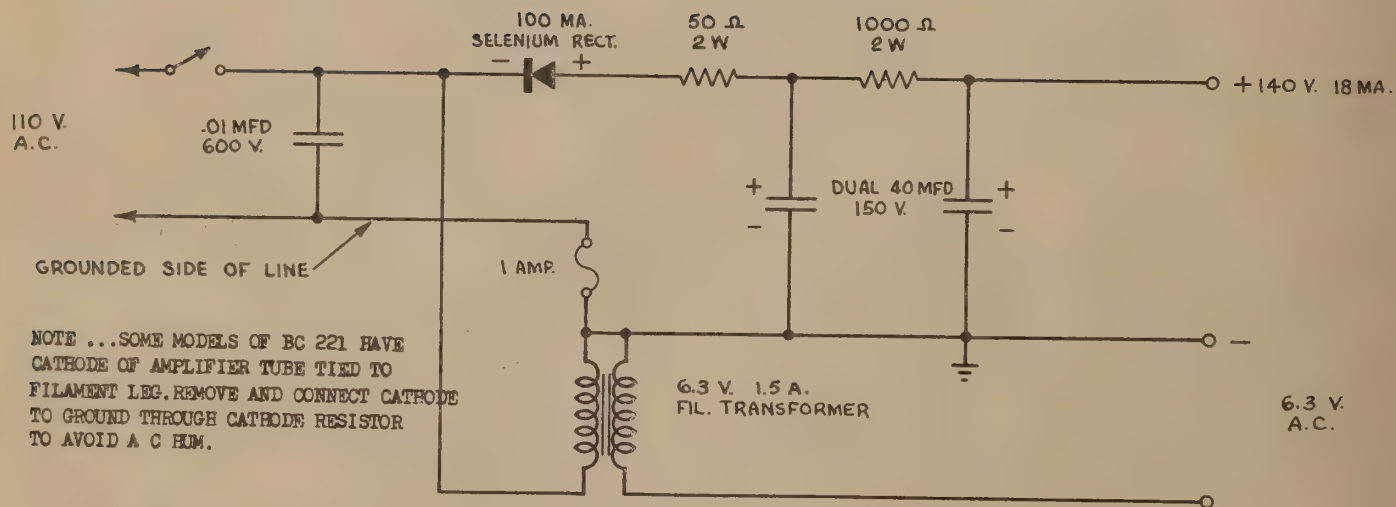


FIGURE 3 - 221

A.C. POWER SUPPLY FOR BC-221

APN-4-#1

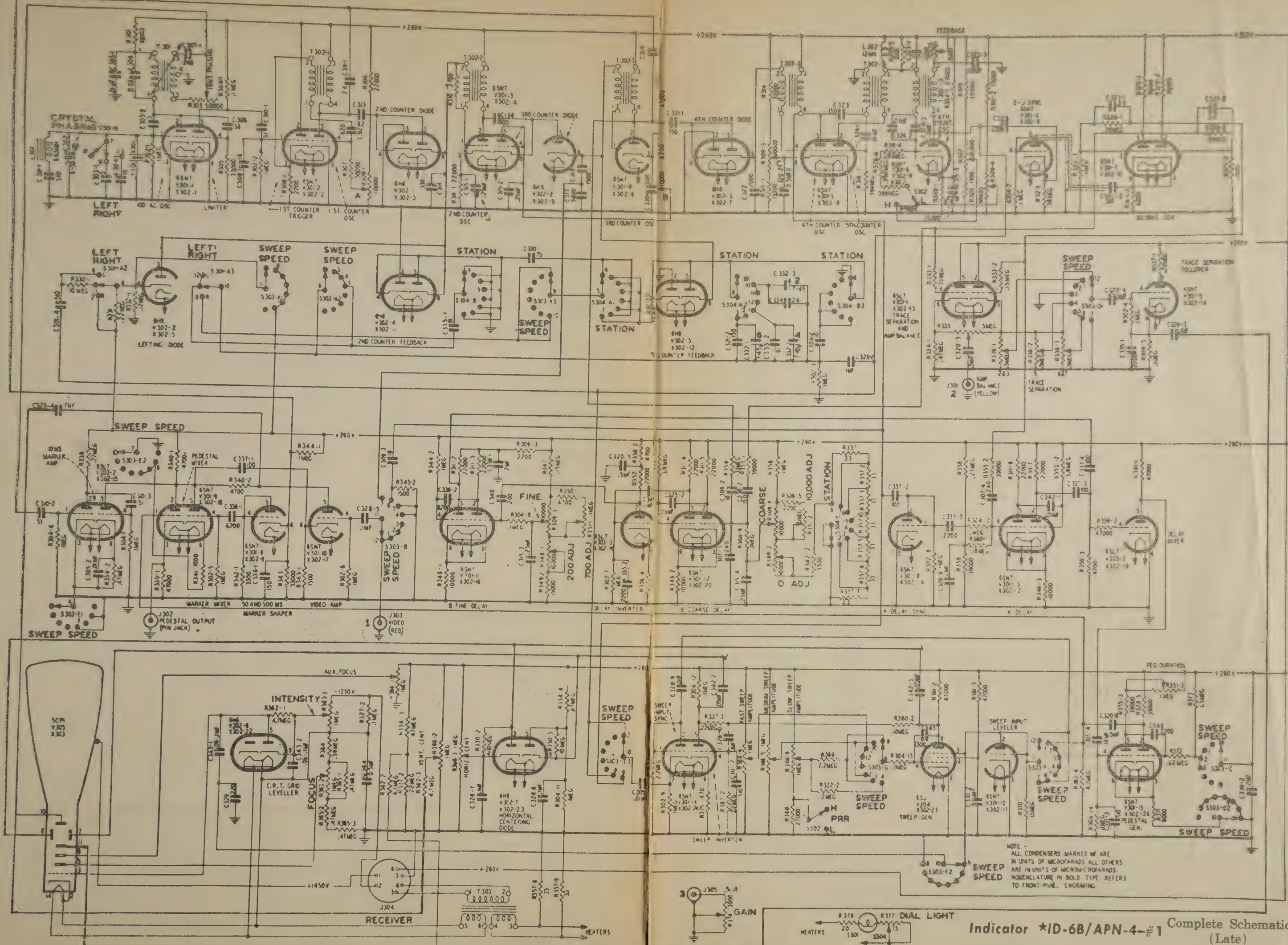

Indicator *ID-6B/APN-4-#1 Complete Schematic (Late)



BC 348-Q

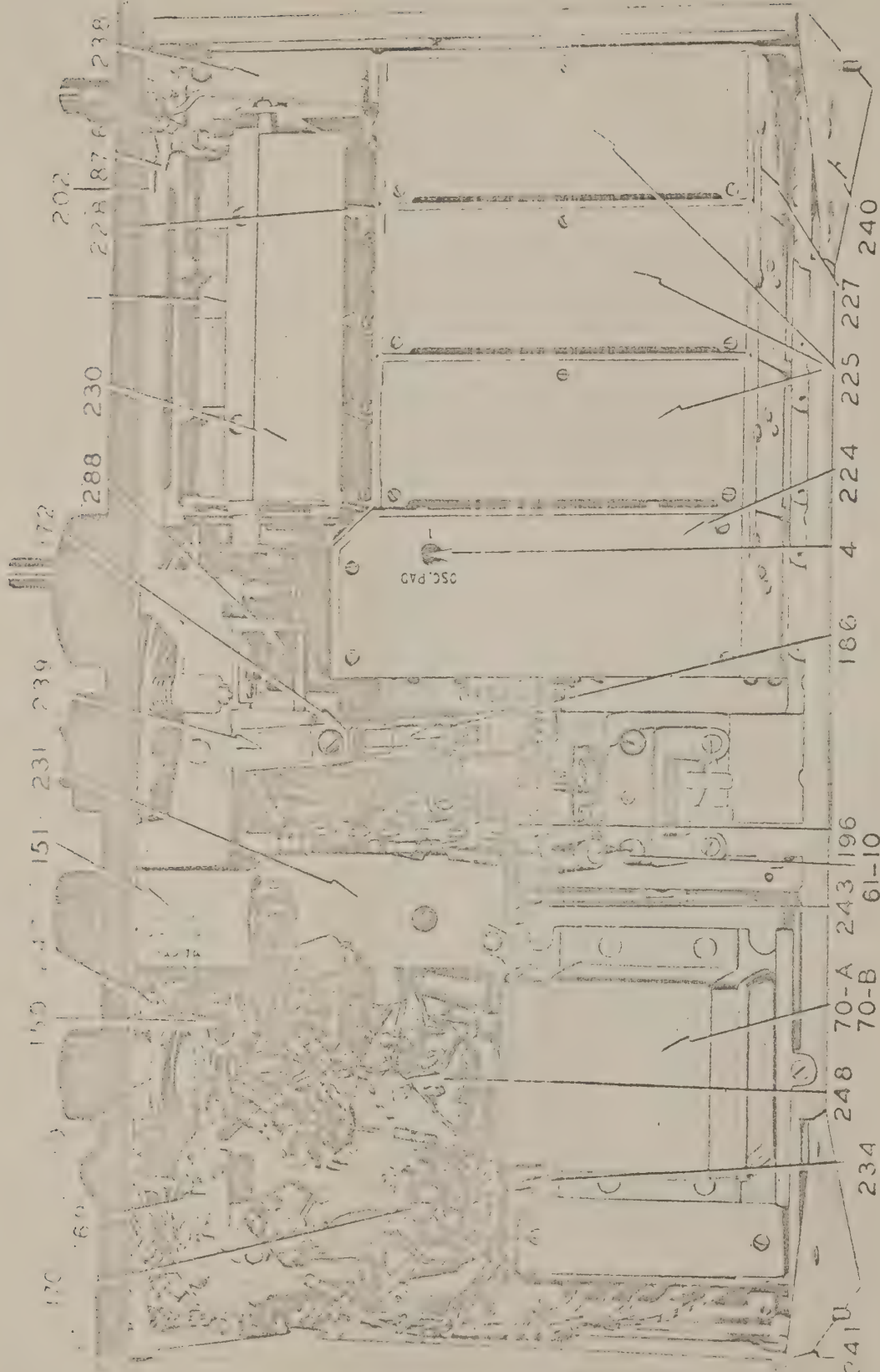


Figure 36 — Radio Receiver BC-348-Q, Bottom View of Chassis

BC 348-Q

AN 08-10-112

Section VIII

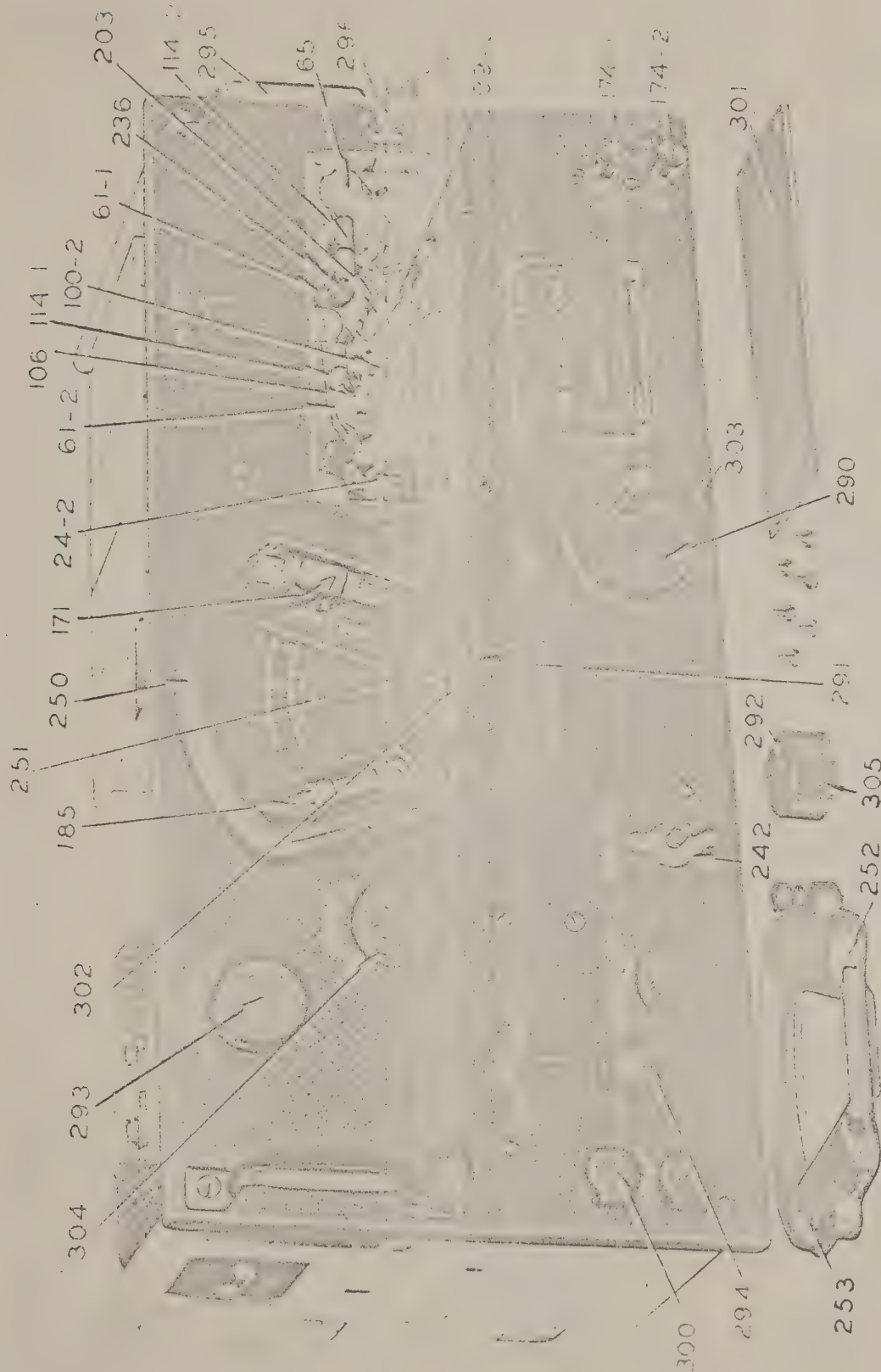


Figure 35 — Radio Receiver BC-348-Q, Front View



AN 08-10-112

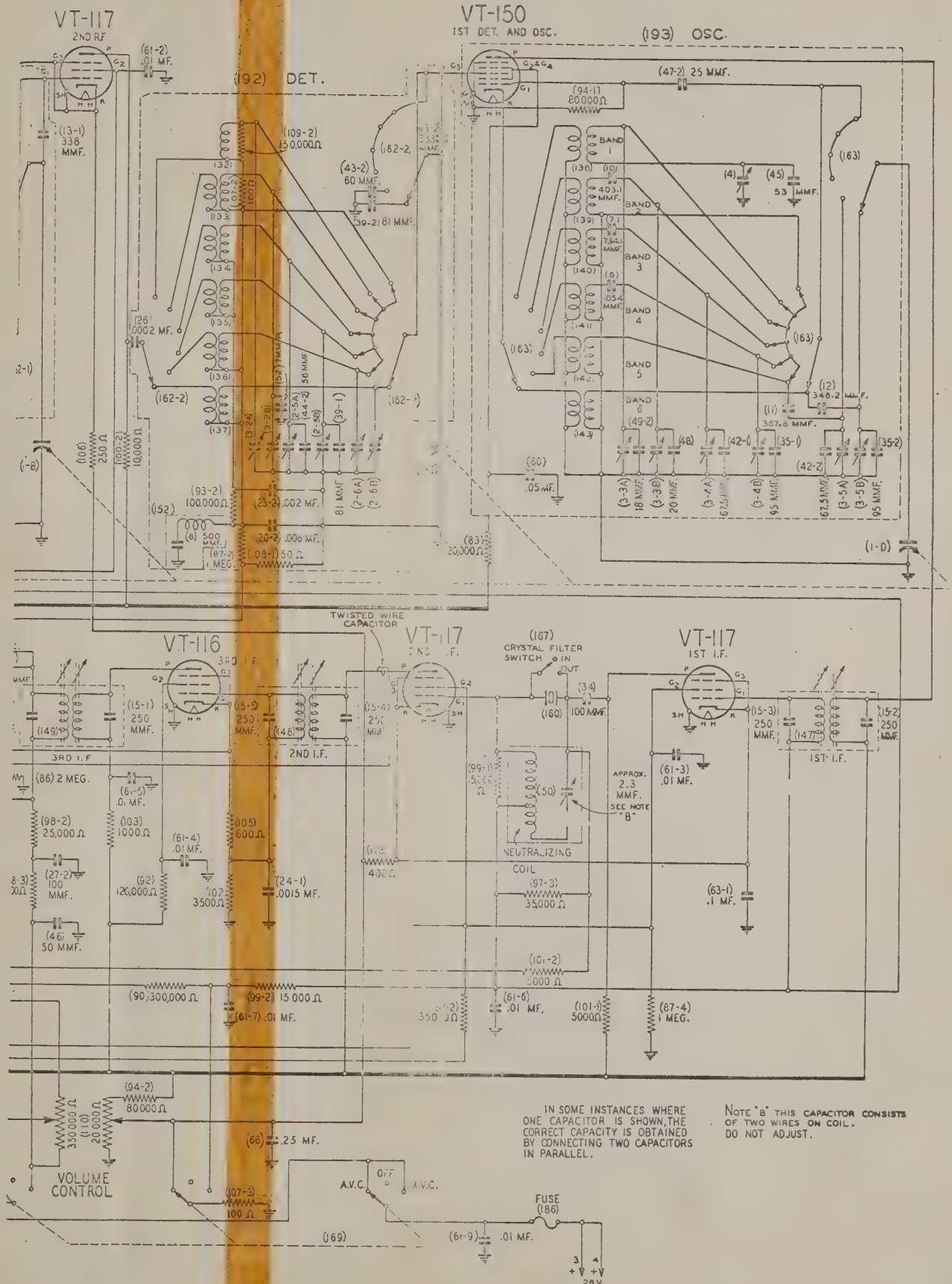


Figure 33 — Radio Receiver BC-348-Q Schematic Diagram

Revised 30 July 1945

ons

M-34, DY-2,
R-9/APN-4,
/ARC-4, RT-
22, SCR-528,
C-5, URC-4,


is book, sub-
is composed
the following
ons. APN-1,
VHF ARC-5,
22, BC-312,
348, BC-603,
BC-652, BC-
BC-728, BC-
94, BC-923,
BC-1206,
31, CRC-7,
-26, RAK-5,
CS, VT tube

lus out. They
Vanderventer
he first book,
ok, by Ken
and contains
about this
R-2, APS-13,
RC-5, ARC-5
RR-2, ART-
AR-231, BC-
2, BC-314,
75, BC-438,
11, BC-620,
53, BC-659,
33, BC-745,
9, BC-1000,
C-1335, BN,
3, DAE, F3,
7, I-208, JT-
-26, PRC-6,
RAS, RAX,
C-57, RDC,
SCR-284,

SCR-288, SCR-300, SCR-506, SCR-522, SCR-
578, SCR-585, SCR-593, SCR-608, SCR-610,
SCR-624, SCR-628, SPR-1, SPR-2, TBS, TBW,
TBX, TBY, TCK, TCS, TG-34, TS-34/AP,
TS-251/UP, VRC, VVX-1.

The other CQ book, the *Surplus Conversion Handbook* by Tom Kneitel K3FLL, (\$3) contains conversion on these pieces of gear: ARC-1, ARC-3, ARC-4, ARC-5, ARC-36, ARC-49, ART-13, ATA, ATC-1, BC-191F, BC-224, BC-312, BC-314, BC-343, BC-344, BC-348, BC-375E, BC-453, BC-454, BC-455, BC-457A, BC-458A, BC-459A, BC-603, BC-604, BC-620, BC-624A, BC-625A, BC-659, BC-669, BC-683, BC-684, BC-696A, BC-779, BC-794, BC-946, BC-1004, BC-1068A, CBY-52232, PE-73, PE-103, R-129/U, RAX-1, SCR-177, SCR-188, SCR-193, SCR-274N, SCR-399, SCR-499, SCR-508, SCR-509, SCR-510, SCR-522, SCR-528, SCR-542, SCR-608, SCR-609, SCR-628.

... WA1CCH

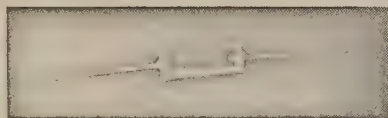

Cheap Coil or Choke Forms

Not liking to pay the price for Z-144's, I consulted the May '62 issue of 73, page 99, to obtain data for a 2 meter choke coil. The form size specified was $\frac{1}{16}$ inch, not a standard size around my shack. The cost of commercial forms of this size was out of the question (when you're as Scotch as I am). Next step: take a $\frac{1}{16}$ inch diameter polystyrene rod and cut a section to required length for winding the choke.

To make the form, prepare polystyrene rod as shown in the photo. Then hold section of polystyrene rod in vise or some other secure manner. Now take lengths of #18 or #20 wire, depending on strength desired in the leads. Place length of wire against end of polystyrene rod in center, carefully apply enough heat with soldering iron to cause the wire to penetrate deep enough into the polystyrene rod for good mechanical strength, then remove heat and let set. Repeat for other end.

After both lengths of wire are firmly set, wind desired choke. Care should be exercised in soldering coil wire to wire leads. A heat sink is recommended to avoid excessive movement of leads.

This inexpensive method of making rf chokes is used quite successfully at my QTH.

... Gary Smith WAØASA

HAMS

START MAKING BIG MONEY IN CB AND MOBILE-RADIO SERVICE!

TO LEARN HOW SEND FOR FREE BOOKLET BELOW!

Five million mobile radios need periodic maintenance and checks on frequency and modulation, by properly licensed and equipped servicemen. Your ham experience is the *ideal background* for getting into this profitable field—and the LAMPKIN 105-B is the *ideal frequency meter* to build your business around!

You can start off small—working part-time, with little investment, maintaining CB radios or local two-way systems—then build up to your own full-time high-profit business.

LAMPKIN 105-B FREQUENCY METER

Micrometer dial. Measures nearby transmitters, continuous coverage 100 KC to 175 MC and up. Internal calibrator. Only 8 lbs. \$295.00.

LAMPKIN 205-A FM MODULATION METER

Tunable 25 to 500 MC any channel. Direct reading. Light weight. Measures peak swing 0-12.5 and 25 KC. \$290.00. Quad-Scale model \$340.00.



MAIL COUPON TODAY!


LAMPKIN LABORATORIES, INC.

MFH Division, Bradenton, Fla. 33505

At no obligation to me, please send me free booklet "HOW to MAKE MONEY in MOBILE-RADIO MAINTENANCE"—and data on Lampkin meters.

Name _____
Address _____
City _____ State _____ Zip _____

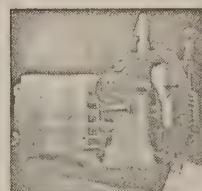LAMPKIN LABORATORIES, INC.
MFH-DIVISION, BRADENTON, FLORIDA 33505



Model TT35


for soldering irons, power tools, tv sets and many other uses. Thousands have been sold to US and foreign govts., armed services, police depts. etc. Fully guaranteed.

Only \$79.50 from: **Algert Sales Co.**
1805 Wilshire Blvd., L.A.

115V-350 WATTS AC

12 1/2 lb. GAS ALTERNATOR

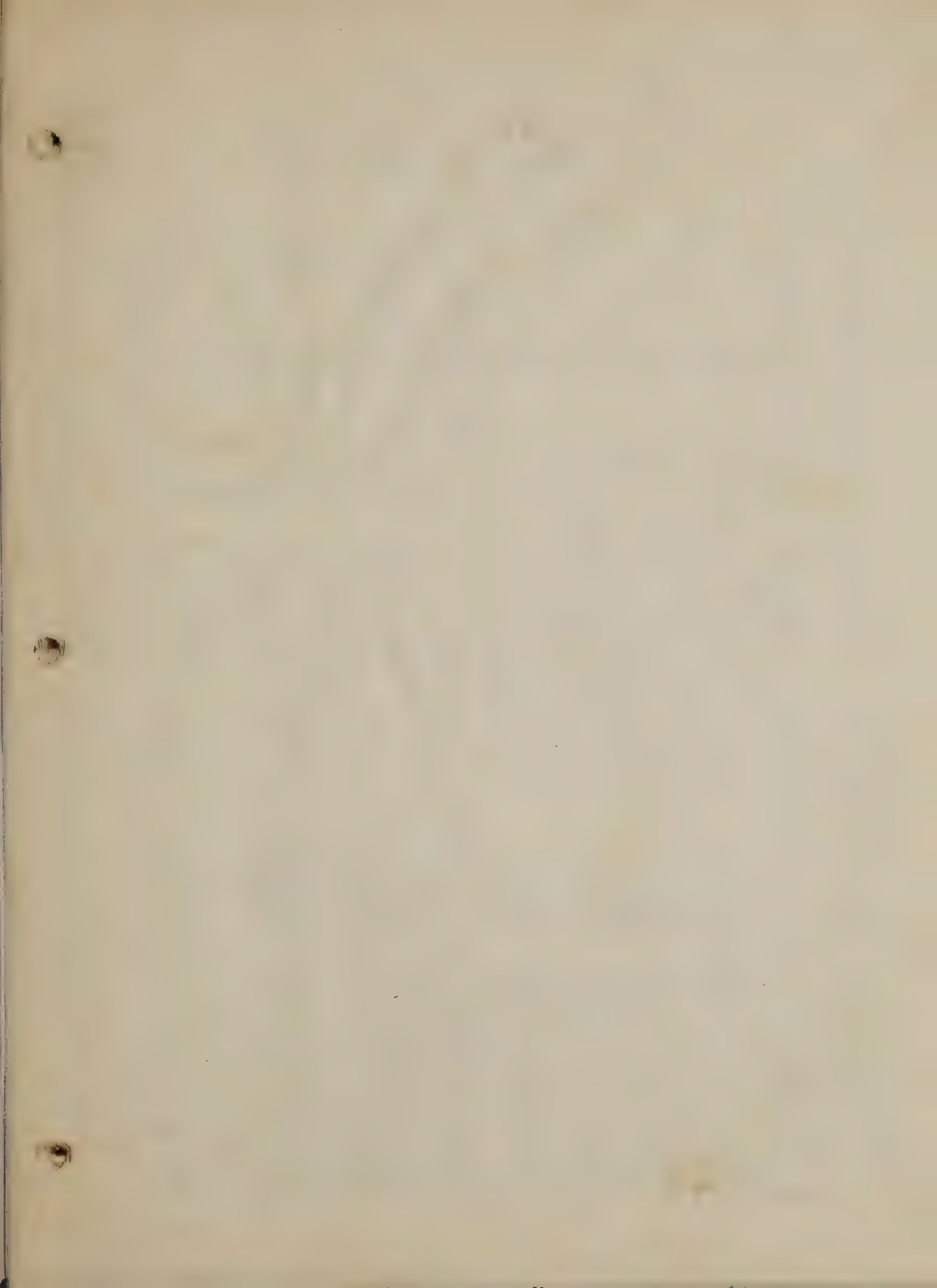Enough power to operate any popular SSB xmitter plus separate DC output to charge 6 and 12 volt batteries. Great for vacations, field days, campers, boats, etc. May be used



Paul Franson WA1CCH
Peterborough, N.H.

Guide to Surplus Conversions

Many articles have been written—and published—about surplus. These articles have ranged from simple suggestions to complete and detailed conversions such as the one by WA6BSO in this issue of 73. But these conversions are often hard to find; this is well demonstrated by the many articles on surplus that are duplications of other articles.

But it's not really that hard to find surplus conversions. Roy Pafenberg W4WKM has compiled a list of all the conversions he could find in the popular electronics magazines since World War II in the *Index to Surplus* available from many distributors or 73 for \$1.50. But the *Index* does not list the articles that have appeared in the various surplus *handbooks* that have been published. That's what this article is for. I've listed the pieces of equipment covered in the six surplus radio handbooks now available. The conversions differ greatly in completeness, so it's suggested that you take a look at any books of interest before you make big plans.

Editors and Engineers

Editors and Engineers, P.O. Box 68003, New Augusta, Indiana, have published three *Surplus Radio Conversion Manuals* by Even-son and Beach and the *Surplus Handbook, Vol. I* by W6NJV and W6NJE. Each costs \$3. Here are the pieces of equipment covered in each manual:

Surplus Radio Conversion Manual, Vol. I. BC-221, BC-342, BC-312, BC-348, BC-412, BC-645, BC-646, SCR-274 (BC-453A and BC-457A series), SCR-522, TBY, PE-103A, BC-1068A/1161A.

Surplus Radio Conversion Manual, Vol. II. BC-454, AN/APS-13, BC-457, ARC-5, GO-9/TBW, BC-946B, BC-375, LM, TA-12B, AN/ART-13, AVT-112A, AM-26/AIC, ARB.

Surplus Radio Conversion Manual, Vol. III. APN-1, APN-4, ARC-4, ARC-5, ART-13, BC-191, BC-312, BC-342, BC-348, BC-375, BC-442, BC-453, BC-455, BC-456-9, BC-603, BC-624, BC-696, BC-1066, BC-1253, CBY-

5200, COL-43065, CRC-7, DM-34, DY-2, DY-8, FT-241A, MD-7/ARC-5, R-9/APN-4, R-28/ARC-5, RM-52-53, RT-19/ARC-4, RT-159, SCR-274N, SCR-508, SCR-522, SCR-528, SCR-538, T-15 to T-23/ARC-5, URC-4, WE701A.

Surplus Handbook, Vol. I. This book, subtitled, *Receivers and Transceivers*, is composed of schematics and pictures of the following gear. It doesn't give conversions. APN-1, APS-13, ARB, ARC-4, LF and VHF ARC-5, ARN-5, ARR-2, ASB-7, BC-222, BC-312, BC-314, BC-342, BC-344, BC-348, BC-603, BC-611, BC-624 (SCR-522), BC-652, BC-654, BC-659, BC-669, BC-683, BC-728, BC-745, BC-764, BC-779, BC-794, BC-923, BC-1000, BC-1004, BC-1066, BC-1206, BC-1306, BC-1335, BC-AR-231, CRC-7, DAK-3, GF-11, Mark II, MN-26, RAK-5, RAX, RAL-5, Super Pro, TBY, TCS, VT tube cross index.

CQ Handbooks

CQ has two handbooks on surplus out. They can be ordered from CQ, 14 Vanderventer Avenue, Port Washington, N.Y. The first book, the *Surplus Schematics Handbook*, by Ken Grayson W2HDM, costs \$2.50, and contains schematics and short comments about this gear: APA-38, APN-1, APR-1, APR-2, APS-13, ARB, ARC-1, ARC-3, ARC-4, ARC-5, ARC-5 VHF, ARJ-ARK-ATJ, ARN-7, ARR-2, ART-13, ASB, AS-81-GR, ATK, BC-AR-231, BC-189, BC-191, BC-221, BC-312, BC-314, BC-342, BC-344, BC-348, BC-375, BC-438, BC-474A, BC-603, BC-610, BC-611, BC-620, BC-640, BC-645, BC-652, BC-653, BC-659, BC-683, BC-684, BC-728, BC-733, BC-745, BC-779, BC-794, BC-906, BC-969, BC-1000, BC-1004, BC-1023, BC-1206, BC-1335, BN, BP, C3, CRC-7, CRO-208, CRT-3, DAE, F3, GF-11, GO-9, GRR-5, I-122, I-177, I-208, JT-350A, LM, Mark II, MD-7, MN-26, PRC-6, PRS-3, R-174, RAK, RAL, RAO-7, RAS, RAX, RBH, RBL, RBM, RBS, RC-56, RC-57, RDC, RDR, RDZ, RU-16, SCR-274, SCR-284,

SCR-288,
578, SCR-
SCR-624, S
TBX, TBY
TS-251/UF

The other
Handbook
contains conv
ARC-1, A
ARC-49,
BC-224, I
BC-348, B
BC-457A,
(04, BC-6
BC-669, B
BC-794, B
52232, P
SCR-177,
SCR-399,
SCR-510,
SCR-608,

Che

Not lik
consulted
to obtain
form size
size aroun
forms of
(when you
take a 1/16
cut a sect
the choke.

To mak
as shown
polystyren
manner. N
depending
Place leng
rene rod
heat with
penetrate
rod for goo
heat and l

After b
wind desin
in solderin
is recomm
of 1/16 in
chokes is

Bibliography of Articles on Equipment for Frequencies of 50MC and Above

From CQ Magazine

Low Loss HF Superhet, BC 406	Feb. 1946
Lighthouse Preselector	March 1947
2 Meter Conversion of the 1068A	June 1947
Modification of the SCR522 for 2 Meters	July 1947
Increasing the Audio Output of the SCR522	May 1948
Lighthouse tube 420 Mc Transmitter	Sept. 1948
Low Noise VHF Converter	March 1949
More on VHF Converters	Nov. 1949
Putting the SCR522 on 6 Meters	Feb. 1949
Improving the BC624 Noise Limiter	July 1949
2 Meter R-9'er	Dec. 1949
Ultimate in Converters	Sept. 1949
Wide Range VHF Converters	Aug. 1949
The 6 and 2	May 1949

Putting Surplus to Work on the 420 Mc Band	Feb. 1950
More Gain with 30 Elements	Nov. 1950
Simplicity on Six	Sept. 1950
Walkie-Talkie for 144 Mc	May 1950
Wide Spread Twin Five	March 1950
Zig-Zag Array (Vertical Polarization)	June 1950

From QST Magazine

Compact Superhet for 144 Mc	Oct. 1947
420 is Fun	Nov. 1947
Improved Receiver for 2 Meters	March 1947
Lets Start Right on 1 1/4	Dec. 1947
Low Cost 6 Meter Fone	March 1947
Low Cost 2 Meter Transmitter	April 1947
Operating the BC 645 on 420 Mc	Feb. 1947
Put Em' Push-Push	Jan. 1947
Practicle Crystal Control for 144 Mc Mobile Operation	Oct. 1947
2400 Mc Oscillator Cavity	Oct. 1947
VHF Crystal Oscillator	Nov. 1947
Adapting the Cathod Coupled Preamplifier to 144 Mc (H & K)	Aug. 1948
Band Pass Converter for 144 Mc	Jan. 1948
Better Reception for 2 Meter Mobile	April 1948
Coaxial Line Receiver for 220 Mc	June 1948
Coaxial Line VHF Receivers	March 1948
Compact 20 Watt Rig for 50 Mc	April 1948
Crystal Control on 220 Mc	May 1948
Fun on 420 with the BC788	July 1948
Grounded Grid Technique on 50 Mc	Feb. 1948

II (Continued)

High Power on 220 Mc	Aug. 1948
Hot Converter for 220 Mc	Oct. 1948
Mobile Midget for 144 Mc	Feb. 1948
Novel Converter for 144 Mc	Sept. 1948
Operating the APS13 on 420 Mc	May 1948
Oscillator for the 1215 Mc Band	April 1948
Simple Crystal Control on 144 Mc	Oct. 1948
So It's Hard to get on VHF	Nov. 1948
Tripling to 420	June 1948
VHF Mans VFO	
ABFO for the 522 Receiver	June 1948
Improved 144 Mc Reception (SCR522)	Sept. 1948

Better Results with the 522	April 1949
Cascode Converter for 144 MC	June 1949
City Slicker Array for 144 Mc	Nov. 1949
Compact Converter for 6 & 10	Feb. 1949
Doorknob Oscillator for 420 Mc	Jan. 1949
Making the Higher Frequencies Pay Off	Jan. 1949
Noise Generator Technique for the VHF Man	Aug. 1949
Simple Gear for the 420 MC Beginner	May 1949
Simple System for 2 Meter NFM	Jan. 1949
Simplicity on 6	Aug. 1949
Using the Cascode on 50MC	March 1949
VHF Sandwich	June 1949
450 Watts on VHF	Sept. 1949
6J6 as a Doubler	Jan. 1949

Two Unusual 144 Mc Antennas	Dec. 1950
Mobile Converter for 144 Mc	Aug. 1950
Utilizing the 826	May 1950
AVHF Frequency Meter	Oct. 1950
2 Meter Station for the Novice	Feb., March & April 1950
Better Results on 420	Aug. 1950
Compact 2 Meter Station for Mobile Use	May 1950
Crystal Controlled Converters for VHF	Sept. 1950
Using the BC-221 Frequency Meter at VHF	Jan. 1950

It will be noted that this Bibliography is incomplete due to the fact that not all issues of CQ Magazine were available. Also this list does not include any references from Radio News or Electronics which contain many articles of merit on VHF equipment. Also articles in the ARRL Handbooks and Radio Handbooks are not listed in this Bibliography.

1941
1942
1943
1944
1945
1946
1947
1948
1949
1950

1951
1952

1953
1954
1955
1956
1957
1958
1959
1960

1961
1962
1963
1964
1965
1966
1967
1968

1969
1970
1971
1972
1973
1974
1975
1976
1977
1978
1979
1980

1981
1982
1983
1984
1985
1986
1987
1988
1989
1990
1991
1992
1993
1994
1995
1996
1997
1998
1999
2000

\$ 2.00 per year

all

Franklin Park

2433 24th Ave

VHF 1000

View of the LR-1 direct reading frequency meter, in use. Note that the two coaxial connectors to the left and right of the meter have been changed to BNC fittings.



THE LR-1

FREQUENCY METER

BY SAM KELLY,* W6JTT

The author describes how to get the LR-1 working and how to operate it. This fine direct reading frequency meter is becoming available on the surplus market in greater quantity.

ONE of the few interesting surplus items to reach the ham market in the past year is the LR-1 frequency meter. It is very attractive to the ham since in addition to its heterodyne frequency meter function it will generate and measure audio frequency up to 5.5 kc and provide crystal calibrator outputs of 10, 20 and

accuracy is specified as $\pm 0.003\%$ to 30 mc. A multiplier chart is supplied for use of harmonics up to 60 mc.

To place the LR-1 in operation remove the cover from the terminal and filter assembly and connect 115 v. 60 cycles to the terminals marked "60." These terminals should have a green and a green/yellow wire connected to them. Install fuse F_{101} in the fuse clips whose voltage markings most closely approximate the line voltage in your shack. The r.f. input and output connectors are impossible to match and should be replaced with BNC type UG-604/U.

*12811 Owen Street, Garden Grove, California 92641.

Operation of the LR-1 is more involved than using a LM or BC-221. It is a direct reading instrument requiring no calibration book, but the operation is unique.

Crystal Calibrator

The calibrator consists of a 100 kc crystal oscillator accurate to one part in 10^5 . A capacitor is provided for adjusting the oscillator against a primary standard such as WWV or WWVH. This adjustment (C_{102}) shouldn't be touched unless it is necessary. If you do adjust the oscillator use an oscilloscope to compare the beat notes—don't rely upon your ears.

Locked to the crystal oscillator is an astable multivibrator which provides 10 and 20 kc calibration markers. To determine if the multivibrator is properly dividing the 100 kc signal proceed as follows:

Remove amplifier tube V_{102} . Place the CALIBRATOR switch in the 100 kc position. Using the heterodyne frequency meter direct reading dial check for the 200 kc harmonic. It should be with-

**"HOW TO MAKE MONEY
Mobile Radio Maintenance"**

AUTHORITATIVE GUIDEBOOK
ABOUT THE BOOM IN TWO-WAY MOBILE-RADIO:
GIVES FACTS, FIGURES, PAY RATES.
WRITE TODAY! **FREE**

LAMPKIN LABORATORIES, INC. Electronic Division BRADENTON, FLA.

**LET W3KT forward your
DX QSLs**

QSLs forwarded promptly to foreign QSL
Bureaus, QSL managers, or, if necessary,
direct to DX station.

Three cents each or 36 per dollar

First Class Mail • No Membership Fee
Save Time! • Save Money!

W3KT QSL SERVICE
RD 1, Valley Hill Road • Malvern, Pa. 19355

For further information, check number 22, on page 110

**LARGEST SELECTION IN UNITED STATES
AT LOWEST PRICES — 48 HR. DELIVERY**

**JAN
CRYSTALS**

Thousands of frequencies in stock.
Types include HC6/U, HC18/U,
FT-241, FT-243, FT-171, etc.
Send 10¢ for catalog with oscillator
circuits. Refunded on first order.
2400A Crystal Dr., Fort Myers, Fla. 33901

FREE!

**BIGGER... BETTER
THAN EVER!**

**40th ANNIVERSARY
1967 CATALOG**

**YOUR BUYING GUIDE
FOR:** • Stereo & Hi-
Fi Systems & Com-
ponents. • Tape Re-
corders. • Electronics
Parts, Tubes, Tools.
• Phonos & Records.
• Ham Gear. • Test
Instruments & Kits.
• Cameras & Film.
• P.A. • Citizens Band.
• Radio & TV Sets.
• Musical Instruments

**SEND FOR
YOURS TODAY!**

BURSTEIN-APPLEBEE CO.

Dept. CQ, 1012 McGee, Kansas City, Mo. 64106
☐ Rush me the FREE 1967 B-A Catalog.

Name.....
Address.....
City..... State..... Zip Code.....

For further information, check number 23, on page 110

in ± 1 kc of the 200 kc dial marker. If not, adjust R_{114} until it is. Replace V_{102} and allow the tube to warm up. Place the RANGE SELECTOR switch in the 1.33—1.87 mc range. Vary the HFM tuning control noting the dial reading on two successive 100 kc harmonics. Place the CALIBRATOR switch in the 20 kc position and count the number of zero beat points between the two 100 kc readings. It should be five. If not, adjust R_{113} until it is. Repeat the above procedure for the 10 kc position adjusting R_{112} until there are ten zero beat points between the two 100 kc readings.

To use the crystal calibrator for external measurements turn the CALIBRATOR switch to the desired range and place the DETECTOR INPUT switch in the MEASURE position. It may be necessary to move the HFM tuning control to eliminate spurious beat notes.

Heterodyne Frequency Meter

The heterodyne frequency meter (H.F.M.) consists of a Colpitts oscillator operating on seven fundamental ranges. Scales with black masks are fundamental ranges while the red masks are harmonic ranges. The COMPENSATOR control is provided for zero beating the H.F.M. with the crystal check points. The interpolator scale test control provides a smoothly controllable change in frequency without the need of disturbing the main tuning control. This is useful in determining the sense of the beat note. Turning this control will reduce the H.F.M. frequency.

Placing the detector input switch in the MEASURE position allows you to adjust the H.F.M. against the crystal calibrator. Also, in this position, the difference in frequency between an unknown signal applied to the r.f. input connector and the crystal calibrator is directly read out on the interpolator dial. The sense (whether the signal is above or below the check point) is determined by means of the INTERPOLATOR SCALE TEST control. As an example, say you zero beat the H.F.M. against the crystal calibrator at 5.120 mc (calibrator in the 20 kc position). An unknown signal is fed in and meter M_{101} reads 6 kc on the lower scale. Turning the INTERPOLATOR SCALE TEST control you observe that the reading on M_{101} drops. This indicates that the H.F.M. is above the unknown signal and therefore the signal is 5.114 mc.

Placing the detector input switch in the MATCH position permits you to zero beat the H.F.M. with an external unknown frequency.

Measuring Audio Frequencies

The LR-1 can be used as an audio frequency meter by connecting the unknown signal to J_{103} (INTERPOLATOR INPUT). Use a standard phone plug and connect the hot side to the tip. The input is a high impedance (about 500K ohms). Place the interpolator scale selector switch in the lower position and read the audio frequency directly from the lower scale.

[Continued on page 102]

Front view of the
are, from 1. to 10
#2, CALIBRATOR

An
Rec
BY EL

HERE is
from
input
controlled co
bands. No fil
cuit to reject
tunes the 80
and the se
this range pr
enough reject

The ante
into the 3.5-
coil of the
tube. It is v
to prevent p
feeding con
it. The input
mc i.f. trans
both the p
secondary
variable cap
output sign
mixer is fed
the mechanid
then amplifi
stages of i.f.
is then fed t
detector and
audio amplifi

Product E

When th
build this rec
I decided to
It would ind
of the art" c
ered from the
azines. Since
circuits desd

*52a Colima

Fig. 1 (A) Cir
if no power s
type but using
i.f. transform
push-pull typ
output. All th
b

The LR-1 [from page 28]

Generating Audio Frequencies

Audio frequencies in the range of 0 to 5.5 kc can be derived from the calibration oscillator and the H.F.M. Place the CALIBRATOR switch in the 20 kc position. Place the H.F.M. in range 1 (160 to 232 kc). Place the DETECTOR INPUT switch in the MEASURE position. With the interpolator test switch in the lower position adjust the H.F.M. frequency control to zero beat with any harmonic of the calibration oscillator near the middle of the band. Advance the H.F.M. frequency control and read the audio frequency from the lower scale of M_{101} . The audio output is obtained from the telephone jacks J_{101} or J_{102} . ■

20 Meter Yagi [from page 78]

most complicated detail of the yagi assembly, it is still a relatively simple task. Any medium spaced capacitor with about 100mmf value will work well. It is important, however, that the rotor plates have a full 360 degree motion and the capacitor circular motion have only the slightest degree of drag. In the original installation, an old ARC-5 tuning capacitor with several plates removed worked perfectly. Since the capacitor is series installed it is important that the unit be insulated above the boom ground potential as well as being insulated from the synchronous motor. The capacitor frame is placed on a sheet of polystyrene and the shaft series insulated from the motor shaft with a short length of dowel or a flexible coupling and fibre shafts. If dowel is used each dowel-end is drilled with the proper diameter bit in order to slip snugly onto the respective shafts. A small amount of Duco cement more than adequately secures the units.

The synchronous motor is the standard 110 v.a.c. unit with about 1-2 r.p.m. The rather slow movement will allow for an accurate determination of the lowest s.w.r.

The input end of the circuit can either utilize a standard coaxial connector or a porcelain feed-through insulator. Neither one offers any particular advantage. The gamma matching rod is soldered to the center of the mating PL-259 connector. No connection is made to the shell of the plug. Use an insulated length of #12 or #10 copper wire terminated 42" from the driven element center for the 50 ohm terminus along the element length. All internal Minibox connections are made with a similar gauge. Simply solder one lead to the stator and the other lead to the rotor section.

For the gamma rod support, a 1×6" length of polystyrene is fastened on the driven element about midway along the gamma rod's length. A small (1") clamp secures the support and insulator. At the other end drill a small hole and tie the rod to the insulator with a small piece of twine. At the far end of the gamma rod (42" point) bend a length of copper sheeting around the terminus point and secure with a nut and

bolt. At the far end of the sheeting (6") solder the gamma rod to the copper stock to complete the installation. These details are shown in fig. 2.

The extra length boom presents a support problem; consequently, the need for a length of nylon rope support. About midway along the length of the boom extensions secure a clamp for the support tie point and install a turnbuckle for any subsequent sag adjustments. A mast extension of about 3-4' is adequate.

Final Adjustment

Coat all joints with Krylon spray to assure a continuation of low resistance inter-element conductivity and a consistent impedance load. Make all final measurements with the antenna at its normal operating height. Connect power to energize the motor-capacitor drive. For those with a remote rotor installation, remove two wires from the rotor cable at the tower and jump them to the drive motor. Remove the same two wires (follow color code) at the control panel. Remember the rotor is now inoperative but it does eliminate the burden of stringing a temporary line. Experience has shown the antenna to reflect a rather constant input characteristic, so a permanent line to the synchronous motor is not really an absolute necessity. The amateur can either adjust the system for maximum signal detection (from a known and stable source using an S-meter) or simply concentrate on the lowest s.w.r. value. Expect a ratio of 1.5:1 or less and a front-to-back ratio in excess of 35 db with a properly tuned unit at a moderate height.

Every care has been taken to insure an inexpensive yet rugged antenna system comparable to the finest commercial counterparts. Even in the extreme cases of low antenna heights and adjacent power absorbing obstacles, the system will cancel out the reactance factor and produce a signal worthy of the serious amateur antenna builder. ■

Radio Club [from page 17]

visitors applying for foreign membership are required to pay a "small cup round table". This means the purchase of a small cup of coffee for each member present at the meeting where the applicant is introduced. The cost usually amounts to about \$2.

Radio amateurs visiting Helsinki are cordially invited to attend the daily meetings of the Café de Colombia Radio Club, and take part in the club's activities. This is an excellent opportunity to enjoy luncheon with members of the world's most active radio club. Radio amateurs interested in becoming members of the Club, can obtain additional information as well as a list of present members from: Café de Colombia Radio Club c/o SRAL, Box 10306 Helsinki 10, Finland. ■

Transistorized Converters [from page 40]

recovery computer diodes make even better multipliers, usually with lower resistor values than the 82K value shown in fig. 4. This resistor can

be connected across the capacitor can be fixed unit of these are less t

Any of these received signals diode noise generator alignment. The ways produces i.f. receiver output all circuits should weak signal receiver

A.M. For SB-1

Before going on, another in Push in the A.M. CARRIER-NULL C instructions. On for a.m. and the should seldom receive Initial receive made by adjusting page 88 of the r


The


Referring to fig. A.M. position and the carrier generator LEVEL control to maximum normal at the 1st i.f. amplifier band filter. On the diode switch, CR the carrier generator from the CARRIER same time, the envelope detector

A small size cou the output of the low-frequency a.f. a "muddy-sounding" narrow bandwidth. With the new swing transmit, the connected from the grounded to prevent At the same time, is disconnected from is connected to the a.f. amplifier.

30 Again [from page 40]

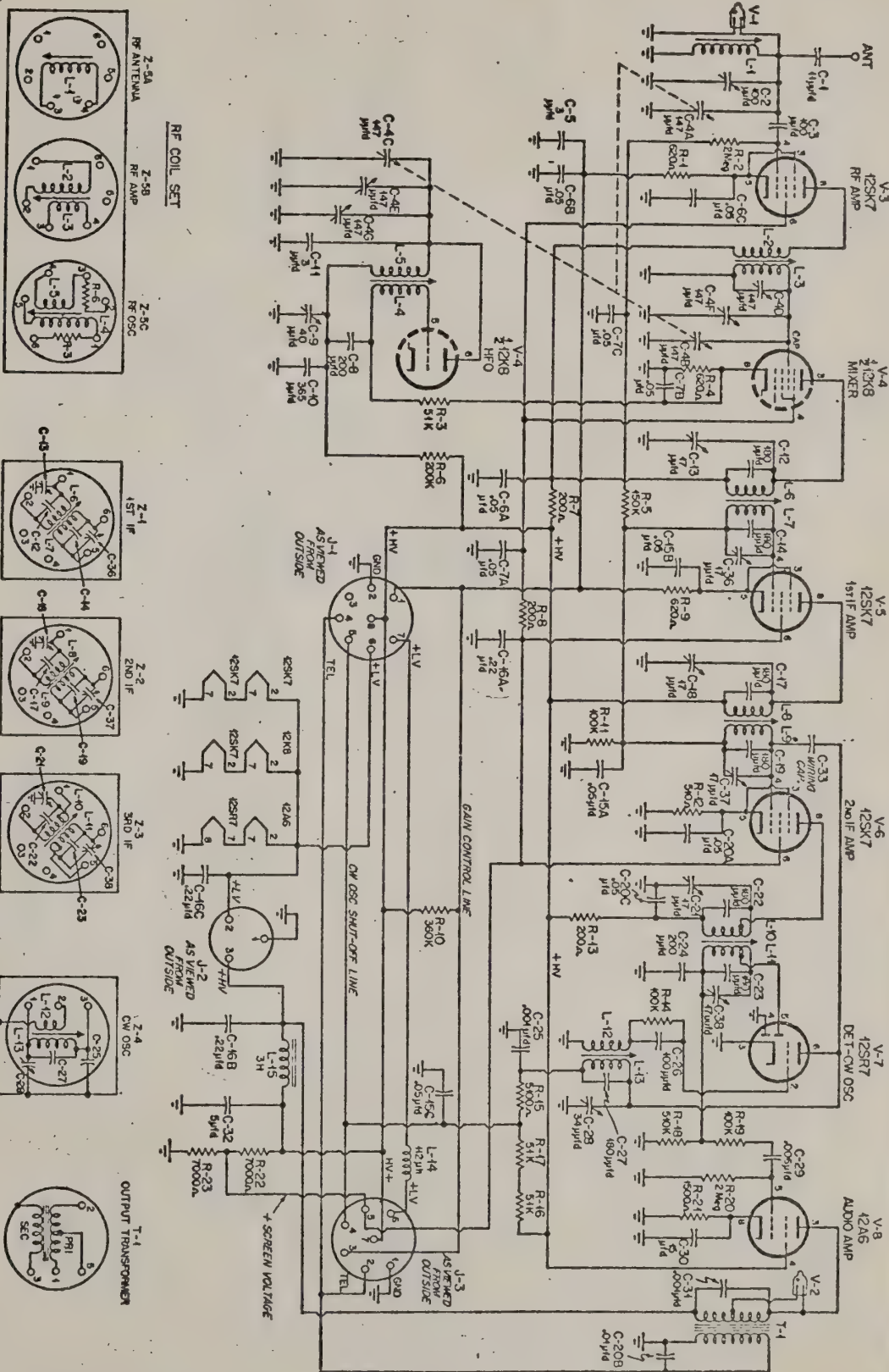as it was the standard on the continent of communication control would henceforth use national code. Look in the International dah dah—dah dah one fast and make it the same characters International code, c




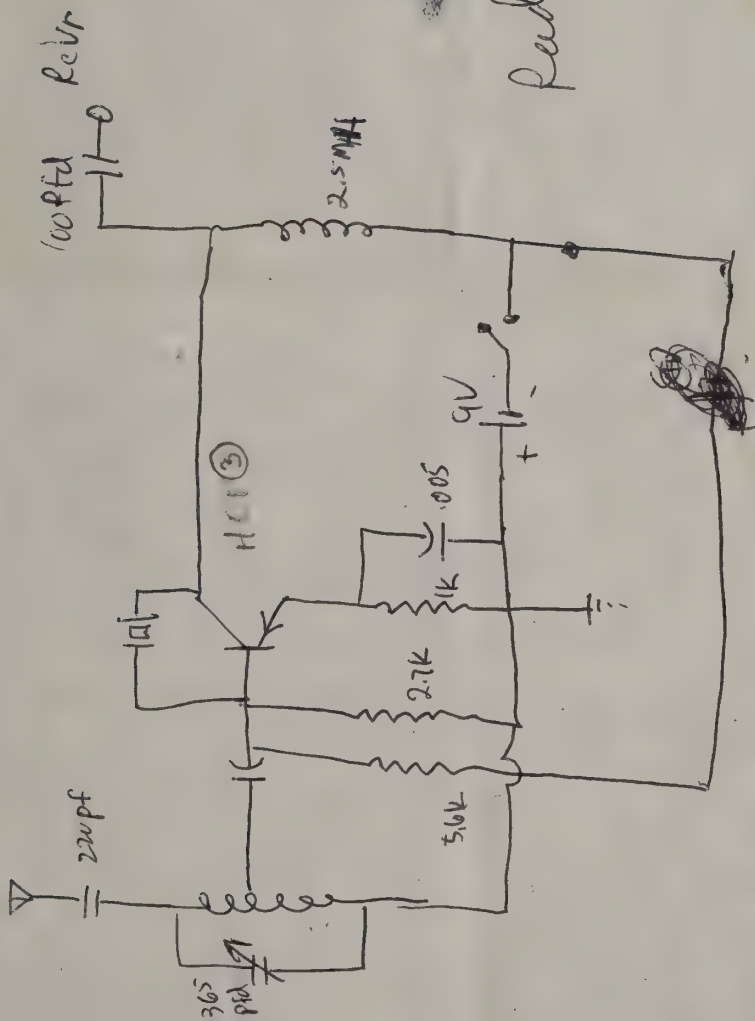


Radio Elec

Mar 1970


Page 50 - 52

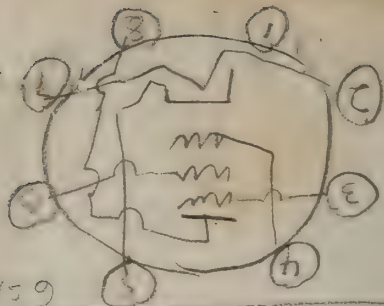

6547 5N

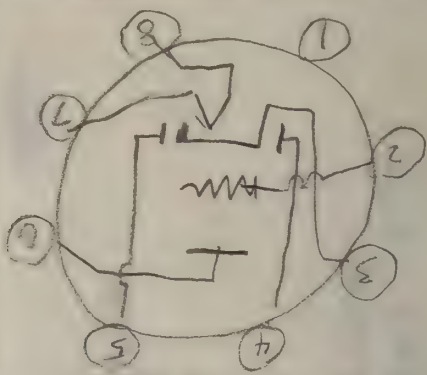

6547 8Q

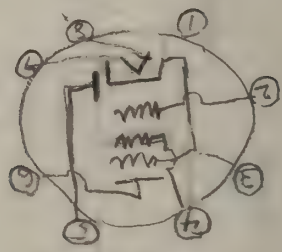

check marks cut off parallel

7A2 (6SF 7)

125F7

- 10

125K7

(6) Plate

were to

(8)

(5) deep

were to ~~be~~ ^{the end} ~~the end~~ ^{the end}

(5+3)

(4) Screen

were to

(6)

(3) Carboys

were to

(5) (5)

(2+5) Rel

were to

(2) (4) (5)

(1) Shells


were to

(1)


(2) grid

were to


(4)

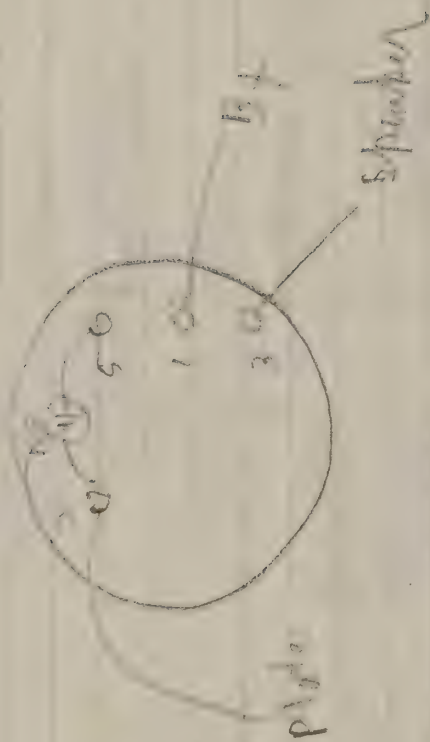

2-4x 2 5 28

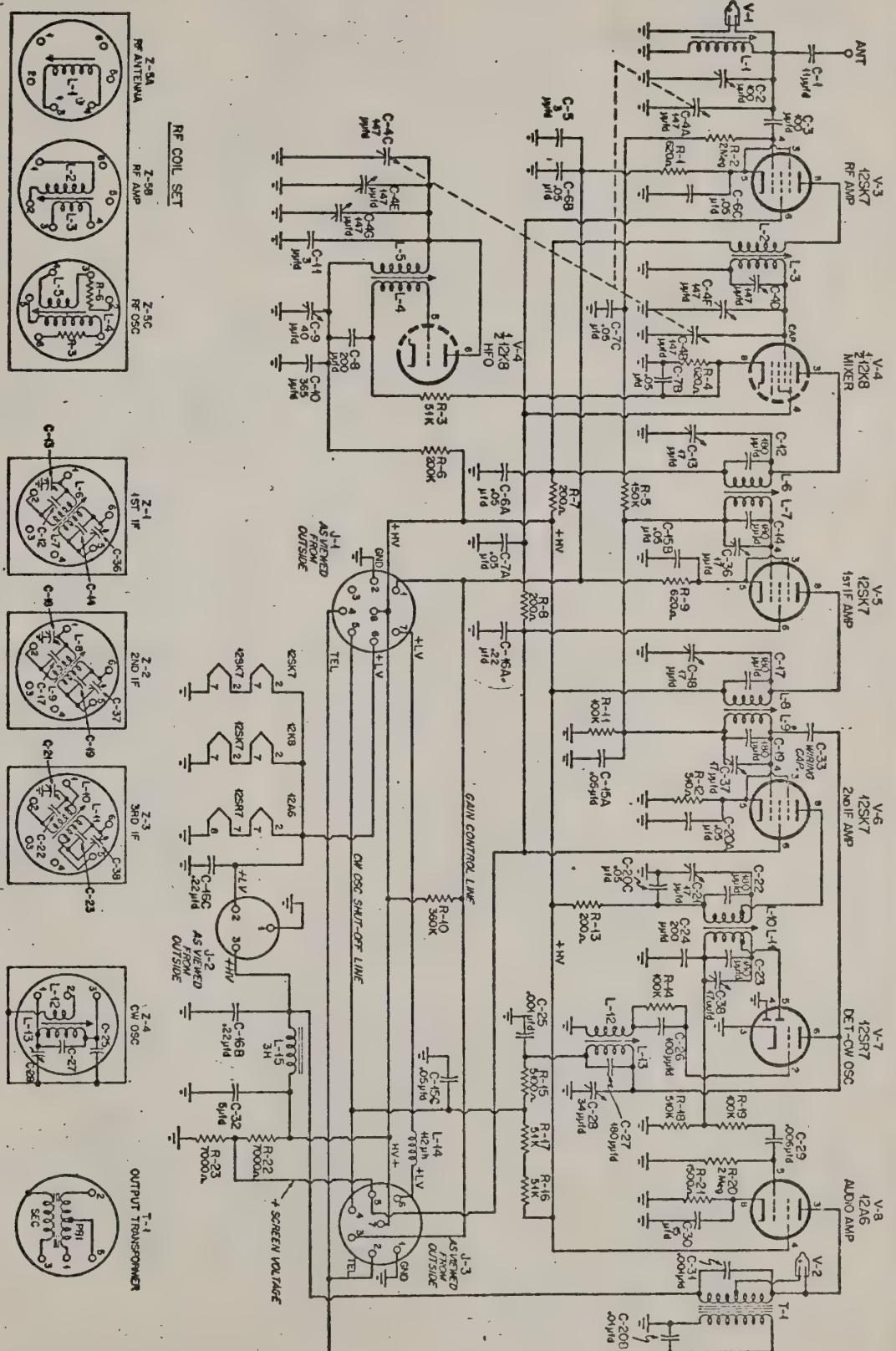

12A6
AUDIO AMP
(VT-134)

 

TO TUBE V2


OUTPUT TRANSFORMER

RADIO RECEIVER BC-454-A


2

PRL

1

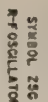SYMBOL Z68
RTAMPLIFIER



SYMBOL 23A
R-F ANTENNA

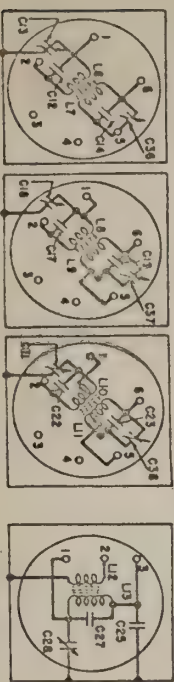

SYNBOC 2
CW OSCILL

1708

AS VIEWED FROM OUTSIDE

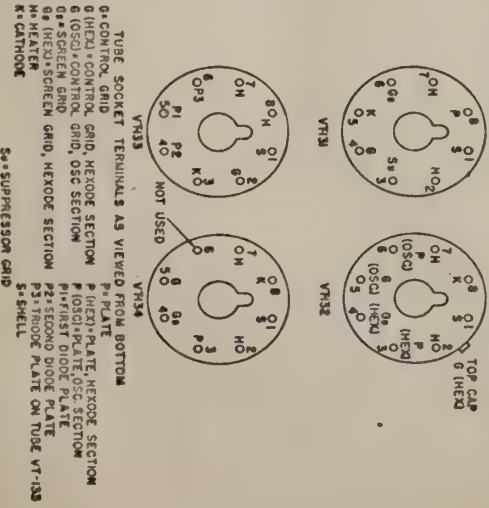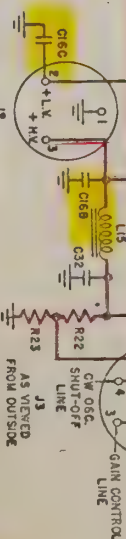

IF COUPLING UNITS
CIRCUITS IN A
COIL SET, IF COUPLING UNITS, TWO-BOLELEATOR, AND OUTPUT TRANSFORMER.
THE TERMINAL
NUMBERS ON THESE UNITS AGREE WITH THOSE SHOWN AT THE CORRESPONDING
LOCATIONS ON THE PRACTICAL WIRING DIAGRAM.

WIRING CAPACITANCE (LESS THAN 2 MIN.)

RADIO RECEIVER BC-454-A (OR -B) (3-6 MC) SCHEMATIC

12KE

R-F AMP
(VT-121)

12KE

FIRST I-F AMP
(VT-121)


SECOND I-F AMP
(VT-121)

DET-OSC OSC
(VT-121)

AUDIO AMP
(VT-24)

12SF7

12A6

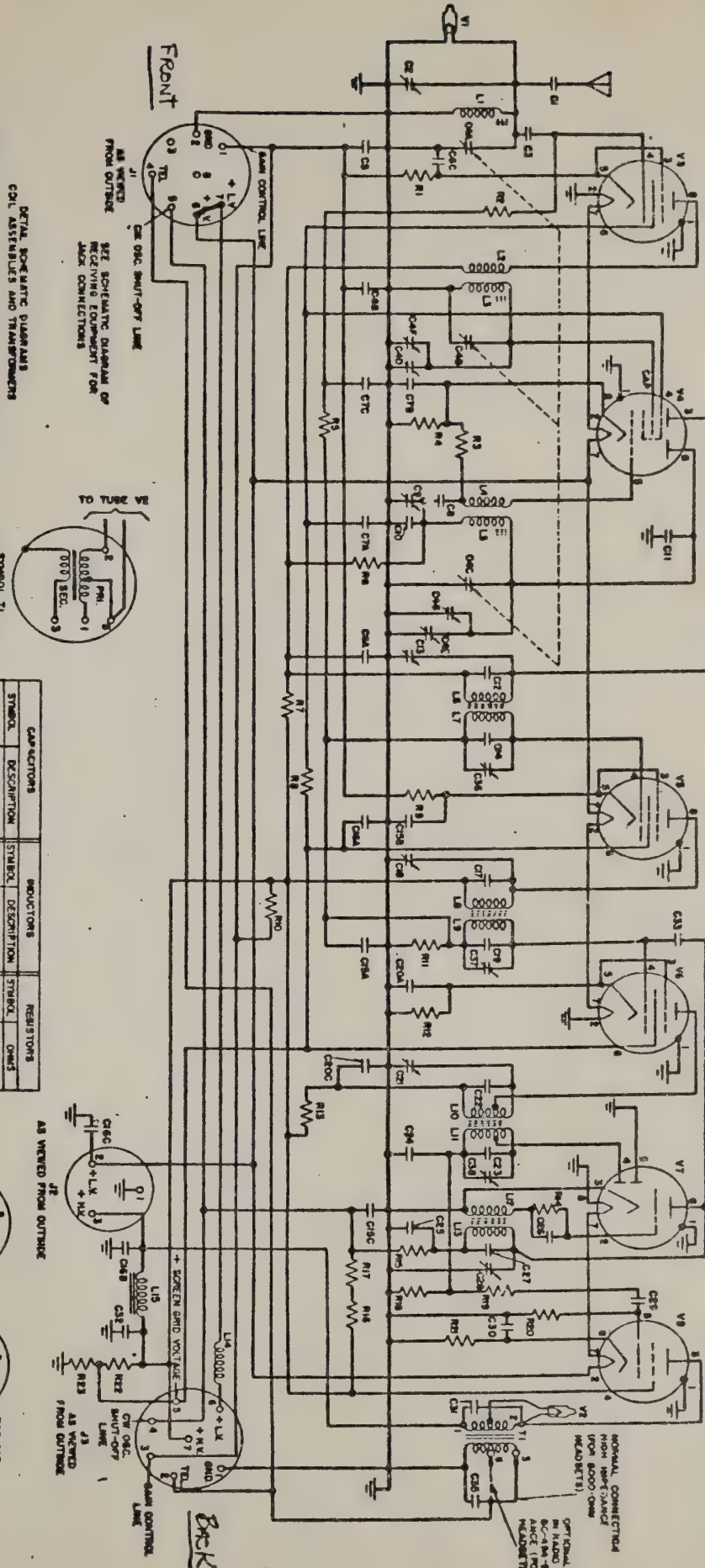

DET. OSC. SHUT-OFF LINE


TO TUBE

TO TUBE


TO TUBE

TO TUBE

TO TUBE

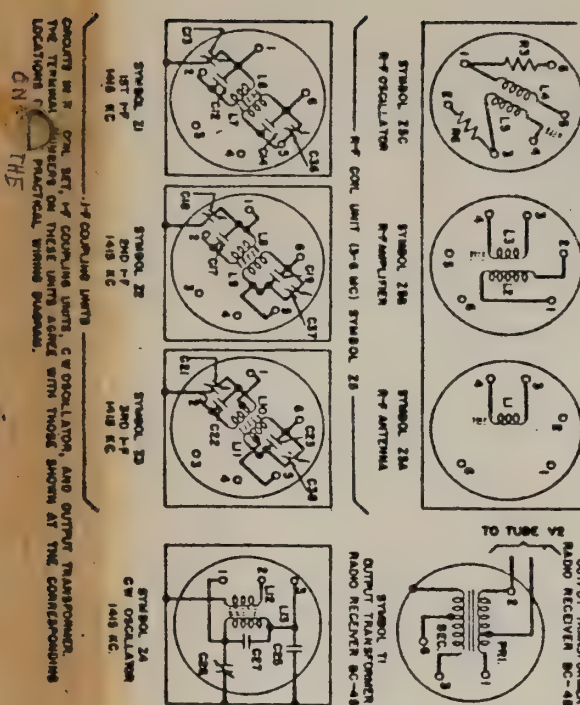

SYMBOL	DESCRIPTION	SYMBOL	DESCRIPTION	SYMBOL	VALUES
C1	15 MUF	L1	1.5 M	R1	500,000
C2	15 MUF	L2	1.5 M	R2	500,000
C3	15 MUF	L3	1.5 M	R3	500,000
C4	15 MUF	L4	1.5 M	R4	500,000
C5	15 MUF	L5	1.5 M	R5	500,000
C6	15 MUF	L6	1.5 M	R6	500,000
C7	15 MUF	L7	1.5 M	R7	500,000
C8	15 MUF	L8	1.5 M	R8	500,000
C9	15 MUF	L9	1.5 M	R9	500,000
C10	15 MUF	L10	1.5 M	R10	500,000
C11	15 MUF	L11	1.5 M	R11	500,000
C12	15 MUF	L12	1.5 M	R12	500,000
C13	15 MUF	L13	1.5 M	R13	500,000
C14	15 MUF	L14	1.5 M	R14	500,000
C15	15 MUF	L15	1.5 M	R15	500,000
C16	15 MUF	L16	1.5 M	R16	500,000
C17	15 MUF	L17	1.5 M	R17	500,000
C18	15 MUF	L18	1.5 M	R18	500,000
C19	15 MUF	L19	1.5 M	R19	500,000
C20	15 MUF	L20	1.5 M	R20	500,000

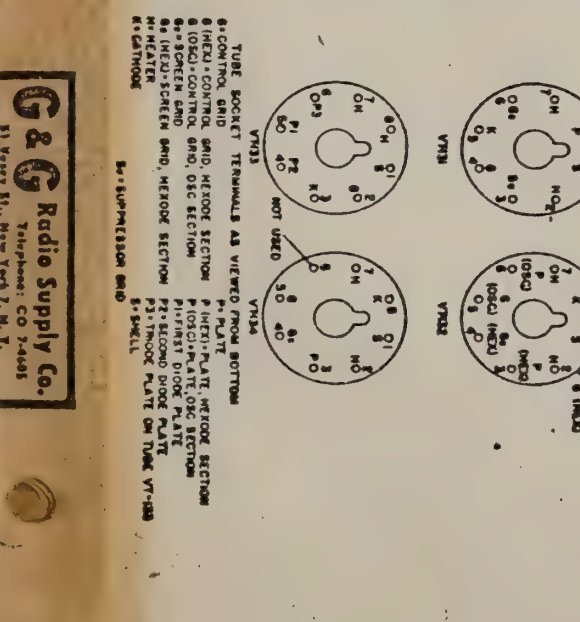

LESS THAN

G & G Radio Supply Co.
31 West 51st St., New York 7, N. Y.
Telephone: CO 7-4495

10-10-1941

10-10-1941

10-10-1941

10-10-1941

10-10-1941

10-10-1941

RADIO RECEIVER BC-454-A (OR-B) (3-6 MC) SCHEMATIC

12K6

12A6


12SF7

12A6


12SF7

12A6


12A6

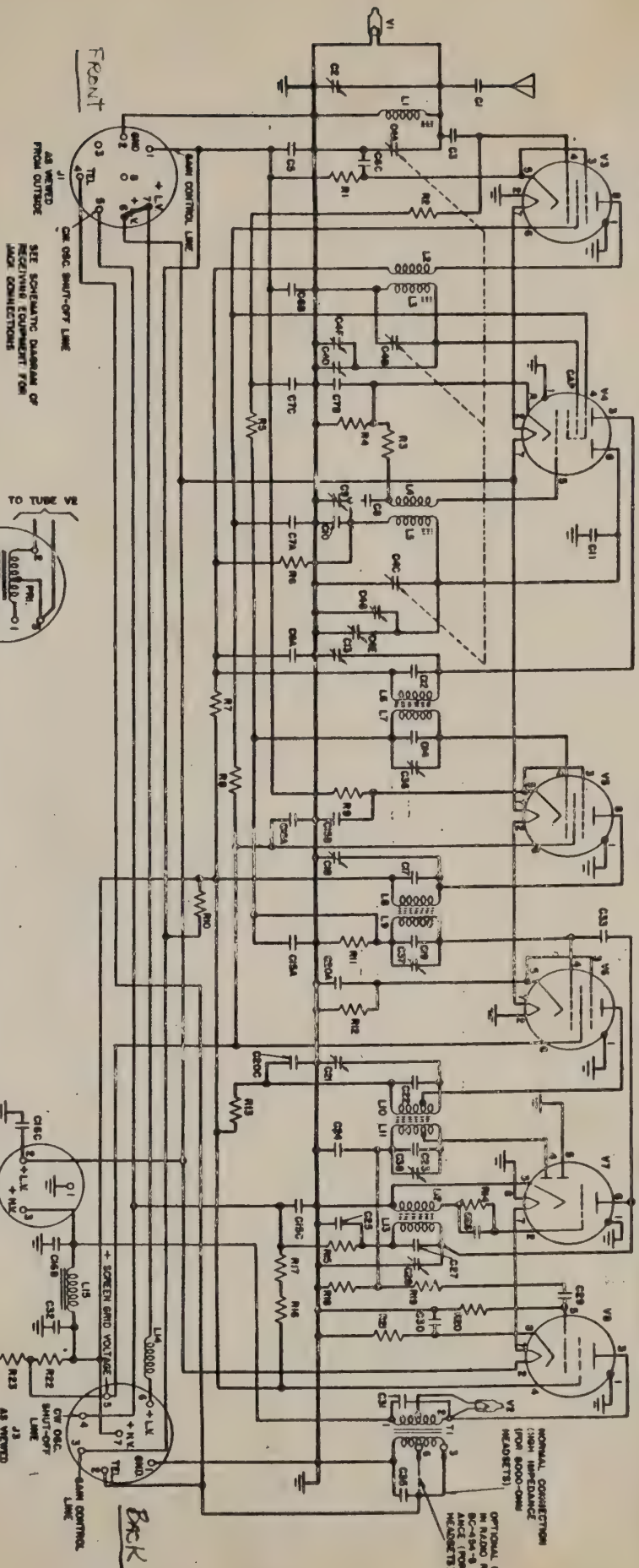

COIL ASSEMBLIES AND TRANSFORMERS

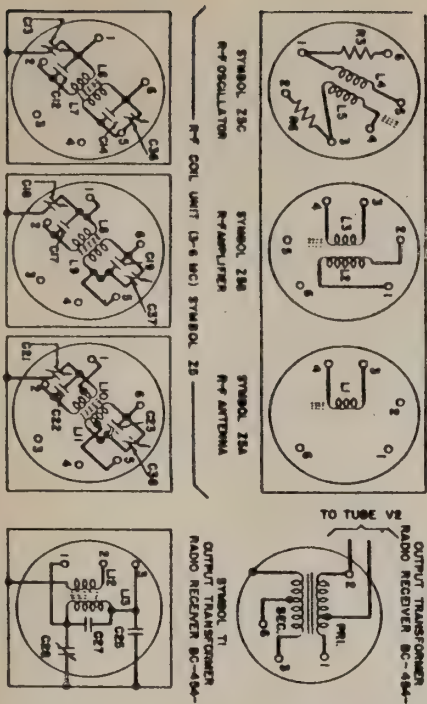


SYMBOL	DESCRIPTION	SYMBOL	DESCRIPTION	SYMBOL	VALUES
C1	11 MUF	L1	ANT. INPUT	R1	650
C2	12 MUF	L2	RF AMP.	R2	200,000
C3	13 MUF	L3	IF AMP.	R3	650
C4	14 TO 15	L4	IF AMP.	R4	650
C5	16 TO 17	L5	IF AMP.	R5	650
C6	18 TO 19	L6	IF AMP.	R6	650
C7	20 TO 21	L7	IF AMP.	R7	650
C8	22 TO 23	L8	IF AMP.	R8	650
C9	24 TO 25	L9	IF AMP.	R9	650
C10	26 TO 27	L10	IF AMP.	R10	650
C11	28 TO 29	L11	IF AMP.	R11	650
C12	30 TO 31	L12	IF AMP.	R12	650
C13	32 TO 33	L13	IF AMP.	R13	650
C14	34 TO 35	L14	IF AMP.	R14	650
C15	36 TO 37	L15	IF AMP.	R15	650
C16	38 TO 39	L16	IF AMP.	R16	650
C17	40 TO 41	L17	IF AMP.	R17	650
C18	42 TO 43	L18	IF AMP.	R18	650
C19	44 TO 45	L19	IF AMP.	R19	650
C20	46 TO 47	L20	IF AMP.	R20	650
C21	48 TO 49	L21	IF AMP.	R21	650
C22	50 TO 51	L22	IF AMP.	R22	650
C23	52 TO 53	L23	IF AMP.	R23	650
C24	54 TO 55	L24	IF AMP.	R24	650
C25	56 TO 57	L25	IF AMP.	R25	650
C26	58 TO 59	L26	IF AMP.	R26	650
C27	60 TO 61	L27	IF AMP.	R27	650
C28	62 TO 63	L28	IF AMP.	R28	650
C29	64 TO 65	L29	IF AMP.	R29	650
C30	66 TO 67	L30	IF AMP.	R30	650
C31	68 TO 69	L31	IF AMP.	R31	650
C32	70 TO 71	L32	IF AMP.	R32	650
C33	72 TO 73	L33	IF AMP.	R33	650
C34	74 TO 75	L34	IF AMP.	R34	650
C35	76 TO 77	L35	IF AMP.	R35	650
C36	78 TO 79	L36	IF AMP.	R36	650
C37	80 TO 81	L37	IF AMP.	R37	650
C38	82 TO 83	L38	IF AMP.	R38	650
C39	84 TO 85	L39	IF AMP.	R39	650
C40	86 TO 87	L40	IF AMP.	R40	650
C41	88 TO 89	L41	IF AMP.	R41	650
C42	90 TO 91	L42	IF AMP.	R42	650
C43	92 TO 93	L43	IF AMP.	R43	650
C44	94 TO 95	L44	IF AMP.	R44	650
C45	96 TO 97	L45	IF AMP.	R45	650
C46	98 TO 99	L46	IF AMP.	R46	650
C47	100 TO 101	L47	IF AMP.	R47	650
C48	102 TO 103	L48	IF AMP.	R48	650
C49	104 TO 105	L49	IF AMP.	R49	650
C50	106 TO 107	L50	IF AMP.	R50	650
C51	108 TO 109	L51	IF AMP.	R51	650
C52	110 TO 111	L52	IF AMP.	R52	650
C53	112 TO 113	L53	IF AMP.	R53	650
C54	114 TO 115	L54	IF AMP.	R54	650
C55	116 TO 117	L55	IF AMP.	R55	650
C56	118 TO 119	L56	IF AMP.	R56	650
C57	120 TO 121	L57	IF AMP.	R57	650
C58	122 TO 123	L58	IF AMP.	R58	650
C59	124 TO 125	L59	IF AMP.	R59	650
C60	126 TO 127	L60	IF AMP.	R60	650
C61	128 TO 129	L61	IF AMP.	R61	650
C62	130 TO 131	L62	IF AMP.	R62	650
C63	132 TO 133	L63	IF AMP.	R63	650
C64	134 TO 135	L64	IF AMP.	R64	650
C65	136 TO 137	L65	IF AMP.	R65	650
C66	138 TO 139	L66	IF AMP.	R66	650
C67	140 TO 141	L67	IF AMP.	R67	650
C68	142 TO 143	L68	IF AMP.	R68	650
C69	144 TO 145	L69	IF AMP.	R69	650
C70	146 TO 147	L70	IF AMP.	R70	650
C71	148 TO 149	L71	IF AMP.	R71	650
C72	150 TO 151	L72	IF AMP.	R72	650
C73	152 TO 153	L73	IF AMP.	R73	650
C74	154 TO 155	L74	IF AMP.	R74	650
C75	156 TO 157	L75	IF AMP.	R75	650
C76	158 TO 159	L76	IF AMP.	R76	650
C77	160 TO 161	L77	IF AMP.	R77	650
C78	162 TO 163	L78	IF AMP.	R78	650
C79	164 TO 165	L79	IF AMP.	R79	650
C80	166 TO 167	L80	IF AMP.	R80	650
C81	168 TO 169	L81	IF AMP.	R81	650
C82	170 TO 171	L82	IF AMP.	R82	650
C83	172 TO 173	L83	IF AMP.	R83	650
C84	174 TO 175	L84	IF AMP.	R84	650
C85	176 TO 177	L85	IF AMP.	R85	650
C86	178 TO 179	L86	IF AMP.	R86	650
C87	180 TO 181	L87	IF AMP.	R87	650
C88	182 TO 183	L88	IF AMP.	R88	650
C89	184 TO 185	L89	IF AMP.	R89	650
C90	186 TO 187	L90	IF AMP.	R90	650
C91	188 TO 189	L91	IF AMP.	R91	650
C92	190 TO 191	L92	IF AMP.	R92	650
C93	192 TO 193	L93	IF AMP.	R93	650
C94	194 TO 195	L94	IF AMP.	R94	650
C95	196 TO 197	L95	IF AMP.	R95	650
C96	198 TO 199	L96	IF AMP.	R96	650
C97	200 TO 201	L97	IF AMP.	R97	650
C98	202 TO 203	L98	IF AMP.	R98	650
C99	204 TO 205	L99	IF AMP.	R99	650
C100	206 TO 207	L100	IF AMP.	R100	650

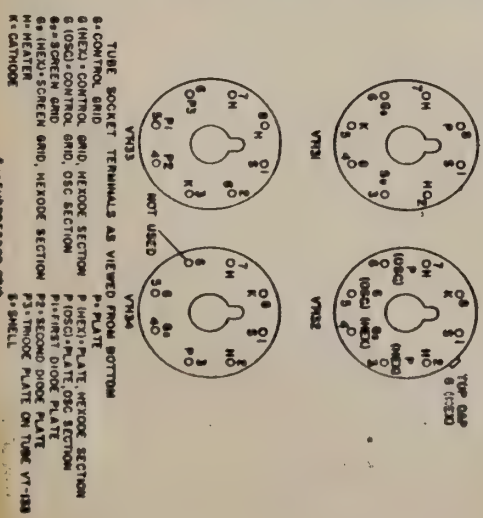

G & C Radio Supply Co.
 51 Varsity St., New York 7, N. Y.
 Telephone: CO 7-4405

h
c
u
o
o
o

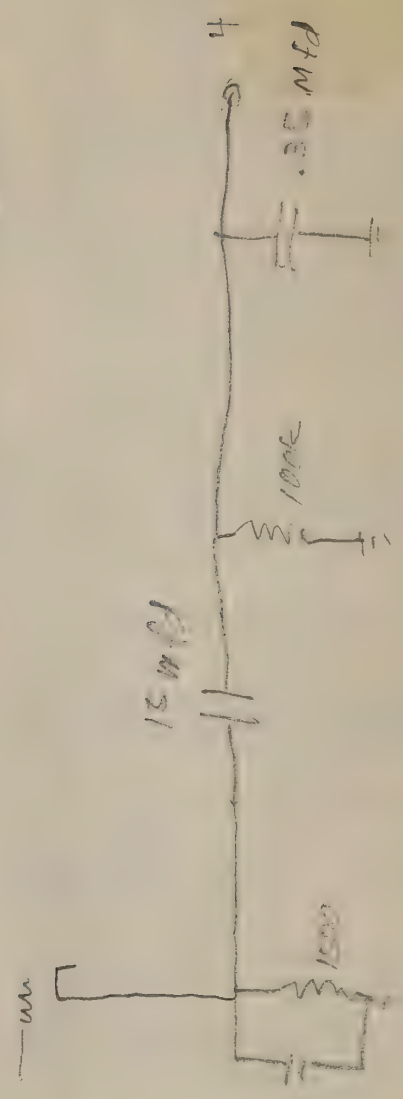

12V


12X⑤




SYMBOL T1
OUTPUT TRANSFORMER
RADIO RECEIVER 9C-434-B

6X4
CW OSCILLATOR
140 MC.

LESS THAN 2

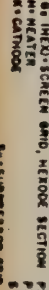

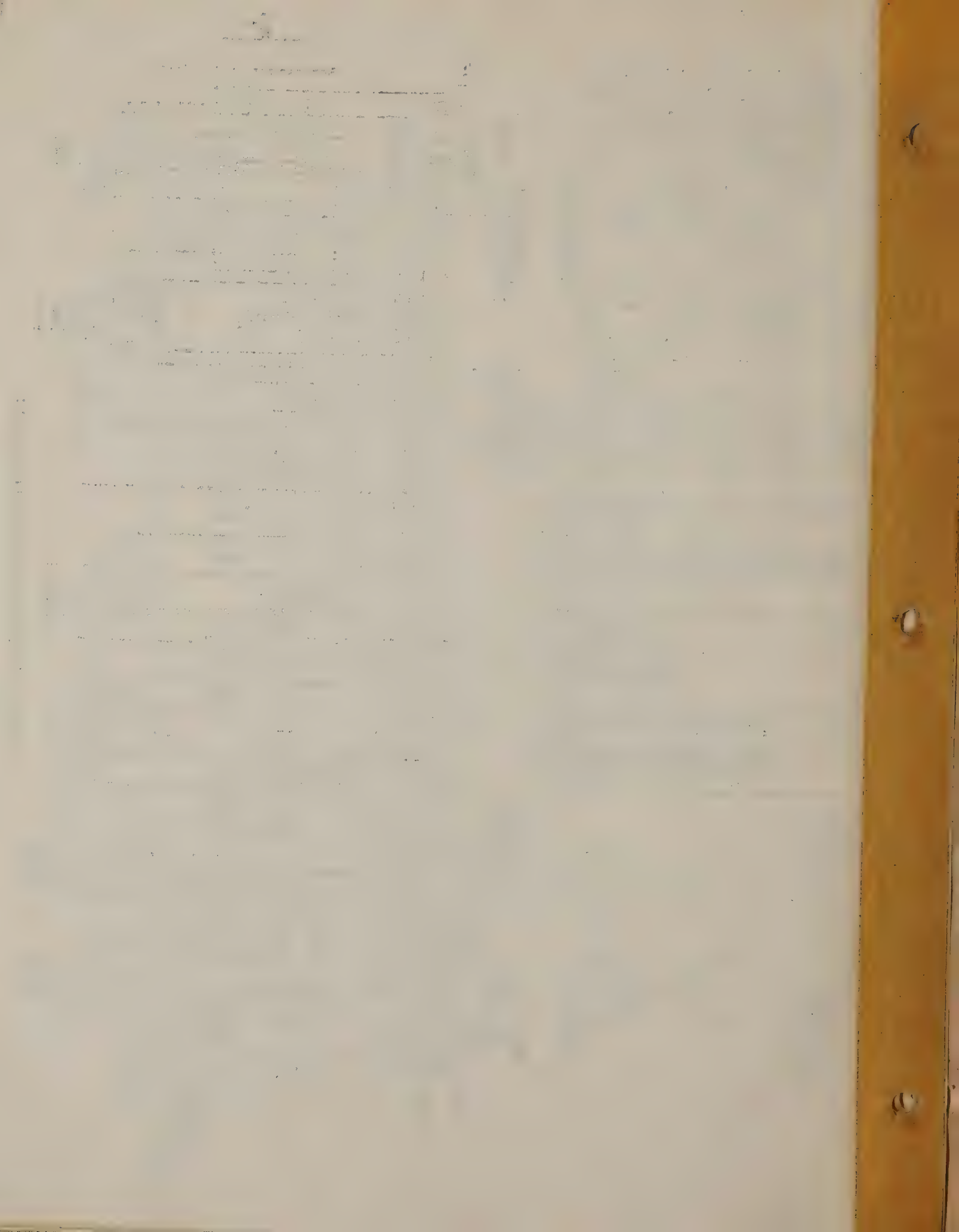


12K8




天

SEE SCHEMATIC DIAGRAM OF RECEIVING EQUIPMENT FOR JACK CONNECTIONS

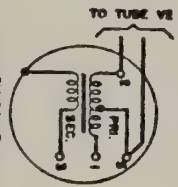


STROBIL. 25A
R-P ANTENNA

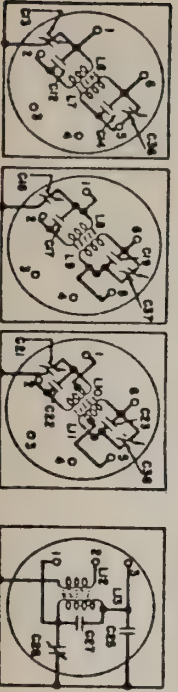


OUTPUT TRANSFORMER
RADIO RECEIVER DC-444-B

AS VIEWED FROM OUTSIDE

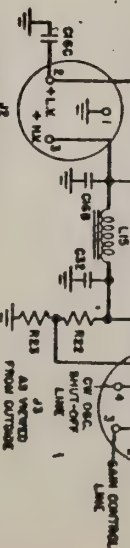


3. CONTROL SOCKET MATERIALS AS VIEWED FROM BOTTOM
4. INEAL. CONTROL AND. MIXED SECTION
5. (O)SCI. CONTROL AND. OSCI SECTION
6. INEAL. GREEN AND. MIXED SECTION
7. INEAL. GREEN AND. MIXED SECTION
8. HEATER
9. CONTROL
10. SUPPLEMENTS AND
11. PLATE
12. MIXED SECTION
13. MIXED SECTION
14. MIXED SECTION
100. MIXED SECTION


12A6
AUDIO AMP
(VT-124)

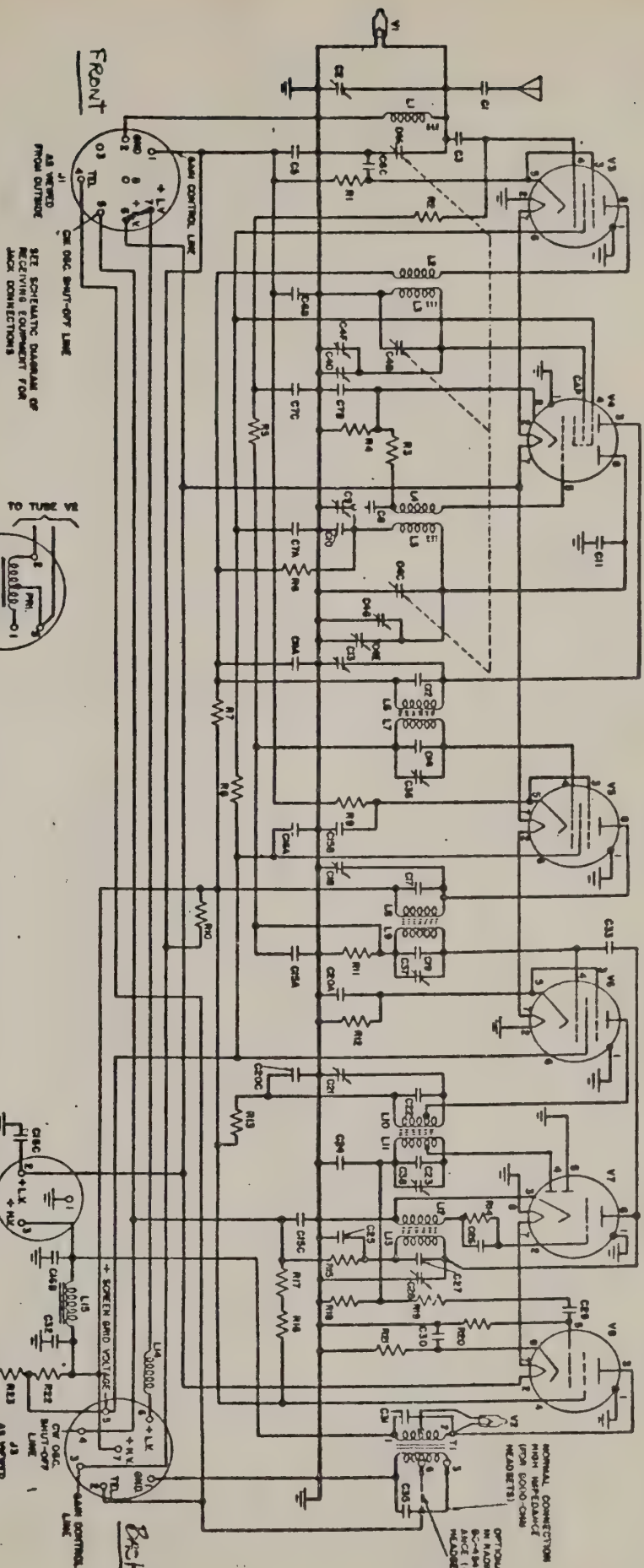

(

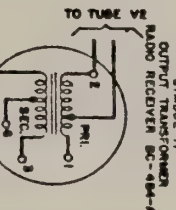


SYMBOL T1

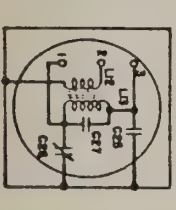

SYMBOL 24
CW OSCILLATOR

CONDUCTS IN A CON. SET, 14 COMMING UNIT, CIRCULATION, AND OUTPUT TRANSPORT. THE THERMAL UNITS ON THESE UNITS AGREE WITH THOSE SHOWN AT THE CORRESPONDING LOCATIONS OF THE THERMAL UNITS.

STANDARD	CAP ACTIONS	SYM BOL	DESCRIPTION	STYLING	REMARKS
C1	11 MWF	L1	ART. IN/PUT	R1	480
C2	13 MWF	L2, L3	PT. APP.	R2	2,000,000
C3	120 MWF	L4, L5	PT. OSG.	R3	81,000
C4	600 (147 MWF)	L6, L7	IN ST. IF	R4	620
C5	3 MWF	L8, L9	IN END IF	R5	80,000
C6	1,000,000,000 MWF	L10, L11	IN END IF	R6	200,000
C7	200 MWF	L12, L13	IN END IF	R7	200,000
C8	40 MWF	L14	PT. OSG.	R8	620
C9	300 MWF		PT. CHARGE, 182	R9	340,000
C10	3 MWF		PT. CHARGE	R10	100,000
C11	3 MWF		3 REMAINS	R11	340
C12	20 MWF			R12	200
C13	17 MWF			R13	200
C14	100,000,000 MWF			R14	100,000
C15	100,000,000 MWF			R15	100,000
C16	82,722,723 MWF			R16	81,000
C17	20 MWF			R17	510,000
C18	120 MWF			R18	510,000
C19	120 MWF			R19	100,000
C20	120,704,000 MWF			R20	2,000,000
C21	17 MWF			R21	1800
C22	180 MWF			R22	7000
C23	200 MWF			R23	7000
C24	100 MWF				
C25	100 MWF				
C26	180 MWF				
C27	180 MWF				
C28	34 MWF				
C29	200 MWF				
C30	15 MWF				
C31	15 MWF				
C32	3 MWF				
C33	3 MWF				
C34	730 MWF				
C35	17 MWF				
C36	17 MWF				
C37	17 MWF				
C38	17 MWF				

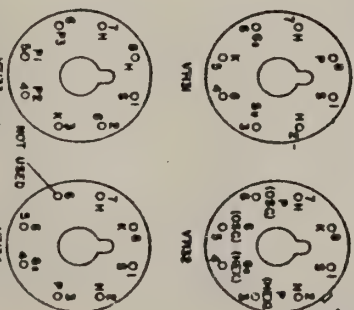


5. TUNE SOCKET	TERMINALS AS VIEWED FROM BOTTOM
6. CONTROL AND	P-PLATE
7. H-HEAT CONTROL AND	H-HEAT CONTROL SECTION
8. (OSC.) CONTROL AND	O (OSC.) CONTROL AND OSC SECTION
9. SCREEN AND	P-PIRST DOOR PLATE
10. H-HEAT SCREEN AND	H-HEAT SCREEN SECTION
11. HEATER	P-PIRST DOOR PLATE
12. D-DRUM	D-DRUM PLATE ON TANK VT-154
	P-BELL

12K8




張

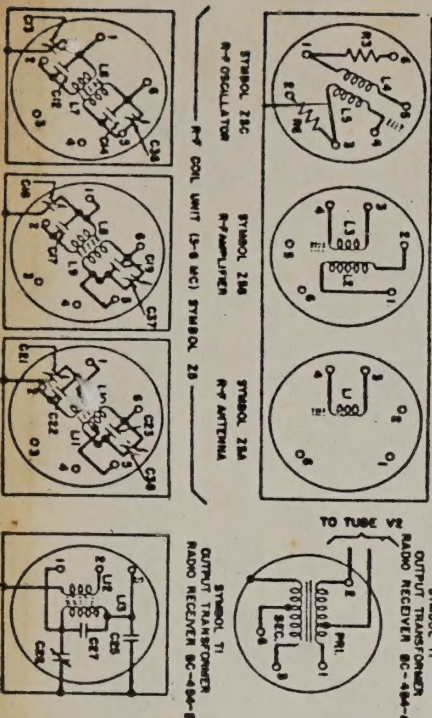SITE SCHEMATIC DIAGRAM OF RECEIVING EQUIPMENT FOR JACK CONNECTIONS



CAP ACTIONS		MODIFICATIONS		NEAR TOWNS	
SYMBOL	DESCRIPTION	SYMBOL	DESCRIPTION	SYMBOL	OWNS
C1	11 MWF.	L1	ART. IN PUT	R1	620
C2	400 MWF.	L2, L3	RT. AMP.	R2	2,000,000
C3	150 MWF.	L4, L5	RT. OSC.	R3	81,000
C4	14 TO 61	L6, L7	IN ST. IF	R4	620
C5	300 MWF. (47 MWF.)	L8, L9	IN ST. IF	R5	340,000
C6 (A,B,C)	1.05/05/05 MWF	L10, L11	IN ST. IF	R6	200,000
C7 (A,B,C)	02/02/02/02 MWF	L12, L13	DR. OSC.	R7	200,000
C8	200 MWF.	U4	RT. CHOICE, 1/2	R8	200
C9	40 MWF.		MICRO-WAVE	R9	620
C10	385 MWF.		RT. CHOICE	R10	340,000
C11	3 MWF.	U5	3 INCHES	R11	100,000
C12	17 MWF.			R12	340
C13	17 MWF.			R13	100,000
C14	180 MWF.			R14	50,000
C15 (A,B,C)	02/03/03/03 MWF			R15	81,000
C16 (A,B,C)	22/22/22 MWF			R16	81,000
C17	180 MWF.			R17	81,000
C18	17 MWF.			R18	100,000
C19	17 MWF.			R19	100,000
C20 (A,B,C)	02/03/03/03 MWF			R20	2,000,000
C21	17 MWF.			R21	81,000
C22	180 MWF.			R22	7000
C23	180 MWF.			R23	7000
C24	200 MWF.				
C25	100 MWF.				
C26	170 MWF.				
C27	180 MWF.				
C28	34 MWF.				
C29	02 MWF.				
C30	13 MWF.				
C31	001 MWF.				
C32	3 MWF.				
C33	17 MWF.				
C34	200 MWF.				
C35	17 MWF.				
C36	17 MWF.				
C37	17 MWF.				
C38	17 MWF.				
C39	17 MWF.				
C40	17 MWF.				

74442

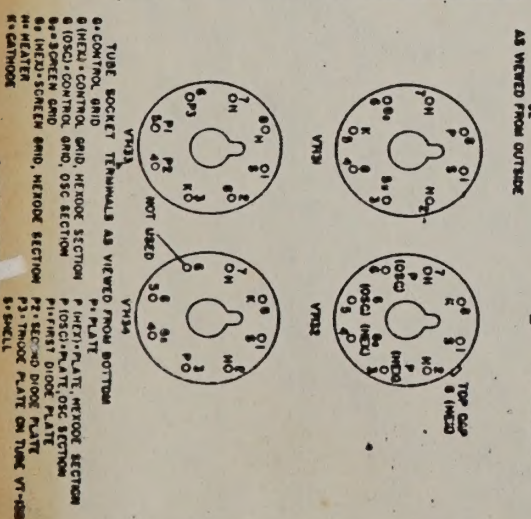

THESE TWO GROUPS OF LOCATIONS ARE
PRACTICAL

